



GTU
Electronics Engineering

ELEC 331
Electronic Circuits 2

Fall Semester

Instructor: Assist. Prof. Önder Şuvak

HW 9
Questions and Answers

Updated November 17, 2017 - 13:04

Assigned:

Due:

Answers Out:

Late Due:

Contents

Title Page	1
Contents	1
Question 1	2
Question	2
Solution	3
Question 2	6
Question	6
Solution	7
Question 3	21
Question	21
Solution	22
Question 4	29
Question	29
Solution	30

Phase Margin as a Measure of Stability in Feedback Systems**Sedra 8.73**

8.73 An amplifier has a dc gain of 10^5 and poles at 10^5 Hz, 3.16×10^5 Hz, and 10^6 Hz. Find the value of β , and the corresponding closed-loop gain, for which a phase margin of 45° is obtained.


Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: Open-loop and closed loop gains in feedback, feedback factor, stability, phase margin as a stability measure, transfer functions, magnitude and phase Bode plots, phases at the poles of a transfer function when the poles are far apart.

Magnitude Bode plot for $A(jf)$

$$20 \log_{10} |10^5| = 100 \text{ dB}$$

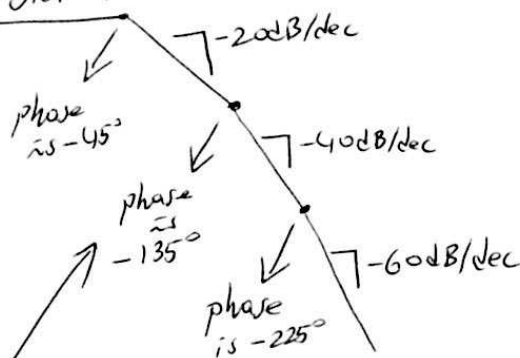

The asymptotic Bode plot and the phase values are accurate if the poles of $A(jf)$ are far apart.

→ β is given to be indep of frequency, positive and real.

→ Note that

$$20 \log_{10} |A(jf)\beta| = 20 \log_{10} |A(jf)| - 20 \log_{10} \left| \frac{1}{\beta} \right|$$

$$\angle A(jf)\beta = \angle A(jf) \quad \text{since } \beta \text{ is real and positive.}$$

→ Phase margin to be 45°

$$\text{then } |A(jf_u)\beta| = 1 \quad \text{and} \quad \angle A(jf_u)\beta = -(180^\circ - 45^\circ) = -135^\circ$$

Since β is real and positive, the unity gain frequency f_u (for $A(jf)\beta$) needs to be at the second pole of $A(jf)$. See here.

→ Note that

$$A(jf) = \frac{10^5}{\left(1 + \frac{jf}{10^5}\right) \left(1 + \frac{jf}{3.16 \times 10^5}\right) \left(1 + \frac{jf}{10^6}\right)}$$

Scanned by CamScanner

①

Now solve for β in

Sedra
8.73
contin.

$$|A(jf)\beta| = \left| \frac{10^5 \beta}{\left(1 + \frac{jf_u}{10^5}\right) \left(1 + \frac{jf_u}{3.16 \times 10^5}\right) \left(1 + \frac{jf_u}{10^6}\right)} \right| = 1$$

where $f_u = 3.16 \times 10^5$ Hz (the second pole)

then


$$1 = \frac{10^5 \beta}{\sqrt{1 + \left(\frac{3.16 \times 10^5}{10^5}\right)^2} \sqrt{1 + \left(\frac{3.16 \times 10^5}{3.16 \times 10^5}\right)^2} \sqrt{1 + \left(\frac{3.16 \times 10^5}{10^6}\right)^2}}$$

$$= \frac{10^5 \beta}{\sqrt{1 + (3.16)^2} \sqrt{2} \sqrt{1 + (0.316)^2}}$$

$$\beta = 4.9 \times 10^{-5}$$

$$\text{then } \frac{1}{\beta} = 2.03 \times 10^4$$

$$\text{and } 20 \log_{10} \left| \frac{1}{\beta} \right| = 86.1 \text{ dB}$$

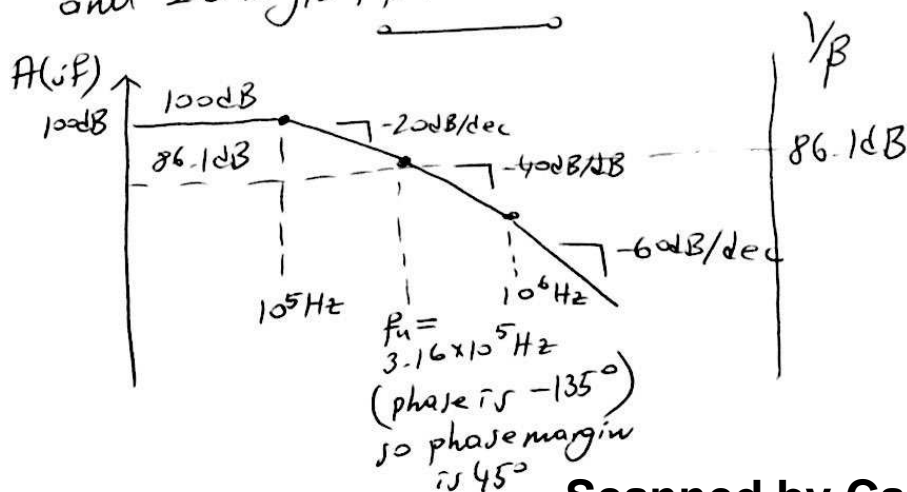

Scanned by CamScanner (2)

Midband gain with feedback

$$A_f = \frac{10^5}{1 + 10^5(4.9 \times 10^{-5})} \approx 16.9 \times 10^3$$

$$= \frac{A}{1 + A\beta}$$

Sedra
8-73
contin.

Analysis of Feedback in OpAmp Circuits

Sedra 8.26

***8.26** For each of the op-amp circuits shown in Fig. P8.26, identify the feedback topology and indicate the output variable being sampled and the feedback signal. In each case, assuming the op amp to be ideal, find an expression for β , and hence find A_f .

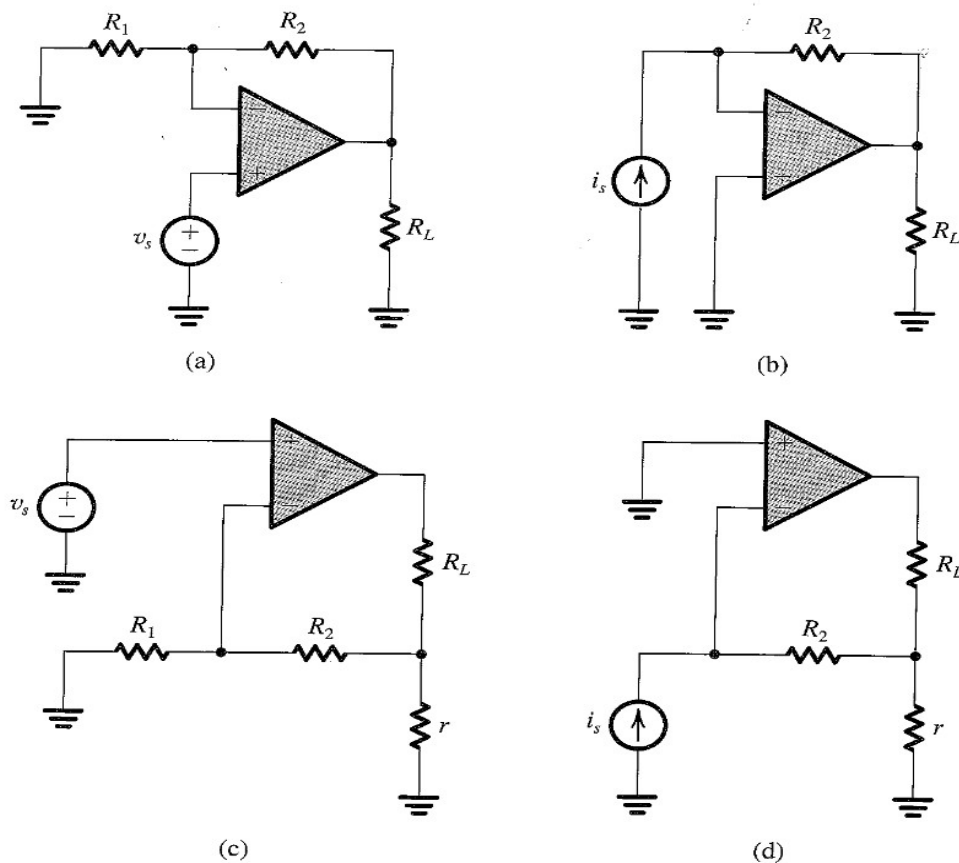


FIGURE P8.26

Notes: None.


Additional Tasks: None.

Necessary Knowledge and Skills: The four types of feedback, identification and modeling of feedback networks, feedback-loaded amplifier analysis, gain and input/output imp. computation.

This is a voltage amplifier with voltage series feedback.


Sedra
8.26a)

(*)

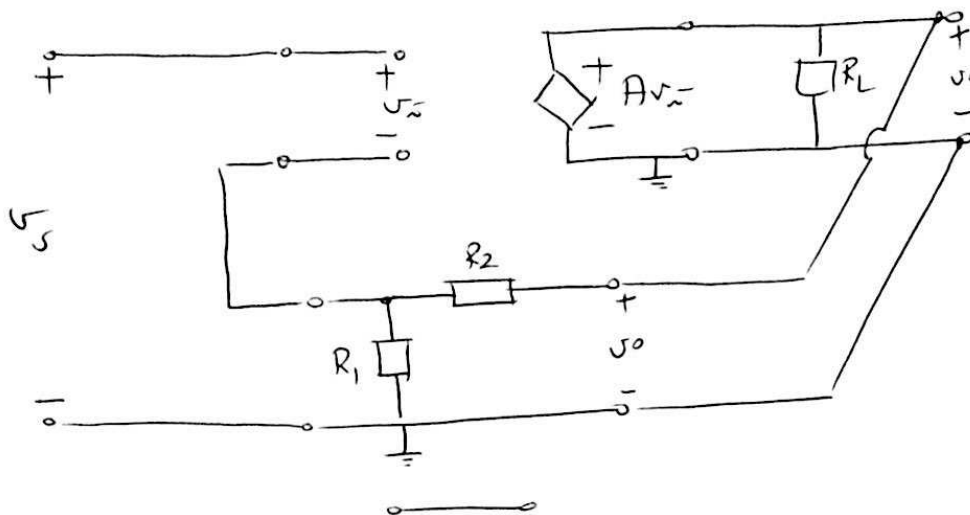


Analyze the feedback network:

(**)

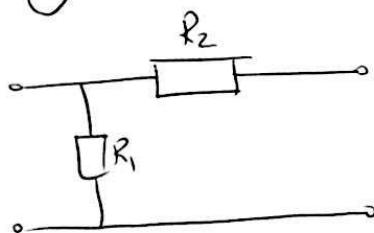

\equiv

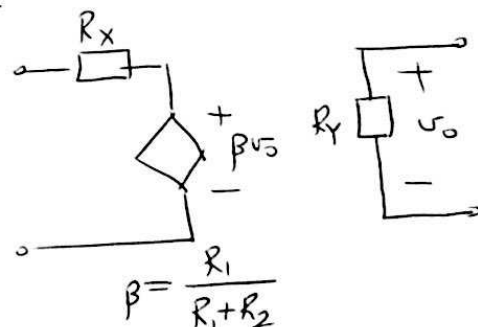


$$\beta = \frac{R_1}{R_1 + R_2}$$

$$R_X = R_1 \parallel R_2$$

$$R_Y = R_1 + R_2$$

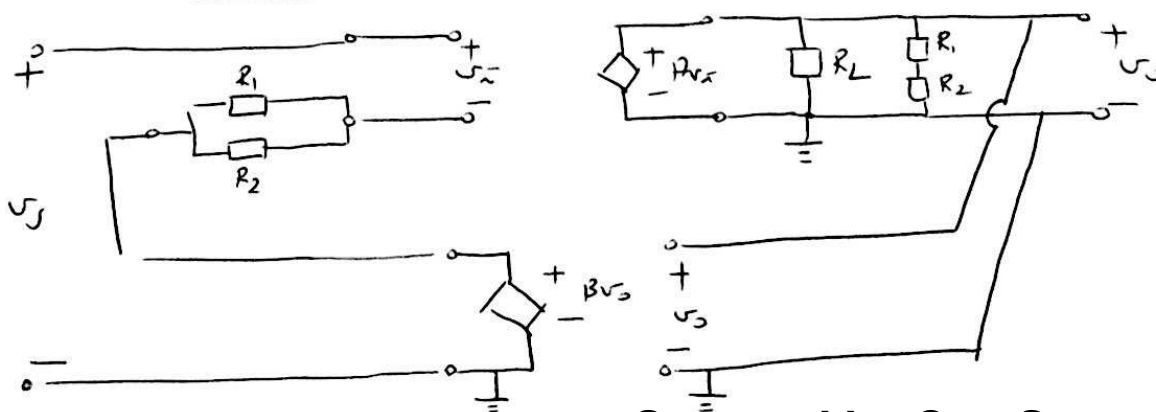(***) Schematic of VFA, \$A\$, and the feedback network (idealized)



Scanned by CamScanner (1)

\Rightarrow Kill β ($\beta=0$)

\Rightarrow Analyze $V_{A, R}$

Sadra
8.26a)
contin.

$$r_{in, V_{A, R}} = \infty \quad \left(\text{would be } r_{in} + R_1 \parallel R_2 \text{ if the opamp were nonideal} \right)$$

$$r_{out, V_{A, R}} = 0 \quad \left(\text{would be } r_{out} \parallel R_L \parallel (R_1 + R_2) \text{ if the opamp were nonideal} \right)$$

$$A_{V_{A, R}} = A \left(\frac{r_{in}}{r_{in} + R_1 \parallel R_2} A \frac{R_L \parallel (R_1 + R_2)}{R_L \parallel (R_1 + R_2) + r_{out}} \right) \quad \left(\text{if the opamp were nonideal} \right)$$

Now analyze the whole feedback amplifier


$$r_{in, f} = r_{in, V_{A, R}} \quad (1 + \beta A_{V_{A, R}}) = \infty \quad \left(\text{or plug in the value above and } \beta \right)$$

$$r_{out, f} = \frac{r_{out, V_{A, R}}}{1 + \beta A_{V_{A, R}}} = 0$$




$$A_f = \frac{A_{V_{A, R}}}{1 + \beta A_{V_{A, R}}} = \frac{A}{1 + \frac{R_1}{R_1 + R_2} A} \approx \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} \quad (\text{if } A \gg 1)$$

This is a transresistance amplifier with voltage-shunt feedback.

Sedra 8.26b)

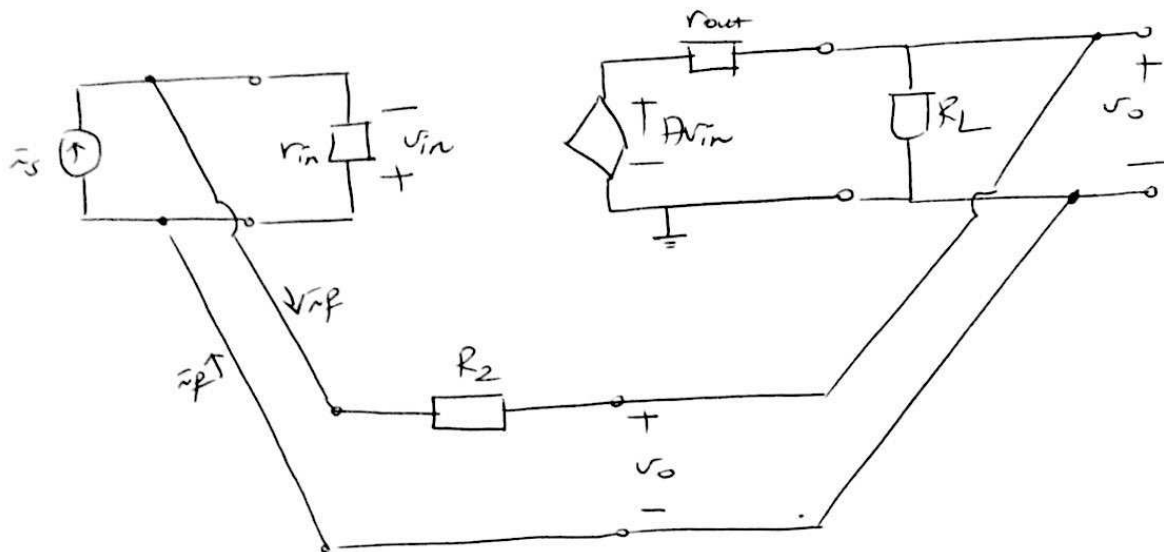

Analysis of the feedback network

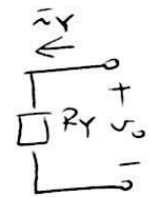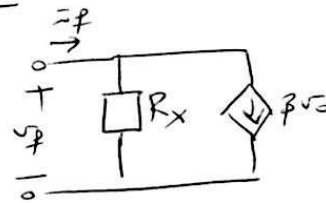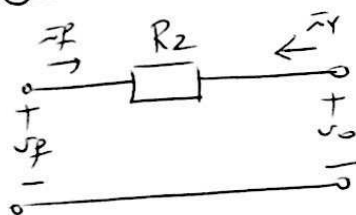

$$\beta = \frac{\tilde{v}_f}{v_o} \Big|_{v_s=0} = \frac{-\tilde{v}_Y}{v_o} = -\frac{1}{R_2}$$


$$R_Y = \frac{v_o}{\tilde{v}_Y} \Big|_{v_s=0} = R_2$$

$$R_X = \frac{v_f}{\tilde{v}_f} \Big|_{v_o=0} = R_2$$

Scanned by CamScanner

TRA, FE and the idealized feedback network

Sedra 8.26b)

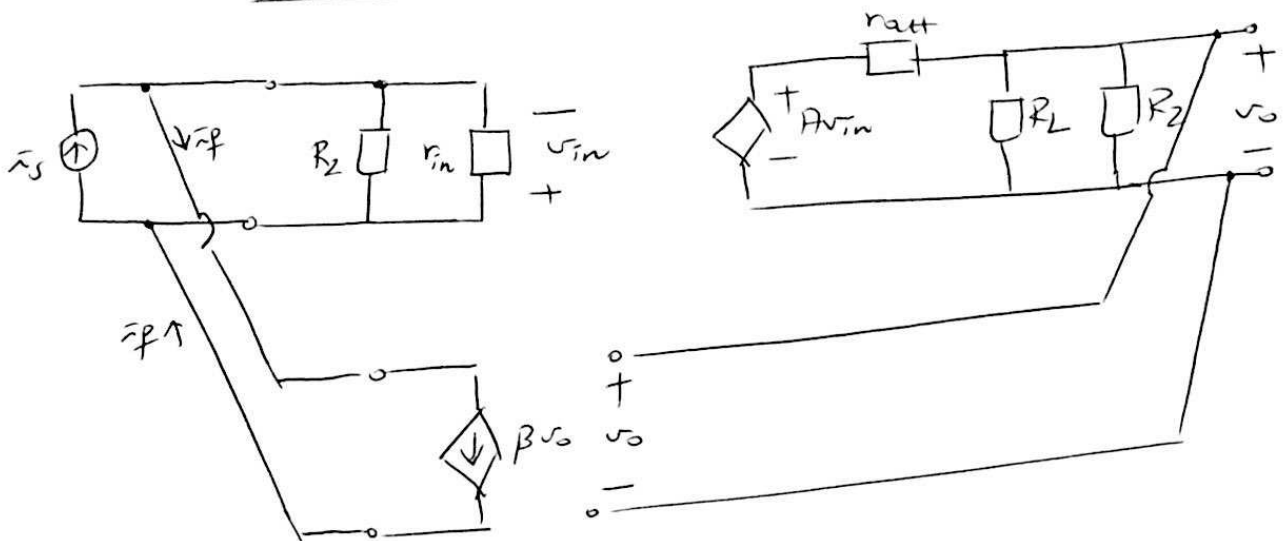

Kill β ($\beta=0$) and analyze TRA, FE

$$r_{in, TRA, FE} = R_2 \parallel r_{in}$$

$$r_{out, TRA, FE} = r_{out} \parallel R_L \parallel R_2$$

$$A_{TRA, FE} = \left[-R_2 \parallel r_{in} \right] A \left[\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}} \right]$$

Note that with $r_{in} = \infty$ and $r_{out} = 0$ the above would be

$$r_{in, TRA, FE} = R_2$$

$$r_{out, TRA, FE} = 0$$

$$A_{TRA, FE} = -R_2 \cdot A$$

Scanned by CamScanner

2

Now analyze the whole feedback ampli.

Sedra 8.26
b)
contin

$$r_{in,f} = \frac{r_{in,TRAP,PE}}{1 + \beta A_{TRAP,PE}}$$

$$= \frac{R_2 \parallel r_{in}}{1 + \left(-\frac{1}{R_2}\right)(-R_2 \parallel r_{in})A \left(\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}}\right)}$$

with $r_{in} = +\infty$
 $r_{out} = 0$

$$\approx \frac{R_2}{1 + \left(-\frac{1}{R_2}\right)(-R_2)A}$$

$$= \frac{R_2}{1 + A}$$

with $A \gg 1 \approx 0$

$$r_{out,f} = \frac{r_{out,TRAP,PE}}{1 + \beta A_{TRAP,PE}}$$

with $r_{in} = +\infty$
 $r_{out} = 0$

$$\approx \frac{0}{1 + \left(-\frac{1}{R_2}\right)(-R_2)A}$$

$$A_f = \frac{A_{TRAP,PE}}{1 + \beta A_{TRAP,PE}} = \frac{\left[-R_2 \parallel r_{in}\right] A \left[\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}}\right]}{1 + \left(-\frac{1}{R_2}\right)\left[-R_2 \parallel r_{in}\right] A \left[\frac{R_L \parallel R_2}{R_L \parallel R_2 + r_{out}}\right]}$$

Scanned by CamScanner 3

$$A_f \stackrel{\sim}{=} \frac{-R_2 A}{1 + \left(-\frac{1}{R_2}\right)(-R_2)A}$$

with $r_{in} = +\infty$
 $r_{out} = 0$

$$= \frac{-R_2 A}{1 + A}$$


$$\text{with } A \gg 1 \stackrel{\sim}{=} -R_2$$




Sedra
8.26
Cont.

Transconductance amplifier with
current-series feedback

Sedra
8.26c

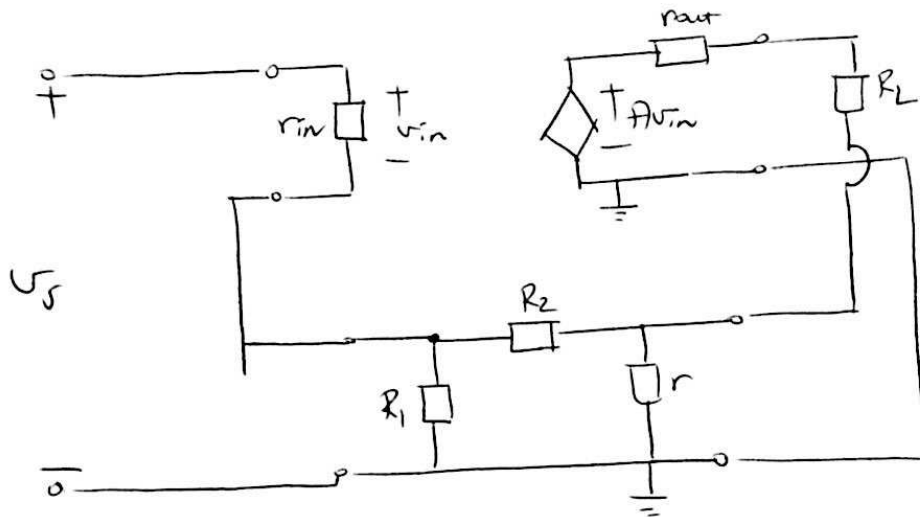


Redraw the above schematic:

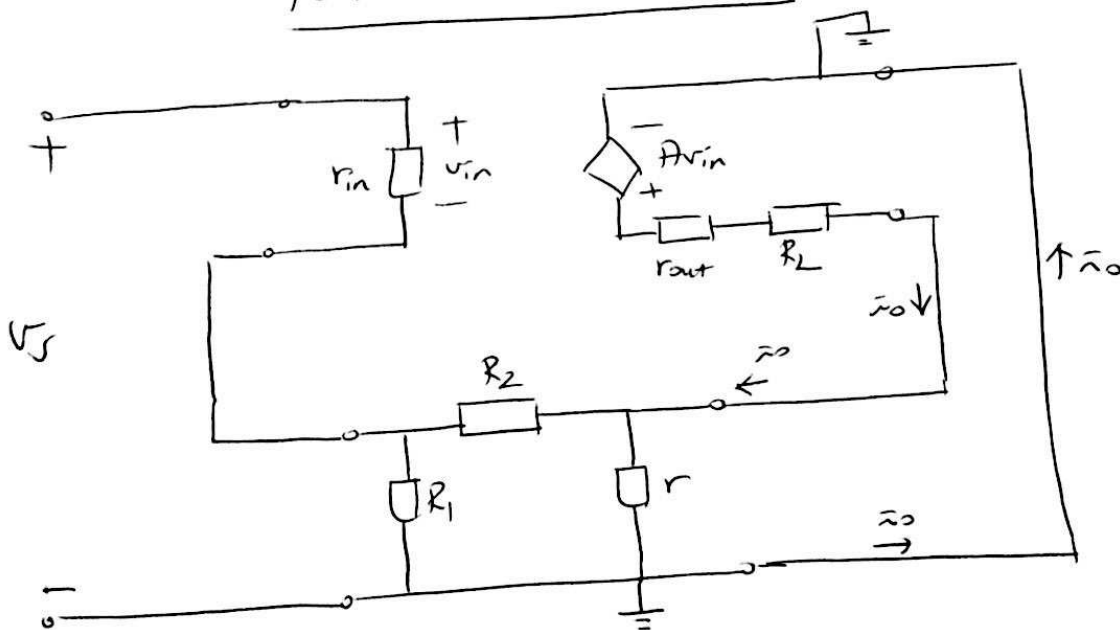

Analyze the feedback network

Sedra
8.26c

cont -

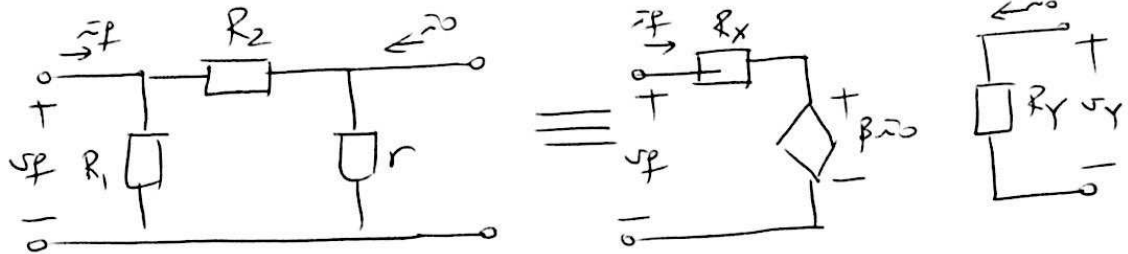


$$\beta = \frac{v_f}{i_o} \Big|_{v_f=0} = \frac{r}{r+R_1+R_2} \cdot R_1$$

$$R_x = \frac{v_f}{i_f} \Big|_{i_o=0} = R_1 \parallel (R_2 + r)$$

$$R_y = \frac{v_y}{i_o} \Big|_{v_f=0} = r \parallel (R_1 + R_2)$$

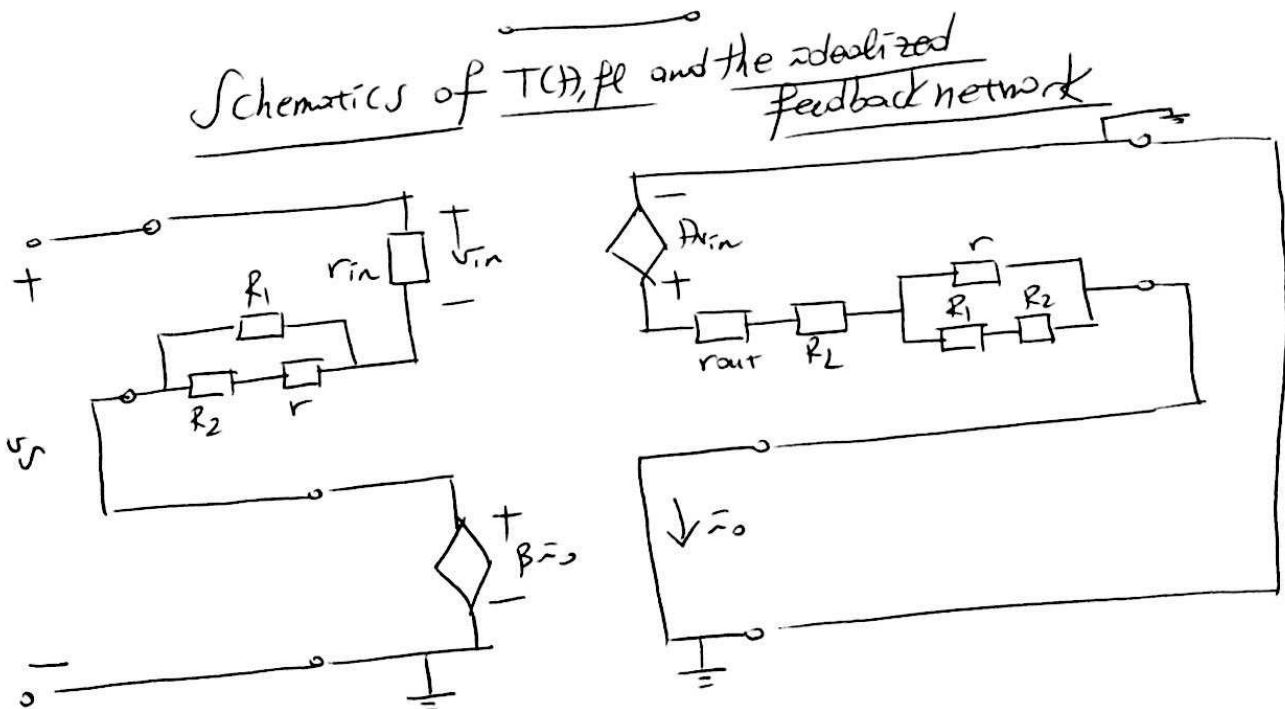Schematics of T(s), β and the idealized feedback network



Scanned by CamScanner 2

\Rightarrow Kill β ($\beta=0$)

\Rightarrow Analyze TCA, $\beta=0$

Sedra
8.26c)
contin.

$$r_{in, TCA, \beta=0} = r_{in} + R_1 \parallel (R_2 + r)$$

$$r_{out, TCA, \beta=0} = r_{out} + R_L + r \parallel (R_1 + R_2)$$

$$A_{TCA, \beta=0} = \frac{r_{in}}{r_{in} + R_1 \parallel (R_2 + r)} A \frac{1}{r_{out} + R_L + r \parallel (R_1 + R_2)}$$



Note that with $r_{in} = \infty$
 $r_{out} = 0$

$$r_{in, TCA, \beta=0} \approx \infty$$

$$r_{out, TCA, \beta=0} \approx R_L + r \parallel (R_1 + R_2)$$

$$A_{TCA, \beta=0} \approx A \frac{1}{R_L + r \parallel (R_1 + R_2)}$$



Now analyze the whole feedback amplifier

Sedra
8.26c
contin.

$$r_{in,f} = (1 + \beta A_{TCA,PE}) r_{in,TCA,PE}$$

$$r_{out,f} = (1 + \beta A_{TCA,PE}) r_{out,TCA,PE}$$

$$A_f = \frac{A_{TCA,PE}}{1 + \beta A_{TCA,PE}}$$

Note that with $r_{in} = +\infty$
 $r_{out} = 0$

$$\rightarrow r_{in,f} = +\infty$$

$$\rightarrow r_{out,f} = \left(1 + \frac{r R_1}{r + R_1 + R_2} A \frac{1}{R_L + r \parallel (R_1 + R_2)} \right) \cdot [R_L + r \parallel (R_1 + R_2)]$$

$$\text{with } A \gg 1 \approx \frac{r R_1 A}{r + R_1 + R_2}$$

$$\rightarrow A_f \approx \frac{A \frac{1}{R_L + r \parallel (R_1 + R_2)}}{1 + \frac{r R_1}{r + R_1 + R_2} A \frac{1}{R_L + r \parallel (R_1 + R_2)}}$$


$$\text{with } A \gg 1 \approx \frac{r + R_1 + R_2}{r R_1} = \frac{1}{r \parallel R_1} + \frac{R_2}{r R_1}$$

Scanned by CamScanner


(4)

This is a current amplifier with
current-shunt feedback

Sedra
8.26d

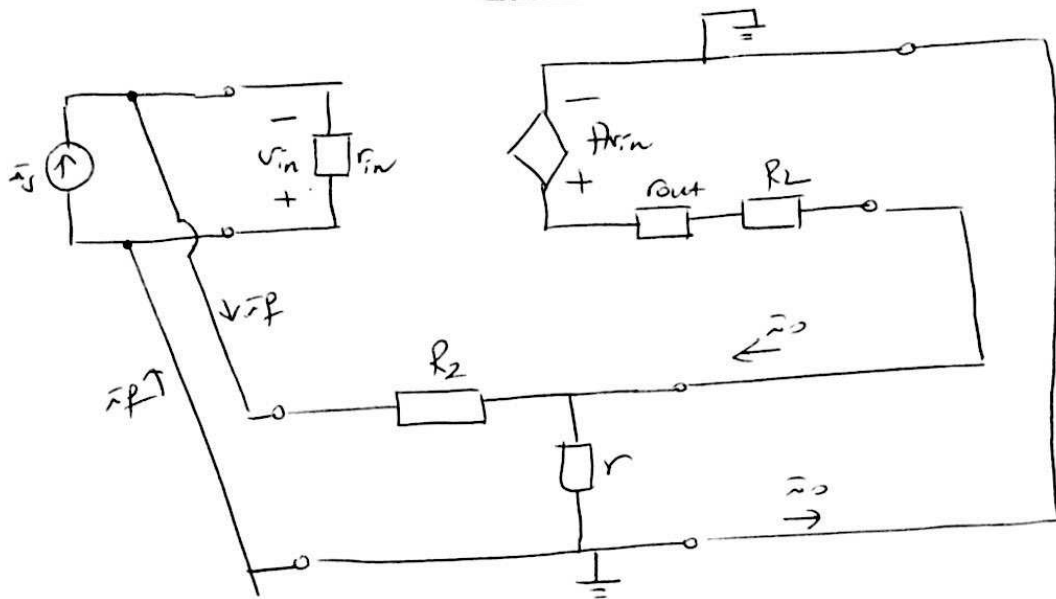

Model the feedback network

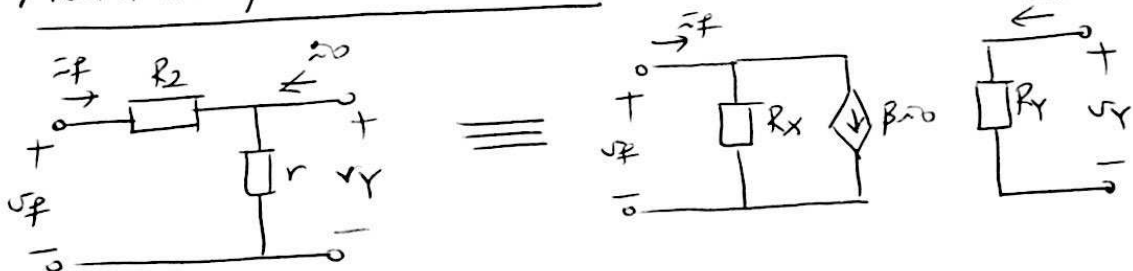

$$R_X = \frac{v_f}{i_f} \Big|_{i_o=0} = R_2 + r$$

$$R_Y = \frac{v_Y}{i_o} \Big|_{v_f=0} = R_2 \parallel r$$



$$\beta = \frac{i_f}{i_o} \Big|_{v_f=0} = -\frac{r}{r+R_2}$$

Scanned by CamScanner

Schematic of CA, FE and the idealized feedback network

Sedra
8.26d

cont.

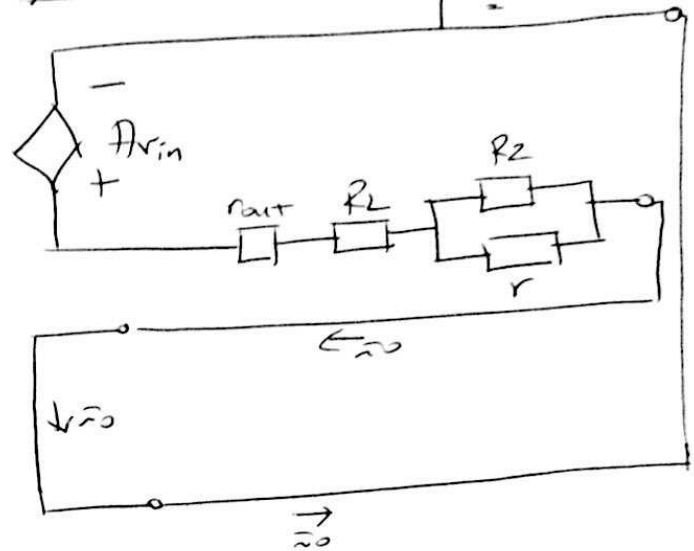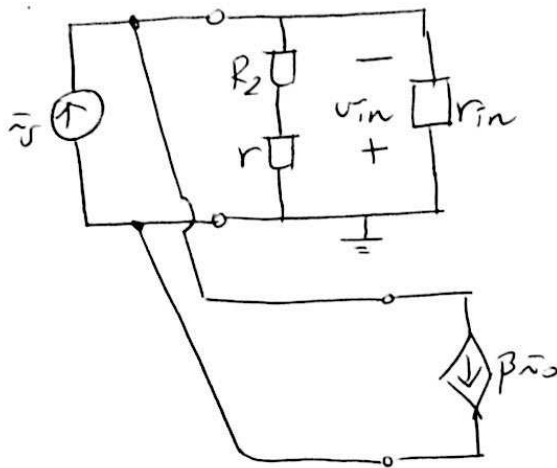

\Rightarrow kill β ($\beta=0$)

\Rightarrow Analyze CA, FE

$$r_{in, CA, FE} = r_{in} \parallel (R_2 + r)$$

$$r_{out, CA, FE} = r_{out} + R_L + R_2 \parallel r$$

$$A_{CA, FE} = - \frac{R_2 + r}{R_2 + r + r_{in}} \cdot A \cdot \frac{1}{r_{out} + R_L + R_2 \parallel r}$$

—————

Scanned by CamScanner (2)

With $r_{in} = +\infty$
 $r_{out} = 0$

Jedra
8.26d)

$$r_{in, CH, PE} \cong R_2 + r$$

$$r_{out, CH, PE} \cong R_L + R_2 \parallel r$$

$$A_{CH, PE} \cong -A \frac{(R_2 + r)}{R_L + (R_2 \parallel r)}$$

→
Analyze the whole current amplifier:

$$A_f = \frac{A_{CH, PE}}{1 + \beta A_{CH, PE}}$$

With $r_{in} = +\infty$
 $r_{out} = 0$

$$\cong \frac{-A \frac{(R_2 + r)}{R_L + (R_2 \parallel r)}}{1 + \left(\frac{-r}{r + R_2}\right)(-A) \left(\frac{R_2 + r}{R_L + R_2 \parallel r}\right)}$$

With $A \gg 1$

$$\cong \frac{-A \frac{(R_2 + r)}{R_L + R_2 \parallel r}}{rA \frac{1}{R_L + R_2 \parallel r}} = -\frac{R_2 + r}{r} = -\left[1 + \frac{R_2}{r}\right]$$

→

$$r_{in, f} = \frac{r_{in, CH, PE}}{1 + \beta A_{CH, PE}} \cong \frac{R_2 + r}{1 + \left(\frac{-r}{r + R_2}\right)(-A) \left(\frac{R_2 + r}{R_L + R_2 \parallel r}\right)}$$

with $r_{in} = +\infty$
 $r_{out} = 0$

with $A \gg 1$

$$\cong \frac{1}{rA} \left[(R_2 + r) \left[R_L + \frac{R_2 r}{R_2 + r} \right] \right]$$

$$= \frac{(R_2 + r) R_L + R_2 r}{rA}$$

Scanned by CamScanner (3)

$$r_{out,f} = (1 + \beta A_{CA,fl}) r_{out,fl}$$

Sedra
8.26 d)
contin.

with
 $r_{in} = +\infty$
 $r_{out} = 0$

$$\approx \left[1 + \left(\frac{-r}{r+R_2} \right) (-A) \left[\frac{R_2+r}{R_L+R_2//r} \right] \right] \left(\frac{R_L+R_2//r}{R_L} \right)$$


with
 $A \gg 1$

$$\approx A r \frac{R_L+R_2//r}{R_L+R_2//r} = A r$$

—————

Voltage-Shunt Feedback on a Trans-Resistance Amplifier**Rashid 10.42**

10.42 The MOS amplifier shown in Fig. P10.42 is biased to have the following small-signal MOS parameters: $g_{m1} = 1.2 \text{ mA/V}$ and $r_{o1} = 25 \text{ k}\Omega$. If $R_F = 100 \text{ k}\Omega$, then $R_D = 2 \text{ k}\Omega$ and $C_F = 10 \text{ nF}$. Determine (a) the voltage gain without feedback $A = v_o/i_s$, (b) the voltage gain with feedback A_f , and (c) the high cutoff frequency f_H .

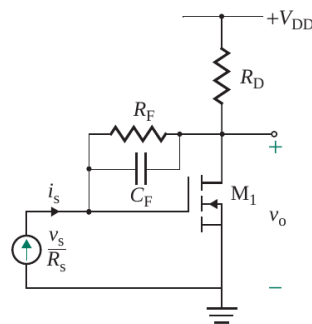FIGURE P10.42


Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: Trans-resistance amplifiers, voltage-shunt feedback, identification and modeling of feedback networks, feedback-loaded amplifier analysis, gain and input/output impedance calculations, OCTC for approximating high-frequency cut-off, transfer functions and high-frequency cut-off and zero/pole approximations.

Voltage-Shunt Feedback


Rashid
10.42

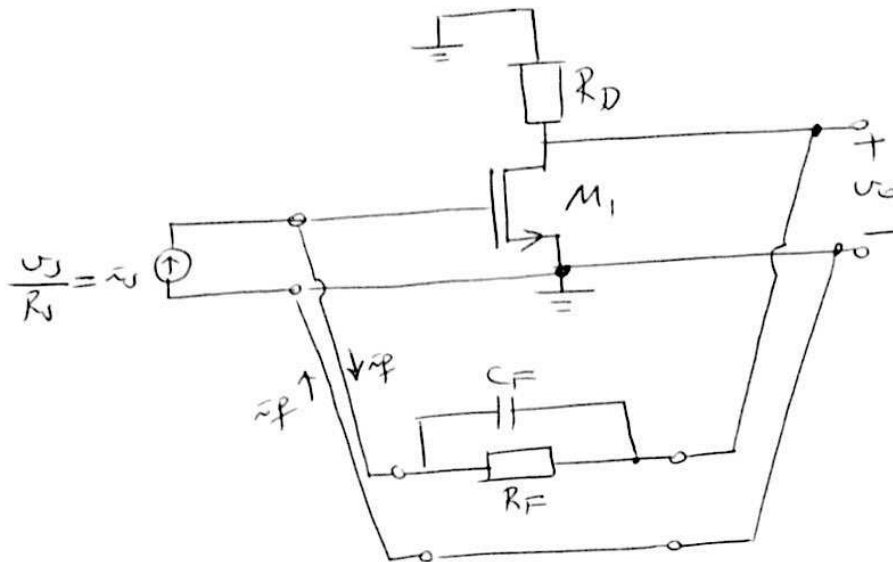

(*)

Transresistance
amplifier
with
voltage-shunt
feedback

Analyze the feedback network:

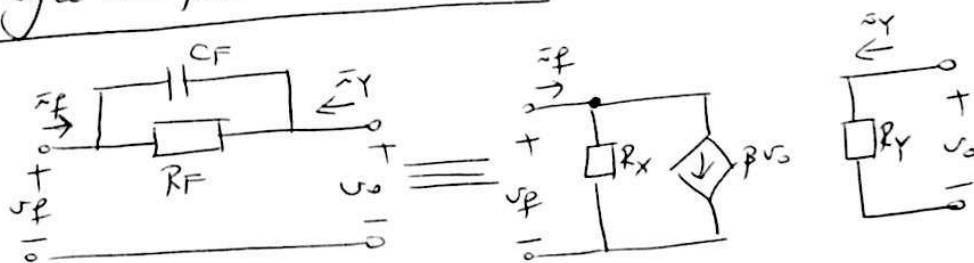

$$Z_X = \frac{v_o}{i_f} \Big|_{v_o=0} = R_F \parallel C_F$$

$$Z_Y = \frac{v_o}{i_f} \Big|_{v_o=0} = R_F \parallel C_F$$

$$\beta(s) = \frac{i_f}{v_o} \Big|_{v_o=0} = -\frac{i_f}{v_o} \Big|_{v_o=0} = \frac{-1}{R_F \parallel \frac{1}{sC_F}}$$


Scanned by CamScanner

$$\begin{aligned} \beta(s) &= \frac{-1}{\frac{R_F \frac{1}{sC_F}}{R_F + \frac{1}{sC_F}}} \\ &= - \frac{R_F + \frac{1}{sC_F}}{R_F \frac{1}{sC_F}} \\ &= - \frac{1 + sC_F R_F}{R_F} \end{aligned}$$

Rashed
10.42
contin.

$$\beta(s) = \underbrace{\left(-\frac{1}{R_F}\right)}_{\text{call this } \beta \text{ (midband value)}} \left[1 + \underbrace{\left(\frac{s}{C_F R_F}\right)}_{\text{call this } \omega_z} \right]$$

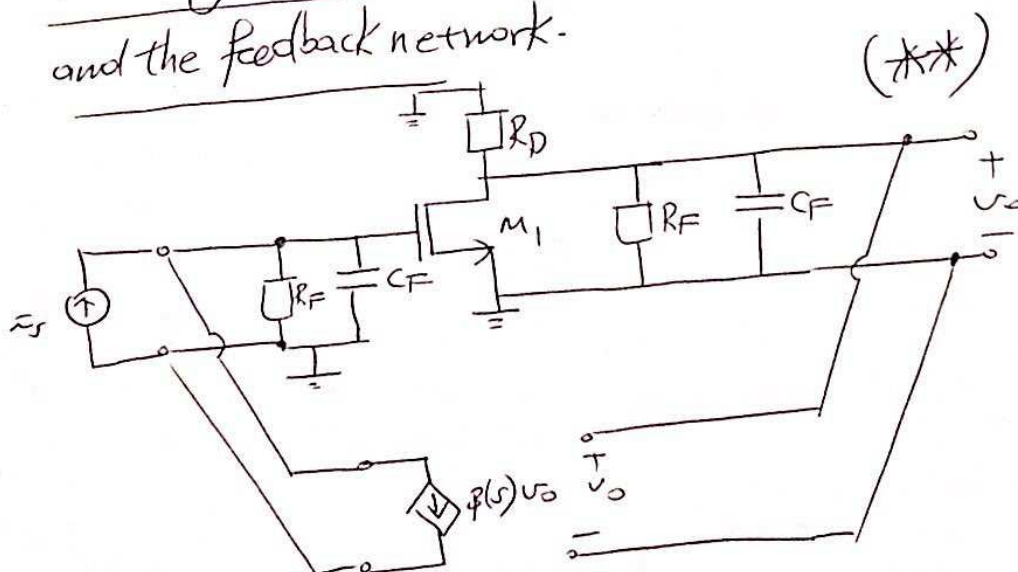Identify TFA, RL (feedback-loaded trans-resistance amplifier)
and the feedback network.



Scanned by CamScanner²

Kill $\beta \Rightarrow \beta \rightarrow 0$

Now analyze TFA, FE:

marked
10.42
contin.

$$A_{TFA, FE} = \frac{v_o}{v_s} = R_F (-g_m) [R_D // R_F // r_{o1}]$$

$$r_{in, TFA, FE} = R_F$$

$$r_{out, TFA, FE} = R_D // R_F // r_{o1}$$

$$W_{H, TFA, FE} = ?$$

$$\tau_1 = R_F C_F$$

$$\tau_2 = C_F (R_D // R_F // r_{o1})$$

$$W_{H, TFA, FE} = \frac{1}{\tau_1 + \tau_2}$$

Note that the frequency response of the gain is:

$$A_{TFA, FE}(j\omega) = \frac{A_{TFA, FE}}{1 + \frac{j\omega}{W_{H, TFA, FE}}}$$

Analysis of the whole feedback amplifier is: $\frac{R_{out}}{10.42}$
contin.

\Rightarrow in midband:

$$r_{in,f} = \frac{r_{in,TRA,FE}}{1 + \beta A_{TRA,FE}}$$

$$r_{out,f} = \frac{r_{out,TRA,FE}}{1 + \beta A_{TRA,FE}}$$

Where the ~~feedback~~ improvement factor is:

$$\begin{aligned} & 1 + \beta A_{TRA,FE} \\ &= 1 + \left(-\frac{1}{R_F}\right) \left(R_F (-g_{m1}) (R_D // R_F // r_{o1})\right) \\ &= 1 + g_{m1} [R_D // R_F // r_{o1}] \end{aligned}$$

Then

$$r_{in,f} = \frac{R_F}{1 + g_{m1} [R_D // R_F // r_{o1}]}$$

$$r_{out,f} = \frac{R_D // R_F // r_{o1}}{1 + g_{m1} [R_D // R_F // r_{o1}]}$$

Analysis of the frequency dependent gain. Rashed
10.42
contin.

$$A_f(j\omega) = \frac{A_{TRA, PE}(j\omega)}{1 + \beta(j\omega) A_{TRA, PE}(j\omega)}$$

$$= \frac{\frac{A_{TRA, PE}}{1 + \frac{j\omega}{\omega_{H, TRA, PE}}}}{1 + \frac{A_{TRA, PE}}{1 + \frac{j\omega}{\omega_{H, TRA, PE}}} \cdot \beta \left[1 + \frac{j\omega}{\omega_z} \right]}$$

$$= \frac{A_{TRA, PE}}{1 + \frac{j\omega}{\omega_{H, TRA, PE}} + A_{TRA, PE} \beta + \frac{j\omega}{\omega_z A_{TRA, PE} \beta}}$$

$$= \left(\frac{A_{TRA, PE}}{1 + A_{TRA, PE} \beta} \right) \frac{1}{1 + \frac{j\omega}{(1 + A_{TRA, PE} \beta) \left[\omega_{H, TRA, PE} \parallel \frac{\omega_z}{A_{TRA, PE} \beta} \right]}}$$

midband
value of
the gain
(as expected)

$$\omega_{H, f} = (1 + A_{TRA, PE} \beta) \left[\omega_{H, TRA, PE} \parallel \frac{\omega_z}{A_{TRA, PE} \beta} \right]$$

high-freq
cut-off
of the
feedback
ampli.

Scanned by CamScanner

5

Compute the voltage gain: (midband)

Rankin
10.42
contin.

$$\frac{v_o}{v_s} = \frac{v_o}{R_s \frac{v_s}{R_s}} = \frac{1}{R_s} \frac{v_o}{i_s}$$

$$= \frac{1}{R_s} A_f = \frac{1}{R_s} \frac{A_{TRA,PE}}{1 + A_{TRA,PE}\beta}$$

Numerical values:

improvement factor

$$1 + \beta A_{TRA,PE} = 1 + g_{m1} (R_D \parallel R_F \parallel r_{o1})$$

$$= 1 + (1.2 \text{ mS}) (2 \text{ k} \parallel 100 \text{ k} \parallel 25 \text{ k})$$

$$\approx 1 + (1.2 \text{ mS}) (2 \text{ k})$$

$$= 1 + 2.4 = 3.4$$

$$W_z = \frac{1}{C_F R_F} = \frac{1}{(10 \text{ nF})(100 \text{ k})} = \frac{1}{(10 \times 10^{-9})(100 \times 10^3)} = \frac{1}{10^3} = 10^3 \text{ rad/s}$$

$$\frac{W_z}{A_{TRA,PE}\beta} = \frac{10^3 \text{ rad/s}}{2.4} \approx 417 \text{ rad/s}$$

$$r_{in,f} = \frac{R_F}{\text{improvement factor}} = \frac{100 \text{ k}}{3.4} = 2.94 \times 10^4 \text{ k}$$

$$r_{out,f} \approx \frac{R_D}{\text{improvement factor}} = \frac{2 \text{ k}}{3.4} = 588 \Omega$$

$$W_{H,TRA,PE} \approx \frac{1}{(10 \text{ nF})(100 \text{ k} + 2 \text{ k})} = \frac{1}{10 \times 10^{-9} \times 102 \times 10^3} = 980 \text{ rad/s}$$

Scanned by CamScanner

6

Numerical values (contin.)

Proved
10.42
contin.

$$w_{H,f} \approx (3.4) \left[\underbrace{980 \text{ rad/s} \parallel 417 \text{ rad/s}}_{\approx 293 \text{ rad/s}} \right]$$

$$= 994 \text{ rad/s}$$

$$\beta = -\frac{1}{100k} = -\frac{10^6}{10^5} 10^{-6} = -10 \mu s$$


$$\begin{aligned} A_{TRA,PE} &\approx -(100k)(1.2ms)(2k) \\ &= -\underbrace{(200)(1.2)}_{240} \underbrace{(10^6)(10^{-3})}_{10^3} \\ &= -240k\Omega \end{aligned}$$

$$\begin{aligned} \frac{A_{TRA,PE}}{1 + \beta A_{TRA,PE}} &= \frac{-240k\Omega}{1 + 2.4} = \frac{-240k\Omega}{3.4} \\ &= -70.6 k\Omega \end{aligned}$$



Current-Shunt Feedback on a Current Amplifier**Rashid 10.50**

10.50 The MOS amplifier shown in Fig. P10.50 is biased to have the following small-signal MOS parameters: $g_{m1} = 1.2 \text{ mA/V}$, $r_{o1} = 25 \text{ k}\Omega$, $g_{m2} = 1.6 \text{ mA/V}$, and $r_{o2} = 25 \text{ k}\Omega$. If $R_D = 1.5 \text{ k}\Omega$, then $R_{SR1} = 500 \text{ k}\Omega$, $R_{SR2} = 2 \text{ k}\Omega$, and $R_F = 8 \text{ k}\Omega$. Determine (a) the voltage gain without feedback $A = i_o/v_s$, (b) the voltage gain with feedback A_f , and (c) the feedback capacitor C_F to limit the high frequency $f_H = 50 \text{ kHz}$.

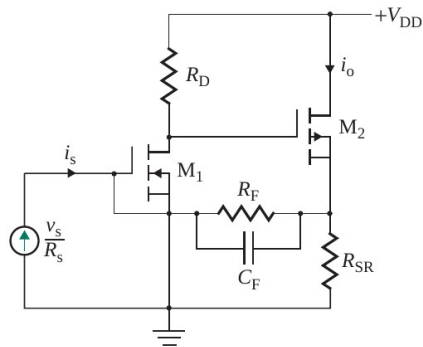FIGURE P10.50

Notes: None.


Additional Tasks: Point out and correct the two mistakes in the schematic before beginning to solve the question.

Necessary Knowledge and Skills: Current amplifiers, current-shunt feedback, identification and modeling of feedback networks, feedback-loaded amplifier analysis, gain and input/output impedance calculations, OCTC for approximating high-frequency cut-off, transfer functions and high-frequency cut-off and zero/pole approximations, design question.

Current amplifier with current shunt feedback


Rashid
10.50

Identify the feedback network

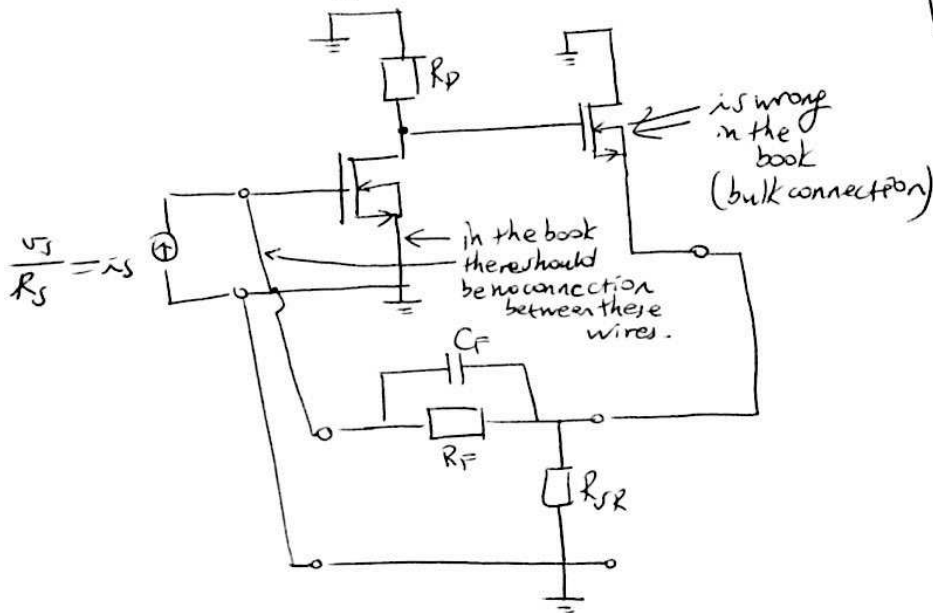

(*)
Current ampli
with current
shunt
feedback

Analyze the feedback network

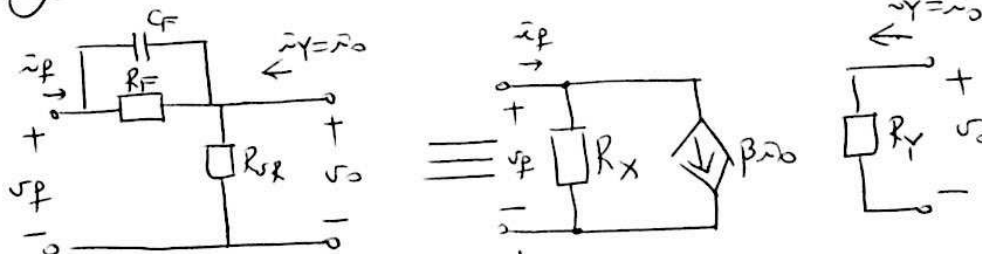

$$Z_X = \frac{v_f}{i_f} \Big|_{v_o=0} = R_F \parallel C_F$$

$$Z_Y = \frac{v_o}{i_o} \Big|_{v_f=0} = R_E \parallel R_F \parallel C_F$$

$$\beta = \frac{i_f}{i_o} \Big|_{v_f=0} = - \frac{R_E}{R_E + R_F \parallel \frac{1}{sC_F}}$$

Scanned by CamScanner

$$\beta(s) = - \frac{R_{SR}}{R_{SR} + \frac{R_F \frac{1}{sC_F}}{R_F + \frac{1}{sC_F}}}$$

Rashed
10.5
contin

$$= - \frac{R_{SR}}{R_{SR} + \frac{R_F}{1 + sC_F R_F}} = - \frac{R_{SR} (1 + sC_F R_F)}{R_{SR} + R_F + sC_F R_F R_{SR}}$$

$$= - \frac{R_{SR}}{R_{SR} + R_F} \frac{1 + sC_F R_F}{1 + \frac{s}{\frac{1}{C_F(R_F // R_{SR})}}}$$

$$= \left(- \frac{R_{SR}}{R_{SR} + R_F} \right) \frac{1 + \frac{s}{\frac{1}{C_F R_F}}}{1 + \frac{s}{\frac{1}{C_F(R_F // R_{SR})}}} \Rightarrow \text{call this } w_z$$

$\Rightarrow \text{call this } w_p$


call this β
(midband value)

$$= \beta \frac{1 + \frac{s}{w_z}}{1 + \frac{s}{w_p}}$$

—

CA, RL (feedback-loaded current amplifier)
and the feedback network

Rashed
10.50
contin.

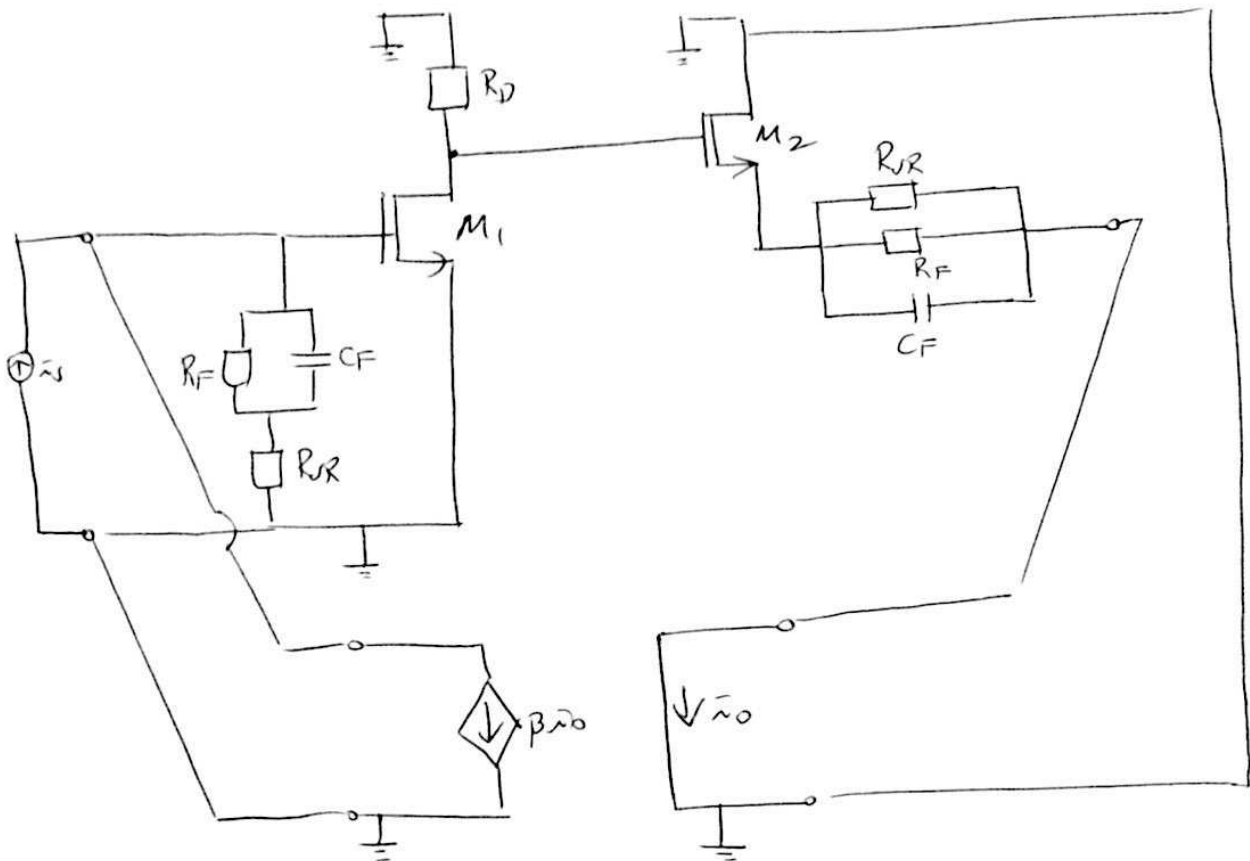

Analyze CA, RL (in midband)


$$r_{in, CA, RL} = R_F + R_{SR}$$

$$r_{out, CA, RL} \approx r_{o2} (1 + g_{m2} (R_{SR} \parallel R_F))$$

$$A_{CA, RL} \approx (-g_{m1} R_D) \left[\frac{g_{m2}}{1 + g_{m2} (R_{SR} \parallel R_F)} \right] (R_F + R_{SR})$$

Compute $\omega_{H,CA,pe}$ by OCTC

Rashed
10.50
contin-

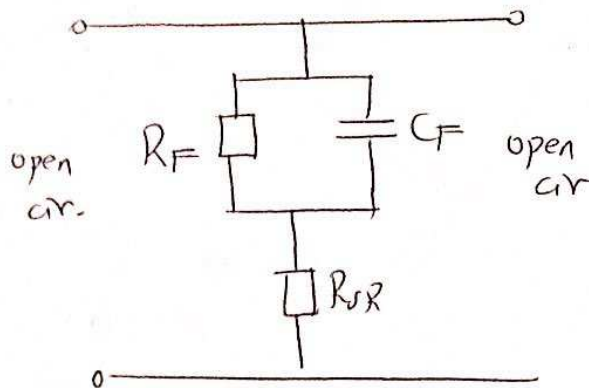


No current through R_{SR}

$$\tau_1 = R_1 C_1$$

$$C_1 = C_F$$

$$R_1 = R_F$$

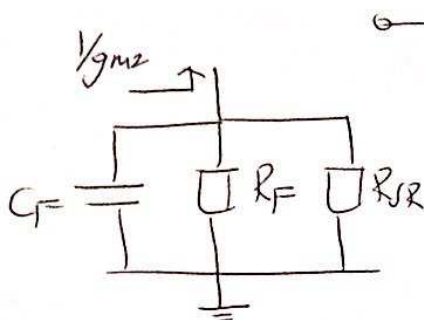

$$\tau_2 = R_2 C_2$$

$$C_2 = C_F$$

$$R_2 = R_F \parallel R_{SR} \parallel \frac{1}{g_{m2}}$$

in reality
 $\frac{r_{o2}}{1 + g_{m2} r_{o2}}$, but $g_{m2} r_{o2} \gg 1$

$$\omega_{H,CA,pe} \approx \frac{1}{\tau_1 + \tau_2}$$

Note that
the freq
response
of the gain is

$$A_{CA,pe}(j\omega) = \frac{A_{CA,pe}}{1 + \frac{j\omega}{\omega_{H,CA,pe}}}$$

Scanned by CamScanner

analysis the whole feedback amplifier

Rashid
10.50
contin.

$$r_{in,f} = \frac{r_{in,CA,FE}}{1 + \beta A_{CA,FE}}$$

$$r_{out,f} = r_{out,CA,FE} (1 + \beta A_{CA,FE})$$

Now analyze the gain with feedback:

$$A_f(j\omega) = \frac{A_{CA,FE}(j\omega)}{1 + \beta(j\omega)A_{CA,FE}(j\omega)}$$

$$= \frac{A_{CA,FE}}{1 + \frac{j\omega}{\omega_{H,CA,FE}}}$$

$$= \left(1 + \frac{A_{CA,FE}}{1 + \frac{j\omega}{\omega_{H,CA,FE}}} \beta \frac{1 + \frac{j\omega}{\omega_z}}{1 + \frac{j\omega}{\omega_p}} \right)$$

$$\approx \frac{A_{CA,FE} \left(1 + \frac{j\omega}{\omega_p} \right)}{1 + \frac{j\omega}{\omega_{H,CA,FE}} + \frac{j\omega}{\omega_p} + A_{CA,FE} \beta + \frac{j\omega}{\omega_z} \frac{1}{A_{CA,FE} \beta}}$$

$$= \frac{A_{CA,FE}}{1 + A_{CA,FE} \beta} \frac{1 + \frac{j\omega}{\omega_p}}{1 + \frac{j\omega}{(1 + A_{CA,FE} \beta) \left[\omega_{H,CA,FE} // \omega_p // \frac{\omega_z}{A_{CA,FE} \beta} \right]}}$$

Midband
values
expected.

Scanned by CamScanner 5

