



GTU

Electronics Engineering

ELEC 331

Electronic Circuits 2

Fall Semester

Instructor: Assist. Prof. Önder Şuvak

HW 6

Questions and Answers

Updated October 20, 2017 - 13:43

Assigned:

Due:

Answers Out:

Late Due:

Contents

Title Page	1
Contents	1
Question 1	2
Question	2
Solution	3
Question 2	8
Question	8
Solution	9
Question 3	11
Question	11
Solution	12
Question 4	14
Question	14
Solution	15
Question 5	17
Question	17
Solution	18


MOS Amplifier Frequency Response

Rashid 7.67

7.67 Design a common-source NMOS amplifier as shown in Fig. P7.67 to give a passband gain of $20 \leq |A_{PB}| \leq 30$, $Z_{in(mid)} \geq 100 \text{ k}\Omega$, a low 3-dB frequency of $f_L \leq 10 \text{ kHz}$, and a high 3-dB frequency of $f_H = 200 \text{ kHz}$.

D
P

FIGURE P7.67

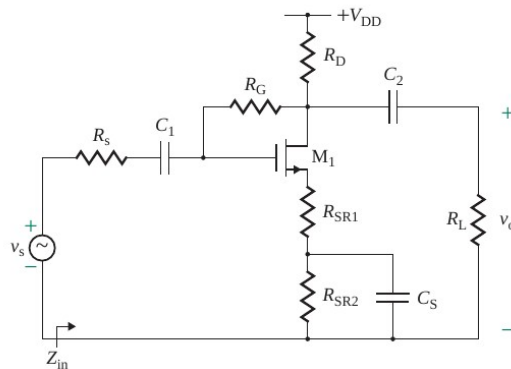

Notes: Carry out only the analysis part of this question and provide the answers in terms of the parameters.

Additional Tasks: Study voltage-shunt feedback and current-series feedback.


Necessary Knowledge and Skills: Trans-conductance amplifier analysis, trans-resistance amplifier analysis, voltage-shunt feedback, feedback network analysis, effect of feedback on frequency response, MOS small signal model, SCTC, OCTC, Miller effect.

Note: Solving this question via feedback concepts.
Alternative one can solve it through applying directly the usual techniques.


Rashid
7.67

→ W_L , W_H and midband gain are to be computed.

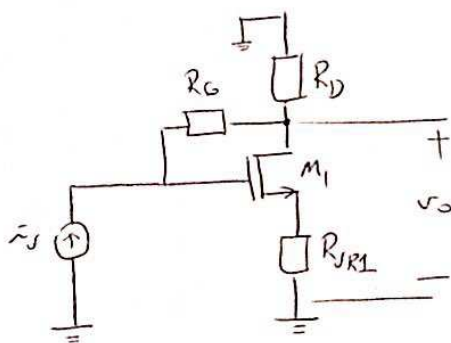Analyzed the following circuit in a separate document:
(see that document for the results in this soln, whose derivations have been omitted)




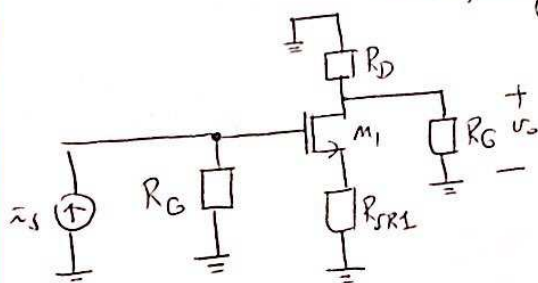The TRA, PL (feedback loaded TransResistance Amplifier) corresponding to the above circuit is:



⇒ Note that in this circuit the idealized feedback network is not shown.

(*)

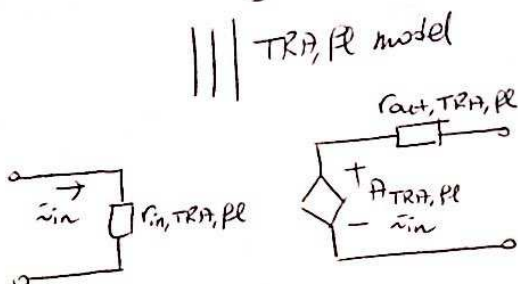

$$r_{in, TRA, PL} = R_G$$

$$r_{out, TRA, PL} = R_G \parallel R_D \parallel r_{out, TCA}$$

$$= R_G \parallel R_D \parallel r_{out, TCA}$$

(***)

$$A_{TRA, PL} = \frac{-g_m R_G}{1 + g_m R_S} \left[R_G \parallel R_D \parallel \left[r_{o1} (1 + g_{m1} R_{SR1}) \right] \right]$$

(see the ~~stated~~ document for derivations)

(1)

Scanned by CamScanner

Refer to (*)

$$\frac{v_{d1}}{v_{g1}} = \frac{-g_{m1}}{1 + g_{m1} R_{SR1}} \left[R_D // R_G // \left[r_{o1} (1 + g_{m1} R_{SR1}) \right] \right] \quad (1)$$

This will play a role in the computation of the Miller cap at $g1$.

if $R_{SR1} \gg \frac{1}{g_{m1}}$, we will, for convenience, not account for C_{gs} in the comput. for w_H .

Miller cap

$$C_{gd1,g1} = C_{gd1} \left(1 - \frac{v_{d1}}{v_{g1}} \right) \rightarrow \text{see (1)}$$

$$R_{Cgd1,g1} = R_G$$


$$\tau_{Cgd1,g1} = R_{Cgd1,g1} C_{gd1,g1}$$

$$w_H \approx \frac{1}{\tau_{Cgd1,g1}}$$

$$\beta = -\frac{1}{R_G} \text{ for the feedback network (6)}$$

see the other document for the derivation

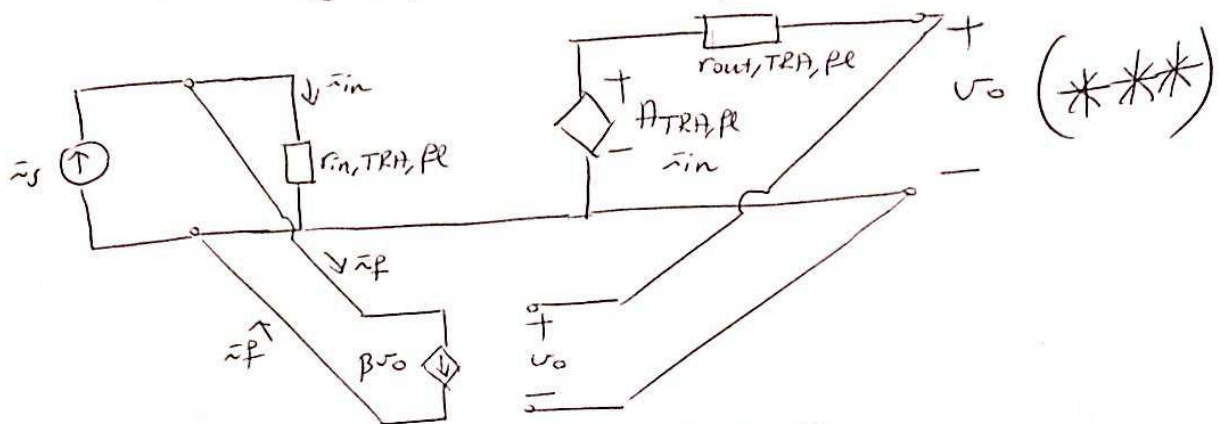We now have the following network:
(the feedback amplifier)



Note that $A_{TRA, PL} < 0$, $\beta < 0$

but the loop gain $A_{TRA, PL} \beta > 0$


so that the improvement factor $(1 + A_{TRA, PL} \beta) > 1$

See (**) and (***) and including what we know of negative feedback theory:

$$A_f = \frac{A_{TRA, PL}}{1 + \beta A_{TRA, PL}}$$

$$r_{in, f} = \frac{r_{in, TRA, PL}}{1 + \beta A_{TRA, PL}}$$

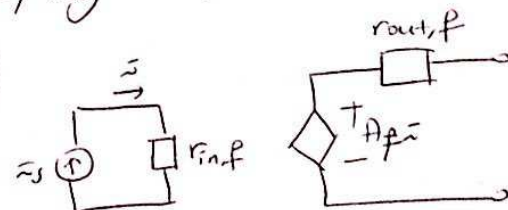
$$r_{out, f} = \frac{r_{out, TRA, PL}}{1 + \beta A_{TRA, PL}}$$



with $w_{H, f} = w_H (1 + A_{TRA, PL} \beta)$
given as in (5)

Scanned by CamScanner (3)

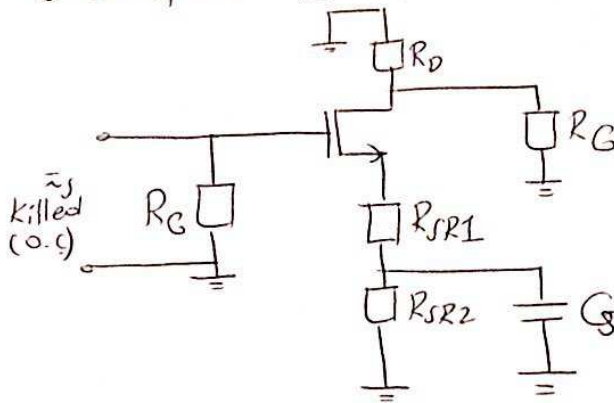Recall the relevant portion of the circuit
to compute w_L :



Rashed
7.67
cont.



$$R_{C_S} \text{ for } C_S \Rightarrow (\tau_{C_S} = R_{C_S} C_S) \quad (7)$$

$$R_{C_S} \cong R_{SR2} \parallel \left(R_{SR1} + \frac{1}{g_{m1}} \right) \quad (8)$$

$$\text{if } r_{o1} \gg R_D \parallel R_G$$

$$w_L \cong \frac{1}{\tau_{C_S}} \Rightarrow w_{L,f} = \frac{w_L}{1 + \beta A_{TRM,FE}} \quad (9)$$

Now analyze the whole circuit:

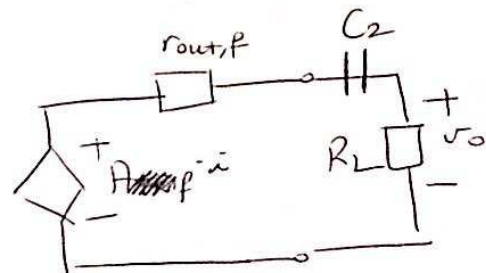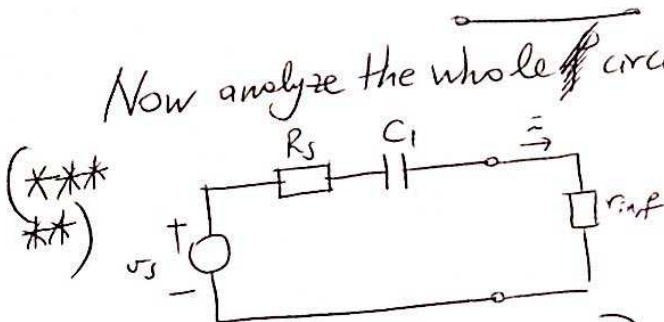

should now compute $\frac{v_o}{v_s}, w_{L,cir}, w_{H,cir}$ } $w_{H,cir} = w_{H,f} = w_H (1 + \beta A_{TRM,FE}) \quad (10)$

(4)

Scanned by CamScanner

$$\frac{v_o}{v_s} = ?$$

Rashed
7.67
cont.

$$i = \frac{v_s}{R_s + r_{in,f}}$$

$$v_o = A_f \cdot i \frac{R_L}{R_L + r_{out,f}}$$

$$v_o = A_f \frac{v_s}{R_s + r_{in,f}} \frac{R_L}{R_L + r_{out,f}}$$

$$\frac{v_o}{v_s} = \frac{A_f}{R_s + r_{in,f}} \frac{R_L}{R_L + r_{out,f}}$$

(11)
see (****)

Refer to (****).

We have new time constants to compute:

• R_{C1} for C_1 ($\tau_{C1} = R_{C1} \cdot C_1$)

$$R_{C1} = R_s + r_{in,f}$$

• R_{C2} for C_2 ($\tau_{C2} = R_{C2} \cdot C_2$)

$$R_{C2} = r_{out,f} + R_L$$

see (9). Using ~~the~~ STC again we have:


$$W_{L,cr} = \frac{1}{\tau_{cs}(1 + \beta A_{TRA,fe})} + \frac{1}{\tau_{C1}} + \frac{1}{\tau_{C2}}$$

Cascaded MOS Amplifier – SCTC and OCTC**Rashid 7.71**

7.71 A two-stage amplifier is shown in Fig. P7.71. The parameters are $R_s = 1 \text{ k}\Omega$, $R_{11} = 500 \text{ k}\Omega$, $R_{21} = 500 \text{ k}\Omega$, $R_{D1} = 10 \text{ k}\Omega$, $R_{12} = 500 \text{ k}\Omega$, $R_{22} = 500 \text{ k}\Omega$, $R_{D2} = 15 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $g_{m1} = 20 \text{ mA/V}$, $g_{m2} = 50 \text{ mA/V}$,

P

$C_1 = 1 \text{ }\mu\text{F}$, $C_2 = 1 \text{ }\mu\text{F}$, $C_3 = 10 \text{ }\mu\text{F}$, $C_{gd1} = C_{gd2} = 2 \text{ pF}$, and $C_{gs1} = C_{gs2} = 5 \text{ pF}$. Calculate the low 3-dB frequency f_L and the high cutoff frequency f_H .

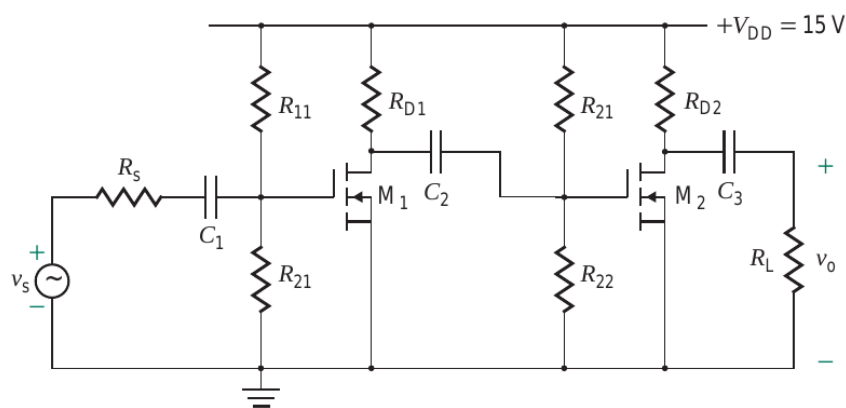FIGURE P7.71

Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: MOS small signal model, amplifier voltage gain computations, SCTC, OCTC, Miller's effect.

Quick answers for the analysisRashed 7-71 \Rightarrow SC TC

$$\cdot R_{C1} \text{ for } C_1 \Rightarrow (\tau_{C1} = R_{C1} C_1)$$

$$R_{C1} = R_S + R_{11} // R_{21}$$

$$\cdot R_{C2} \text{ for } C_2 \Rightarrow (\tau_{C2} = R_{C2} C_2)$$

$$R_{C2} = R_{D1} // r_{o1} + R_{21} // R_{22}$$

$$\cdot R_{C3} \text{ for } C_3 \Rightarrow (\tau_{C3} = R_{C3} C_3)$$

$$R_{C3} = R_L + R_{D2} // r_{o2}$$

$$\text{Then } w_L \approx \frac{1}{\tau_{C1}} + \frac{1}{\tau_{C2}} + \frac{1}{\tau_{C3}}$$

 \Rightarrow Midband gain

$$A_m = \frac{v_{g1}}{v_s} \frac{v_{d1}}{v_{g1}} \frac{v_{d2}}{v_{g2}} \Rightarrow \text{Note that } v_{d1} = v_{g2}$$

$$\begin{array}{ccc} \swarrow & \downarrow & \searrow \\ \frac{R_{11} // R_{21}}{R_{11} // R_{21} + R_S} & -g_{m1} (R_{D1} // R_{21} // R_{22} // r_{o1}) & -g_{m2} (R_{D2} // R_L // r_{o2}) \end{array}$$

\Rightarrow OCTC $\Rightarrow C_{gd1}$ and C_{gd2} will have time constants that are large enough to dominate the others

$C_{gd1,g1} \Rightarrow$ Miller cap at g_1

$$C_{gd1,g1} = C_{gd1} \left(1 - \frac{v_{d1}}{v_{g1}} \right) = C_{gd1} \left(1 + g_{m1} (R_{D1} // R_{21} // R_{22} // r_{o1}) \right)$$

$C_{gd2,g2} \Rightarrow$ Miller cap at g_2

$$C_{gd2,g2} = C_{gd2} \left(1 - \frac{v_{d2}}{v_{g2}} \right) = C_{gd2} \left(1 + g_{m2} (R_{D2} // R_L // r_{o2}) \right)$$

Scanned by CamScanner 1

Rashid
7-71
contin-

$$R_{C_{gd1},g1} = R_s // R_{i1} // R_{21}$$

$$R_{C_{gd2},g2} = R_{21} // R_{22} // R_{D1} // r_{o1}$$

$$\tau_{C_{gd1},g1} = R_{C_{gd1},g1} C_{gd1,g1}$$

$$\tau_{C_{gd2},g2} = R_{C_{gd2},g2} C_{gd2,g2}$$

$$W_H \approx \frac{1}{\tau_{C_{gd1},g1} + \tau_{C_{gd2},g2}}$$

CE Amplifier Frequency Response


Rashid 8.54

For Probs. 8.54–8.59 involving BJT amplifiers, use transistors whose parameters are $\beta_f = 100$, $C_{je} = 8$ pF at $V_{BE} = 0.5$ V, $C_{\mu} = 4$ pF at $V_{CB} = 5$ V, $C_{cs} = 4$ pF at $V_{CS} = 8$ V, $\beta_f = 100$, $V_{je} = V_{jc} = V_{js} = 0.8$ V, and $h_{oe} = 1/r_o = 5$ μS at $V_{CE} = 10$ V. The transition frequency is $f_T = 300$ MHz at $V_{CE} = 20$ V, $I_C = 10$ mA. The substrate is connected to the ground. Assume $I_C = 5$ mA (unless specified), $V_{CC} = 15$ V, $V_{BE} = 0.7$ V, $R_s = 1$ k Ω , and $R_L = 10$ k Ω . Use PSpice/SPICE to check your design by plotting the frequency response and give an approximate cost estimate.

- 8.54** Design a CE amplifier as shown in Fig. P8.54 to give a passband gain of $40 \leq |A_{PB}| \leq 50$, a low 3-dB frequency of $f_L \leq 1$ kHz, and a high 3-dB frequency of $f_H = 50$ kHz.

D
P

FIGURE P8.54

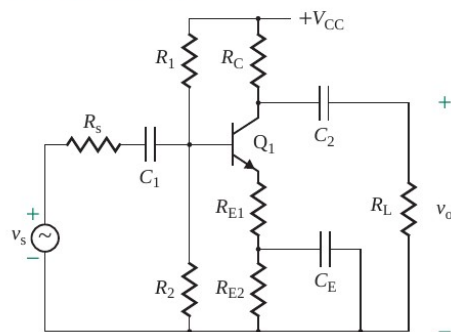

Notes: Analyze the circuit to compute its high and low frequency response. State your answers in terms of the parameters.

Additional Tasks: None.

Necessary Knowledge and Skills: BJT small signal model, Miller effects, OCTC, SCTC.

Quick answers for the analysis

Rashid
8.54

\Rightarrow Midband gain

$$A_m = \frac{v_o}{v_s}$$

$$\approx \frac{R_1 // R_2 // R_{in,b1}}{R_1 // R_2 // R_{in,b1} + R_s} \left[\frac{-g_{m1}}{1 + g_{m1} R_{E1}} \right] \left[\frac{(R_C // R_L) // [r_{o1}(1 + g_{m1} R_{E1})]}{[r_{o1}(1 + g_{m1} R_{E1})]} \right]$$

where $R_{in,b1} \approx r_{\pi 1} [1 + g_{m1} R_{E1}]$ (*)

\Rightarrow SCTC $\Rightarrow \omega_L \approx \frac{1}{\tau_{c1}} + \frac{1}{\tau_{c2}} + \frac{1}{\tau_{CE}}$

• R_{c1} for C_1 ($\tau_{c1} = R_{c1} \cdot C_1$)

$$R_{c1} \approx R_s + R_1 // R_2 // R_{in,b1}$$

where $R_{in,b1}$ is as above in (*)

• R_{CE} for C_E ($\tau_{CE} = R_{CE} C_E$)

$$R_{CE} \approx R_{E2} // \left[R_{E1} + \frac{r_{\pi 1} + R_s // R_1 // R_2}{1 + \beta_1} \right]$$

• R_{c2} for C_2 ($\tau_{c2} = R_{c2} C_2$)

$$R_{c2} = R_L + R_C // R_{in,c1}$$

where $R_{in,c1} \approx r_{o1} (1 + g_{m1} R_{E1})$

assuming $R_s \ll R_1 // R_2$
and $R_s \ll r_{\pi 1}$

Scanned by CamScanner ①

\Rightarrow OCTC

account for only C_M (Miller effect component at $b1$)

Rashid
8.54
Cont'n

$$C_{M,b1} = C_M \left[1 + \frac{g_{m1}}{1 + g_{m1} R_{E1}} (R_C // R_L // [r_{o1} (1 + g_{m1} R_{E1})]) \right]$$

$$R_{C_{M,b1}} \approx R_1 // R_2 // R_S // \underbrace{R_{in,b1}}_{\text{as in (*)}}$$

$$\rightarrow W_H \approx \frac{1}{R_{C_{M,b1}} C_{M,b1}}$$

CB Amplifier Frequency Response


Rashid 8.55

For Probs. 8.54–8.59 involving BJT amplifiers, use transistors whose parameters are $\beta_F = 100$, $C_{je} = 8$ pF at $V_{BE} = 0.5$ V, $C_{\mu} = 4$ pF at $V_{CB} = 5$ V, $C_{cs} = 4$ pF at $V_{CS} = 8$ V, $\beta_F = 100$, $V_{je} = V_{jc} = V_{js} = 0.8$ V, and $h_{oe} = 1/r_o = 5 \mu\text{S}$ at $V_{CE} = 10$ V. The transition frequency is $f_T = 300$ MHz at $V_{CE} = 20$ V, $I_C = 10$ mA. The substrate is connected to the ground. Assume $I_C = 5$ mA (unless specified), $V_{CC} = 15$ V, $V_{BE} = 0.7$ V, $R_s = 1$ k Ω , and $R_L = 10$ k Ω . Use PSpice/SPICE to check your design by plotting the frequency response and give an approximate cost estimate.

8.55 Design a CB amplifier as shown in Fig. P8.55 to give a passband gain of $20 \leq |A_{PB}| \leq 30$, a low 3-dB frequency of $f_L \leq 1$ kHz, and a high 3-dB frequency of $f_H = 100$ kHz. Assume $R_s = 15$ k Ω and $R_L = 10$ k Ω .

D
P

FIGURE P8.55

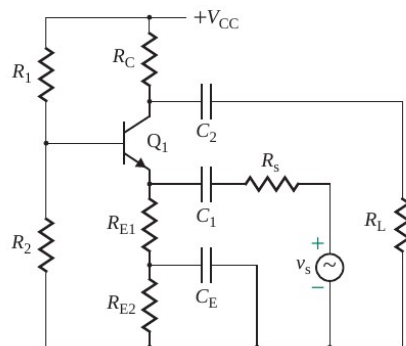

Notes: Analyze the circuit to compute its high and low frequency response. State your answers in terms of the parameters.

Additional Tasks: None.

Necessary Knowledge and Skills: BJT small signal model, Miller effects, OCTC, SCTC.

Quick answers for the analysis of freq response

Rashid
8.55

I am assuming that B (base of the BJT)
is gnd-ed ~~via~~ via a large cap. C_B .

\Rightarrow SCTC method (all cap except the chosen one
are short cir)

- R_{CE} corresponding to C_E to be computed $\Rightarrow \tau_{CE} = R_{CE} C_E$

$$R_{CE} \approx R_{E2} // \left[R_{E1} + R_S // \frac{1}{g_{m1}} \right]$$

- R_{C1} corresponding to C_1 to be computed $\Rightarrow \tau_{C1} = R_{C1} C_1$

$$R_{C1} \approx R_S + R_{E1} // \frac{1}{g_{m1}}$$

- R_{C2} corresponding to C_2 to be computed $\Rightarrow \tau_{C2} = R_{C2} C_2$

$$R_{C2} \approx R_L + R_C // \left[r_{o1} (1 + g_{m1} R_{E1}) \right]$$

- R_{CB} corresponding to C_B to be computed $\Rightarrow \tau_{CB} = R_{CB} C_B$

$$R_{CB} \approx R_1 // R_2 // \left[r_{\pi 1} (1 + g_{m1} R_{E1}) \right]$$

$$\rightarrow W_L \approx \frac{1}{\tau_{CE}} + \frac{1}{\tau_{C1}} + \frac{1}{\tau_{C2}} + \frac{1}{\tau_{CB}}$$

⇒ Midband gain (all coupling or bypass caps are shorted)

$$\frac{R_{avhd}}{8.55}$$

cont.

$$A_M = \frac{v_o}{v_s}$$

$$\approx \frac{R_{E1} // \frac{1}{g_{m1}}}{R_{E1} // \frac{1}{g_{m1}} + R_s} g_{m1} (R_C // R_L)$$

⇒ There is no Miller effect, C_π and C_μ have one node gnd-ed if we assume C_B is between B and gnd.

⇒ OCTC method (all cap except the chosen one are open cir.) But big coupling cap are already short cir.)

• R_{C_μ} for C_μ ($\tau_{C_\mu} = R_{C_\mu} C_\mu$)

$$R_{C_\mu} \approx R_C // R_L // [r_{o1} (1 + g_{m1} R_{E1})]$$

• R_{C_π} for C_π ($\tau_{C_\pi} = R_{C_\pi} C_\pi$)

$$R_{C_\pi} \approx R_{E1} // R_s // \frac{1}{g_{m1}}$$

$$\rightarrow W_H \approx \frac{1}{\tau_{C_\mu} + \tau_{C_\pi}}$$

Cascaded Amplifier Frequency Response


Rashid 8.58

For Probs. 8.54–8.59 involving BJT amplifiers, use transistors whose parameters are $\beta_f = 100$, $C_{je} = 8$ pF at $V_{BE} = 0.5$ V, $C_{\mu} = 4$ pF at $V_{CB} = 5$ V, $C_{cs} = 4$ pF at $V_{CS} = 8$ V, $\beta_f = 100$, $V_{je} = V_{jc} = V_{js} = 0.8$ V, and $h_{oe} = 1/r_o = 5 \mu\text{S}$ at $V_{CE} = 10$ V. The transition frequency is $f_T = 300$ MHz at $V_{CE} = 20$ V, $I_C = 10$ mA. The substrate is connected to the ground. Assume $I_C = 5$ mA (unless specified), $V_{CC} = 15$ V, $V_{BE} = 0.7$ V, $R_s = 1$ k Ω , and $R_L = 10$ k Ω . Use PSpice/SPICE to check your design by plotting the frequency response and give an approximate cost estimate.

- 8.58** Design a CE-CC amplifier as shown in Fig. P8.58 to give a passband gain of $20 \leq |A_{PB}| \leq 30$, $Z_{i1(\text{mid})} \leq 100 \Omega$, a low 3-dB frequency of $f_L \leq 1$ kHz, and a high 3-dB frequency of $f_H = 100$ kHz.



FIGURE P8.58

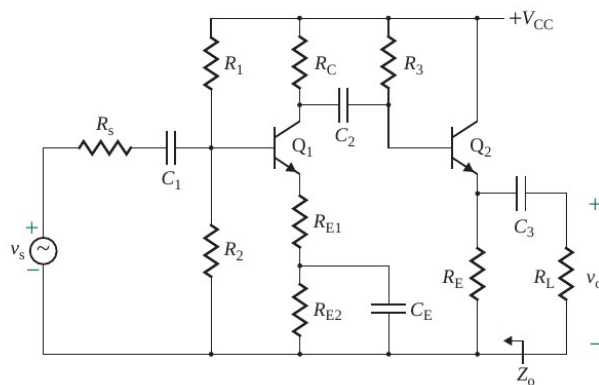

Notes: Analyze the circuit to compute its high and low frequency response. State your answers in terms of the parameters.


Additional Tasks: None.

Necessary Knowledge and Skills: BJT small signal model, Miller effects, OCTC, SCTC.

SCTC for computing ω_L
(low freq cutoff)

Rashid
8.58

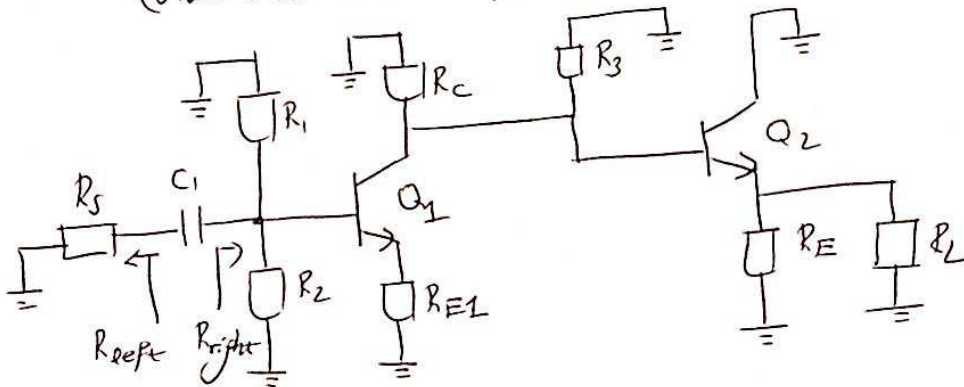\Rightarrow Compute R_{C1} corresponding to C_1
(short or other cap, kill indep sources in s.s.)




$$R_{C1} = R_{\text{left}} + R_{\text{right}}$$

$$R_{\text{left}} = R_s$$

$$R_{\text{right}} \approx R_1 \parallel R_2 \parallel \left[(1 + g_{m1} R_{E1}) r_{\pi 1} \right]$$

$$\tau_{C1} = R_{C1} C_1$$

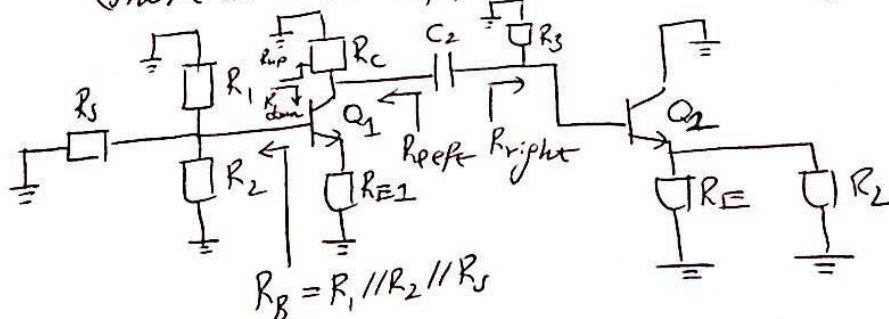\Rightarrow Compute R_{C2} corresponding to C_2
(short or other cap, kill indep sources in s.s.)



$$R_B = R_1 \parallel R_2 \parallel R_s$$

Scanned by CamScanner

SCTC continued $\Rightarrow R_{C2} = R_{\text{left}} + R_{\text{right}}$ $\frac{R_{\text{achd}}}{8.58}$

$$R_{\text{right}} = R_3 \parallel \left[(1 + g_{m2} (R_E \parallel R_L)) r_{\pi 2} \right]$$

$$R_{\text{left}} = R_{\text{up}} \parallel R_{\text{down}}$$

$$R_{\text{up}} = R_C$$


$$R_{\text{down}} = r_{o1} \left[1 + \frac{g_{m1} R_{E1} r_{\pi 1}}{R_{E1} + r_{\pi 1} + R_B} \right] + R_{E1} \parallel (r_{\pi 1} + R_B)$$

(see the derivation elsewhere, in a separate document)

R_B defined on the prev page.

$$\tau_{C2} = R_{C2} C_2$$

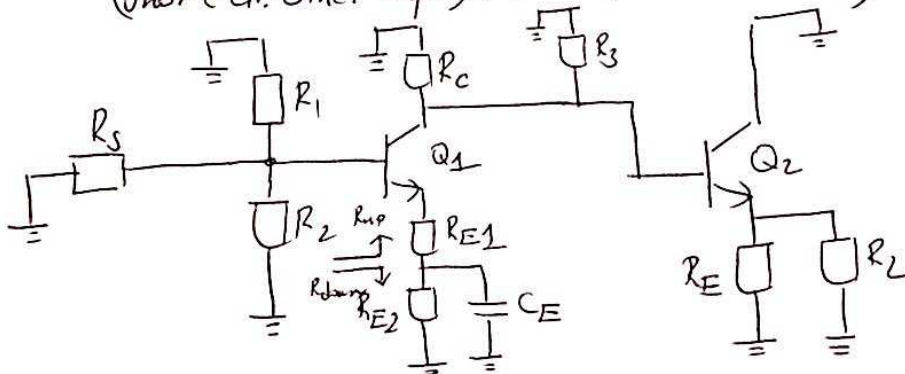\Rightarrow compute R_{CE} corresponding to C_E
(short wr. other cap., kill indep. sources in c.s.)



$$R_{CE} = R_{\text{up}} \parallel R_{\text{down}}$$

$$R_{\text{down}} = R_{E2} \quad \frac{r_{\pi 1} + R_1 \parallel R_2 \parallel R_S}{1 + \beta_1} \quad \left(\text{see related derivations} \right)$$


$$R_{\text{up}} = R_{E1} +$$

$$\tau_{CE} = R_{CE} C_E$$

Scanned by CamScanner

SETC continuedRashid
8-58

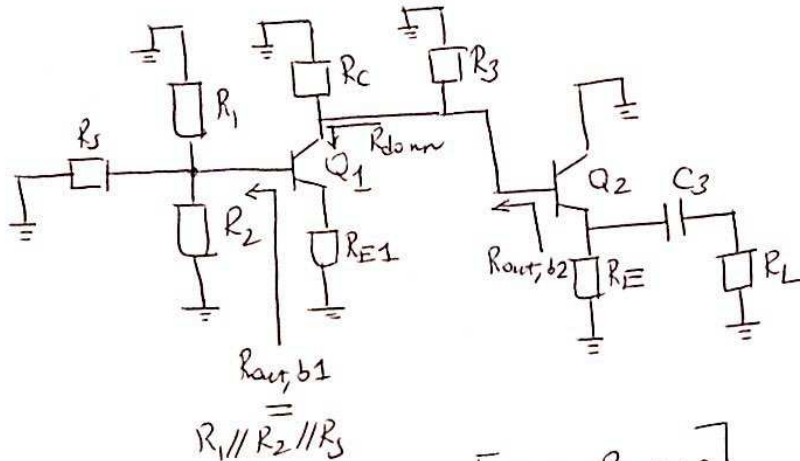⇒ Compute R_{C3} corresponding to C_3 :
(short other cap, kill indep sources in ss.)



$$R_{C3} = R_L + R_E \parallel \left[\frac{r_{\pi 2} + R_{out,b2}}{1 + \beta_2} \right]$$

$$R_{down} = R_3 \parallel R_C \parallel R_{down}$$

$$R_{down} = r_{o1} \left[1 + \frac{g_{m1} R_{E1} r_{\pi 1}}{R_{E1} + r_{\pi 1} + R_{out,b1}} \right] + R_{E1} \parallel (r_{\pi 1} + R_{out,b1})$$

(see related derivations in separate documents)


$$\tau_{C3} = R_{C3} C_3$$

$$W_L \approx \frac{1}{\tau_{C1}} + \frac{1}{\tau_{C2}} + \frac{1}{\tau_{C3}} + \frac{1}{\tau_{CE}}$$

- ⇒ High Freq ^{voltage} W_H approx will follow
- Gain computations
 - Miller's effects accounted for
 - OCTC applied

$$\frac{R_{shd}}{8.58}$$

Gain computations

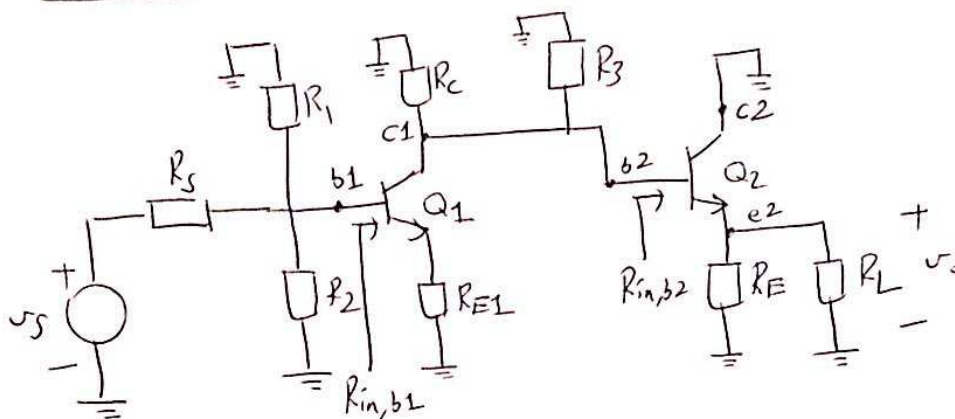

$$\frac{v_o}{v_s} = \frac{v_{b1}}{v_s} \cdot \frac{v_{c1}}{v_{b1}} \cdot \frac{v_{e2}}{v_{c1}}$$

$$\frac{v_{b1}}{v_s} = \frac{R_{in,b1} \parallel R_1 \parallel R_2}{R_{in,b1} \parallel R_1 \parallel R_2 + R_s}$$

$$\frac{v_{c1}}{v_{b1}} \approx \left[- \frac{g_{m1}}{1 + g_{m1} R_{E1}} \right] [R_C \parallel R_3 \parallel R_{in,b2}]$$



$$\frac{v_{e2}}{v_{c2}} \approx \frac{R_E \parallel R_L}{R_E \parallel R_L + \frac{1}{g_{m2}}}$$

Note that, above

$$R_{in,b1} \approx r_{\pi 1} (1 + g_{m1} R_{E1})$$

$$R_{in,b2} \approx r_{\pi 2} (1 + g_{m2} (R_E \parallel R_L))$$

Scanned by CamScanner (4)

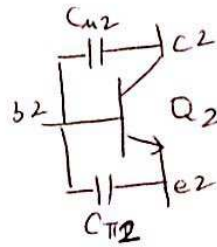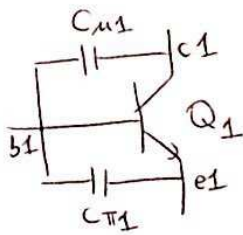Miller's effectsRashid
8-58

$C_{\mu 1}$: Miller's effect applies.
Converted to grounded cap. at b1
 $C_{\mu 1, b1} = \left(1 - \frac{v_{c1}}{v_{b1}}\right) C_{\mu 1}$

Also converted to
 $C_{\mu 1, c1} = \left(1 - \frac{v_{b1}}{v_{c1}}\right) C_{\mu 1} \leftarrow \text{small cap, do not account for this one}$

$C_{\pi 1}$: Provided that $R_{E1} \gg \frac{1}{g_{m1}}$ ($\frac{v_{e1}}{v_{b1}}$ will be very close to 1)
Miller's effect renders this capacitor ineffective
(see related lecture notes)

$C_{\pi 2}$: the same conclusion as for $C_{\pi 1}$
provided that $R_E \parallel R_L \gg \frac{1}{g_{m2}}$ ($\frac{v_{e2}}{v_{b2}}$ will be very close to 1)

$C_{\mu 2}$: one node is grounded \Rightarrow no Miller effect
 $C_{\mu 2, b2} = C_{\mu 2} \leftarrow \text{small cap, do not account for this}$



OCTCRashed
8-58

\Rightarrow There is only one time constant that is big enough to dominate the others.

$$W_H \approx \frac{1}{\tau_{C_{u1,b1}}} = \frac{1}{R_{C_{u1,b1}} C_{u1,b1}}$$

$R_{C_{u1,b1}}$ needs to be computed

$$R_{C_{u1,b1}} = R_S // R_1 // R_2 // R_{in,b1}$$

where $R_{in,b1} \approx r_{\pi 1} (1 + \beta_{u1} R_{E1})$

—————

