



GTU
Electronics Engineering

ELEC 331
Electronic Circuits 2

Fall Semester

Instructor: Assist. Prof. Önder Şuvak

HW 3
Questions and Answers

Updated October 20, 2017 - 13:39

Assigned:

Due:

Answers Out:

Late Due:

Contents


Title Page	1
Contents	1
Question 1	2
Question	2
Solution	3
Question 2	7
Question	7
Solution	8
Question 3	14
Question	14
Solution	15
Question 4	21
Question	21
Solution	22
Question 5	24
Question	24
Solution	25
Question 6	29
Question	29
Solution	30

CMOS Differential Amplifier with Active Load

Rashid 9.14

9.14 A CMOS amplifier is shown in Fig. P9.14. The parameters for the NMOS are $V_t = +2$ V, $V_M = -40$ V, and $V_{GS} = +4$ V at $I_D = 1$ mA; the parameters for the PMOS are $V_t = -3$ V, $V_M = 40$ V, and $V_{GS} = -6$ V at $I_D = 1$ mA. Calculate (a) A_d , A_c , and CMRR and (b) R_{id} and R_{ic} .

FIGURE P9.14

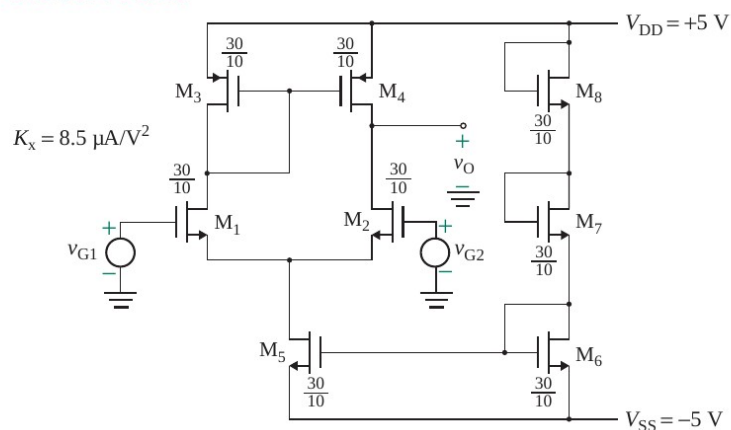

Necessary Knowledge and Skills: MOS differential amplifier, MOS active load, MOS current source, MOS nonlinear resistors (diode connected MOS), DC bias, voltage gain computation with active load, single ended amplifier with voltage gain the same as that of the fully differential amplifier, MOS small signal equivalent model, output impedance calculations.

DC biasing of the current sourceRevised
9.14

Since all of M_6 , M_7 and M_8 are identical, we will have

$$\begin{aligned} V_{GS6} &= V_{DS6} \\ &= V_{GS7} = V_{DS7} \\ &= V_{GS8} = V_{DS8} = \frac{V_{DD} - V_{SS}}{3} = \frac{10}{3} = 3.33 \text{ Volts} \end{aligned}$$

All are in satur, because of the diode connection.

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 = I_D \Rightarrow \text{compute}$$

$\underbrace{\mu_n C_{ox}}_{8.5 \mu A/V^2} \quad \underbrace{V_{GS} - V_t}_{V_{DS} = 3.33V} \quad \underbrace{V_{DS}}_{2V}$

$\frac{30}{10}$

the tail current $I_{tail} = I_D$


$$I_{tail} \quad \downarrow \quad r_{tail} = \frac{V_m}{I_D} = r_{o5} \quad \left(\begin{array}{l} \text{size} \\ \text{is the} \\ \text{same} \end{array} \right)$$

\downarrow compute

At the differential stage, we have an active loaded single ended diff amp. analysis is different \Rightarrow because it is asymmetrical.

Differential mode

Prashant
9.14
Continued

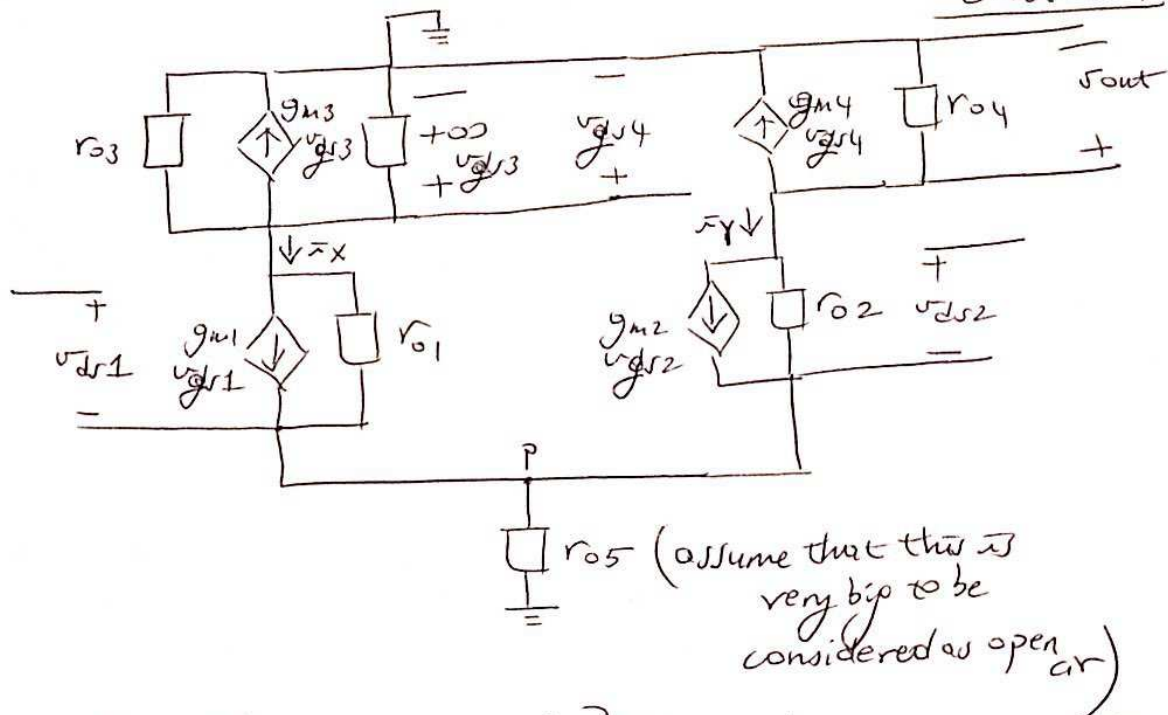

PMOS devices are identical } All carry the same DC current = $\frac{I_{tail}}{2}$
 NMOS " " " }

Therefore $g_{m3} = g_{m4} = g_{mP}$ $r_{o3} = r_{o4} = r_{oP}$
 $g_{m1} = g_{m2} = g_{mN}$ $r_{o1} = r_{o2} = r_{oN}$

denote $V_A = v_{gs3} = v_{gs4}$

$v_{ds1} = v_1$

$v_{ds2} = v_2$

Note that $\bar{v}_x + \bar{v}_y = 0$

Prashad
9.14
Continued

$$v_A = -\bar{v}_X \left(\frac{1}{g_{mp}} \parallel r_{op} \right)$$

$$\bar{v}_Y + g_{mp} \bar{v}_A + \frac{v_{out}}{r_{op}} = 0$$

\Downarrow
 substitute

—————

$$-\bar{v}_Y = \frac{v_{out}}{r_{op}} - g_{mp} \bar{v}_X \left(\frac{1}{g_{mp}} \parallel r_{op} \right)$$

$$= \bar{v}_X$$

$$\text{Then } \bar{v}_X = \frac{v_{out}}{r_{op} \left[1 + g_{mp} \left(\frac{1}{g_{mp}} \parallel r_{op} \right) \right]}$$

—————

$$(KVL) -v_A + (\bar{v}_X - g_{mN} v_1) r_{oN} - (\bar{v}_Y - g_{mN} v_2) r_{oN} + v_{out} = 0$$

Note that $v_{in,1} \neq v_1$

$v_{in,2} \neq v_2$

But $v_1 - v_2 = v_{in,1} - v_{in,2}$

and $\bar{v}_X = -\bar{v}_Y$

$$\text{then } -v_A + 2\bar{v}_X r_{oN} - g_{mN} r_{oN} (v_{in,1} - v_{in,2}) + v_{out} = 0$$

Substitute v_A and \bar{v}_X

Rashed
9.14
continued

$$\frac{v_{out}}{r_{op} \left[1 + g_{mP} \left(\frac{1}{g_{mP}} \parallel r_{op} \right) \right]} \left(\frac{1}{g_{mP}} \parallel r_{op} \right)$$

$$+ 2r_{oN} \frac{v_{out}}{r_{op} \left[1 + g_{mP} \left(\frac{1}{g_{mP}} \parallel r_{op} \right) \right]} + v_{act} = g_{mN} r_{oN} (v_{in1} - v_{in2})$$

≈ 1 since $\frac{1}{g_{mP}} \ll r_{op}$

$$v_{out} \left[\frac{\cancel{g_{mP}} + 2r_{oN} + 2r_{op}}{r_{op} \left[1 + g_{mP} \left(\frac{1}{g_{mP}} \parallel r_{op} \right) \right]} \right] = g_{mN} r_{oN} (v_{in1} - v_{in2})$$

neglected

$$\frac{v_{out}}{v_{in1} - v_{in2}} = g_{mN} r_{oN} \frac{r_{op} \left[1 + g_{mP} \left(\frac{1}{g_{mP}} \parallel r_{op} \right) \right]}{2r_{oN} + 2r_{op}}$$

$$\approx g_{mN} r_{oN} \frac{2r_{op}}{2r_{oN} + 2r_{op}}$$

$$= g_{mN} \frac{r_{oN} r_{op}}{r_{oN} + r_{op}} = g_{mN} (r_{oN} \parallel r_{op})$$

The circuit is single ended but the gain is approximately equal to that of the fully differential one.


see pp 512-514 of Razavi

Generated by CamScanner

(4)

BJT Differential Amplifier with Active Load**Rashid 9.42**

- 9.42** A differential amplifier is shown in Fig. P9.42. The transistors are identical. Assume $V_{BE} = 0.7$ V, $V_T = 26$ mV, $\beta_{F(\text{nnpn})} = 100$, $\beta_{F(\text{pnp})} = 50$, $V_A = 40$ V, and $V_{CC} = 10$ V. Calculate the values of R_1 , R_2 , A_d , R_{id} , A_c , R_{ic} , and CMRR.

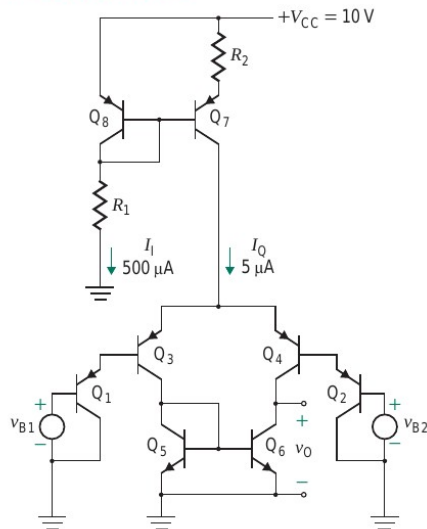
FIGURE P9.42

Necessary Knowledge and Skills: BJT input stages for BJT differential amplifier (for higher input impedance), BJT differential amplifier with current mirror active load, Widlar current source for tail current, single ended amplifier with the same gain as that of the fully differential amplifier, small signal equivalent model for BJT, voltage gain computations, input/output impedance computations.

Analysis and Design of the circuit

Rashid
9.42

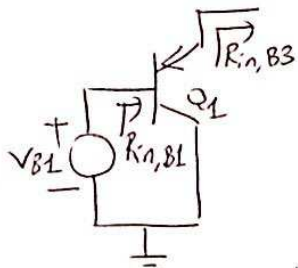- Design of the tail current source
- Output impedances of the tail current source needs to be computed
- Calculation of the impedances (small signal)



and similarly $R_{in,B4}$

$$\Rightarrow \text{Note } R_{in,B1} \approx (1 + g_{m1} R_{in,B3}) r_{\pi 1}$$

$$\text{and } R_{in,B2} \approx (1 + g_{m2} R_{in,B4}) r_{\pi 2}$$

(the purpose here is to have larger input impedance)

\Rightarrow Note here that

$$v_{B3} = v_{B1} \frac{R_{in,B3}}{R_{in,B3} + \frac{1}{g_{m1}}}$$

$$v_{B4} = v_{B2} \frac{R_{in,B4}}{R_{in,B4} + \frac{1}{g_{m2}}}$$

(Remember the gain of emitter follower stages)

$\Rightarrow R_{in,B3}$ and $R_{in,B4}$ are going to be large, $\frac{1}{g_{m1}}$ and $\frac{1}{g_{m2}}$ are small

then $v_{B3} \approx v_{B1}$ and $v_{B4} \approx v_{B2}$

→ calculation of the differential mode gain (small signal)

→ " " " " common " " (" ")


→ Compute CMRR

Above are the tasks that need to be completed in this question.

Simplified model of the differential stage
in small signal

Rankin
9.42

Cont-

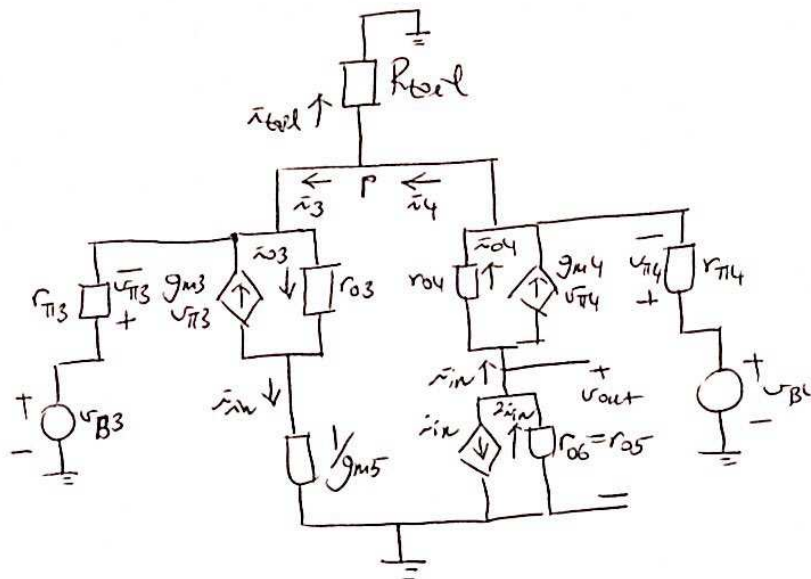

$$v_{out} = -2\tilde{v}_{in}r_{o5}$$

$$\tilde{v}_4 = \tilde{v}_3 + \tilde{v}_{tail}$$

$$v_p = \tilde{v}_{tail} - R_{tail} = (\tilde{v}_4 - \tilde{v}_3) R_{tail}$$

$$-\tilde{v}_3 + \tilde{v}_{o3} - g_{m3}v_{\pi3} + \frac{(\tilde{v}_4 - \tilde{v}_3)R_{tail} - v_{B3}}{r_{\pi3}} = 0$$

$$v_{\pi3} = v_{B3} - (\tilde{v}_4 - \tilde{v}_3)R_{tail}$$

$$\tilde{v}_{in} + g_{m3}v_{\pi3} - \tilde{v}_{o3} = 0$$

$$-\tilde{v}_{in} + \tilde{v}_{o4} + g_{m4}v_{\pi4} = 0$$

$$\tilde{v}_4 - \tilde{v}_{o4} - g_{m4}v_{\pi4} + \frac{(\tilde{v}_4 - \tilde{v}_3)R_{tail} - v_{B4}}{r_{\pi4}} = 0$$

$$v_{\pi4} = v_{B4} - (\tilde{v}_4 - \tilde{v}_3)R_{tail}$$

$$v_{B3} - v_{\pi3} = v_{B4} - v_{\pi4} \Rightarrow v_{B3} - v_{B4} = v_{\pi3} - v_{\pi4}$$

$$(KVL) \quad \tilde{v}_{o3}r_{o3} + \tilde{v}_{in}\frac{1}{g_{m5}} + 2\tilde{v}_{in}r_{o5} + \tilde{v}_{o4}r_{o4} = 0$$

$$\Downarrow \qquad \qquad \qquad \Downarrow$$

$$(\tilde{v}_{in} + g_{m3}v_{\pi3}) \qquad \qquad \qquad (\tilde{v}_{in} - g_{m4}v_{\pi4})$$

Generated by CamScanner

Continue from the KVL

$$r_{o3} = r_{o4}$$

$$g_{m3} = g_{m4}$$

$$(\tilde{v}_{in} + g_{m3} v_{\pi 3}) r_{o3} + \tilde{v}_{in} \frac{1}{g_{m5}} + 2 \tilde{v}_{in} r_{o5} + (\tilde{v}_{in} - g_{m3} v_{\pi 3}) r_{o5} = 0$$

$$2 \tilde{v}_{in} r_{o5} + 2 \tilde{v}_{in} r_{o3} + \tilde{v}_{in} \frac{1}{g_{m5}} + g_{m3} r_{o3} (v_{\pi 3} - v_{\pi 4}) = 0$$

$$2 \tilde{v}_{in} [\cancel{r_{o5}} + \cancel{r_{o3}}] + g_{m3} r_{o3} (v_{B3} - v_{B4}) = 0$$

$$\underbrace{[-2 \tilde{v}_{in} r_{o5}]}_{v_{out}} \left[\frac{-(r_{o5} + r_{o3})}{r_{o5}} \right] = -g_{m3} r_{o3} (v_{B3} - v_{B4}) = 0$$

$$\frac{v_{out}}{v_{B3} - v_{B4}} = g_{m3} \frac{r_{o3} r_{o5}}{r_{o5} + r_{o3}}$$


$$\begin{aligned} \text{Differential mode gain} &= g_{m3} (r_{o3} \parallel r_{o5}) \\ \text{Common mode gain} &\Rightarrow \left[v_{B3} = v_{B4} \Rightarrow v_{out} = 0 \right] \end{aligned}$$

CMRR in this approx $\rightarrow +\infty$.

Pushed
9.42
cont.

Design of the tail current source

Harshit
9.42
cont-

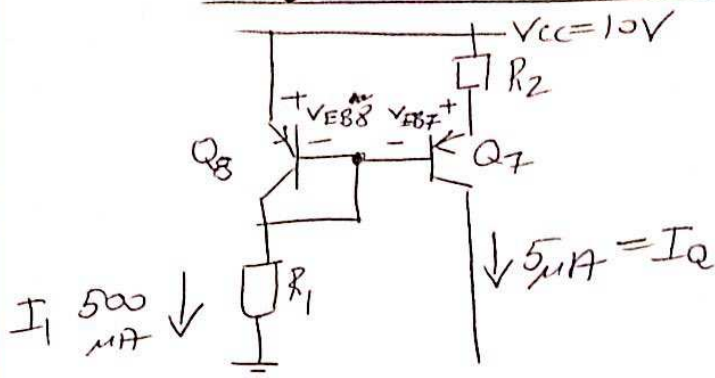

⇒ Neglect base currents

⇒ eqns


$$\left. \begin{aligned} V_{EB8} + I_1 R_1 &= V_{CC} \\ -V_{EB8} + V_{EB7} + I_Q R_2 &= 0 \\ I_1 &= I_S \exp\left(\frac{V_{EB8}}{V_T}\right) \\ I_Q &= I_S \exp\left(\frac{V_{EB7}}{V_T}\right) \end{aligned} \right\}$$

4 eqns

4 unknowns: $\begin{bmatrix} V_{EB8} \\ V_{EB7} \\ R_1 \\ R_2 \end{bmatrix}$


R_{tail} = Output impedance of the tail current source
see the soln to problem 9.29 in Rashid.

Small-signal equivalent circuit

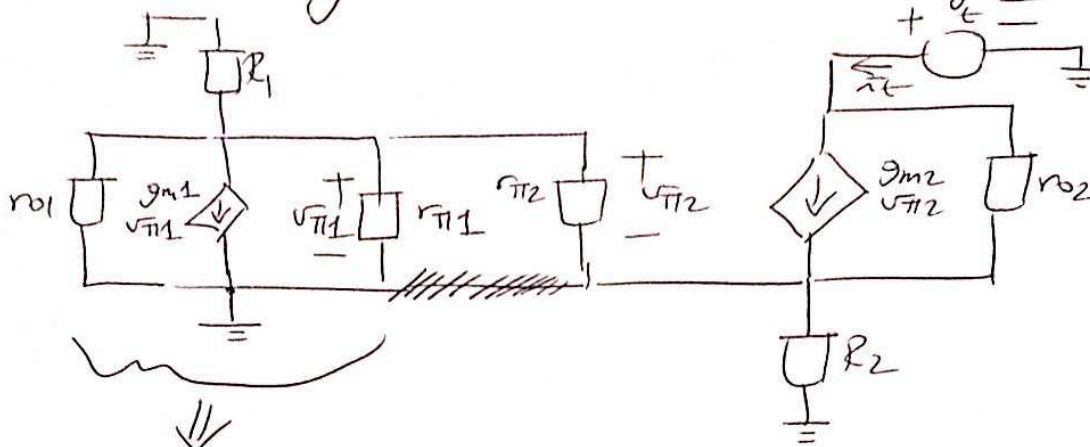

$$R = R_1 \parallel r_{o1} \parallel \frac{1}{g_{m1}} \parallel r_{\pi 1}$$

then we have

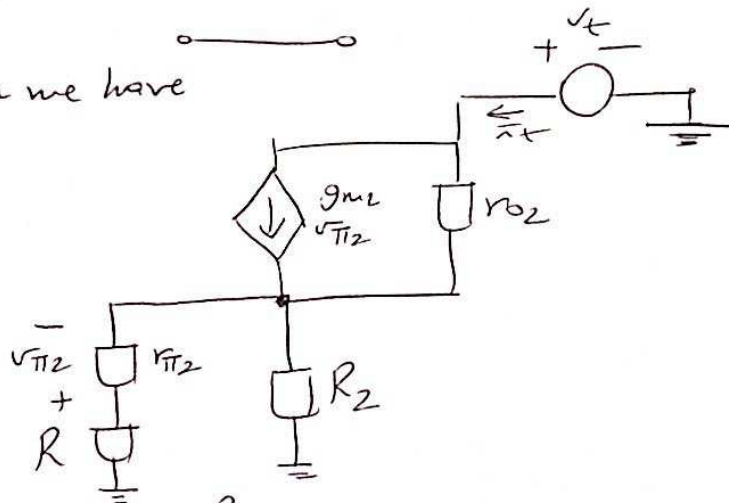

$$-v_{\pi 2} = \tilde{v}_t \frac{R_2}{R_2 + r_{\pi 2} + R} \cdot r_{\pi 2}$$

$$v_t = (\tilde{v}_t - g_{m2} v_{\pi 2}) r_{o2} + \tilde{v}_t \frac{R_2 (R + r_{\pi 2})}{R_2 + r_{\pi 2} + R}$$


$$R_{out} = \frac{v_t}{\tilde{v}_t} = r_{o2} + g_{m2} r_{o2} \frac{R_2 r_{\pi 2}}{R_2 + r_{\pi 2} + R} + \frac{R_2 (R + r_{\pi 2})}{R_2 + r_{\pi 2} + R}$$

Generated by CamScanner

$$R_{out} = r_{o2} + (1 + g_{m2} r_{o2}) \frac{R_2 r_{\pi 2}}{R_2 + r_{\pi 2} + R} + \frac{R_2 R}{R_2 + r_{\pi 2} + R}$$

Rashid
9.29
Cont-

large signal analysis

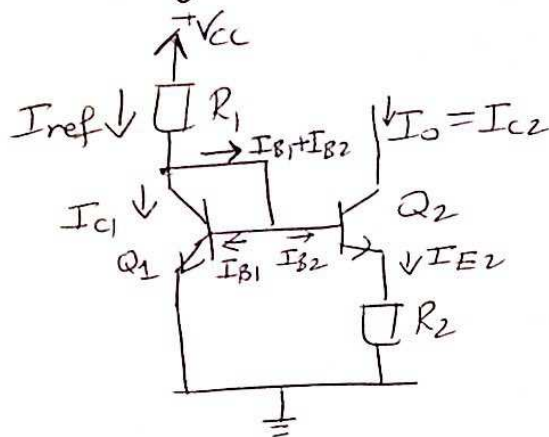

$$I_{ref} = I_{C1} + I_{B1} + I_{B2} = \frac{V_{CC} - V_{BE1}}{R_1} = \frac{V_{CC} - V_T \ln \frac{I_{C1}}{I_S}}{R_1} \quad (1)$$

$$I_{C1} = I_S \exp \left(\frac{V_{BE1}}{V_T} \right)$$

$$I_{C2} = I_o = I_S \exp \left(\frac{V_{BE2}}{V_T} \right) = \beta I_{B2}$$

$$V_{BE1} = V_{BE2} + (\beta + 1) I_{B2} R_2$$

$$V_T \ln \frac{I_{C1}}{I_S} = V_T \ln \frac{I_{C2}}{I_S} + (\beta + 1) I_{B2} R_2$$


$$V_T \ln \frac{I_{C1}}{I_{C2}} = (\beta + 1) I_{B2} R_2 = V_T \ln \frac{I_{B1}}{I_{B2}} \quad (2)$$

Make use of (1) and (2) and V_T, I_S and other parameters
 \Rightarrow solve for I_{B1} and I_{B2}

Generated by CamScanner

PMOS Differential Amplifier with NPN BJT Active Load**Rashid 9.47**

9.47 A BiCMOS amplifier is shown in Fig. P9.47. The PMOS parameters are $V_t = -3$ V and $V_{GS} = -6$ V at $I_D = 1$ mA. The BJT parameters are $\beta_{F(\text{nnp})} = 100$, $\beta_{F(\text{pnp})} = 50$, and $V_A = 40$ V. Assume $V_{DD} = -V_{EE} = 15$ V and $I_Q = 200$ μ A. Calculate A_d , A_c , and CMRR.

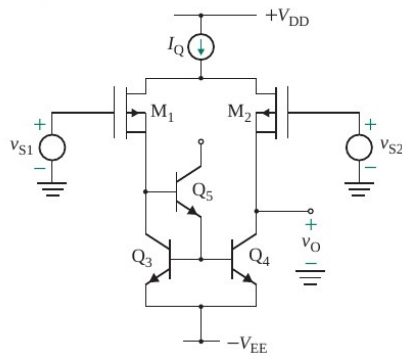FIGURE P9.47

Necessary Knowledge and Skills: PMOS differential amplifier, ideal current source for tail current, BJT current mirror for active load, smaller base current drawn by Q5 from the reference current at the expense of higher power and another VBE loss, single ended amplifier with a voltage gain the same as that of the fully differential amplifier, MOS and BJT small signal equivalent models, voltage gain and input/output impedance computations.

Extra Tasks: Point out the error in the schematic.

Rankin
9.47

Notes on the DC biasing
of the differential stage

$$I_Q = 200 \mu A$$

$$I_{p1} = I_{p2} = 100 \mu A$$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_t|)^2 \quad \text{for PMOS transistors}$$

$$\frac{100 \mu A}{1 \text{ mA}} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (6 \text{ V} - | -3 \text{ V} |)^2$$

compute

then


$$100 \mu A = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - | -3 \text{ V} |)^2$$

computed above

compute in this case (take the positive root that is larger than $| -3 \text{ V} |$)

Small signal analysis of
the modified current source (mirror)

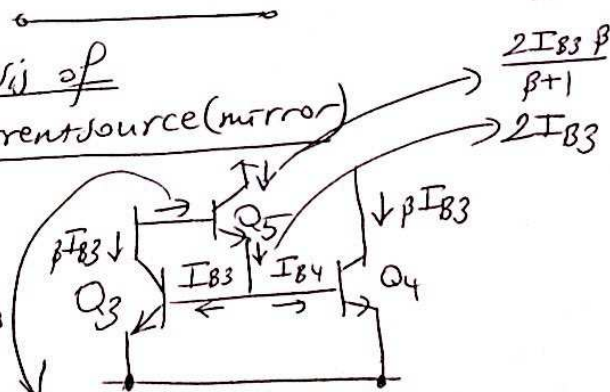⇒ compute large signal currents and then small signal parameters



$$g_{m4} = g_{m3} = \frac{\beta I_{B3}}{V_T}$$

$$g_{m5} = \frac{2\beta I_{B3}}{(\beta+1)V_T}$$

$$r_{\pi3} = r_{\pi4} = \frac{\beta}{g_{m3}} = \frac{V_T}{I_{B3}}$$

$$r_{\pi5} = \frac{(\beta+1)V_T}{2I_{B3}}$$


$$r_{o3} = r_{o4} = \frac{V_A}{\beta I_{B3}}$$

$$r_{o5} = \frac{(\beta+1)V_A}{2\beta I_{B3}}$$


Generated by CamScanner

Model the structure as a current ampli

Part d
9.17
continued

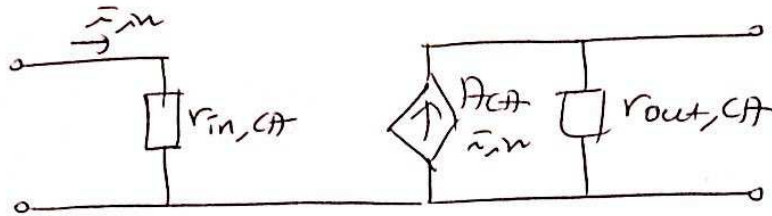

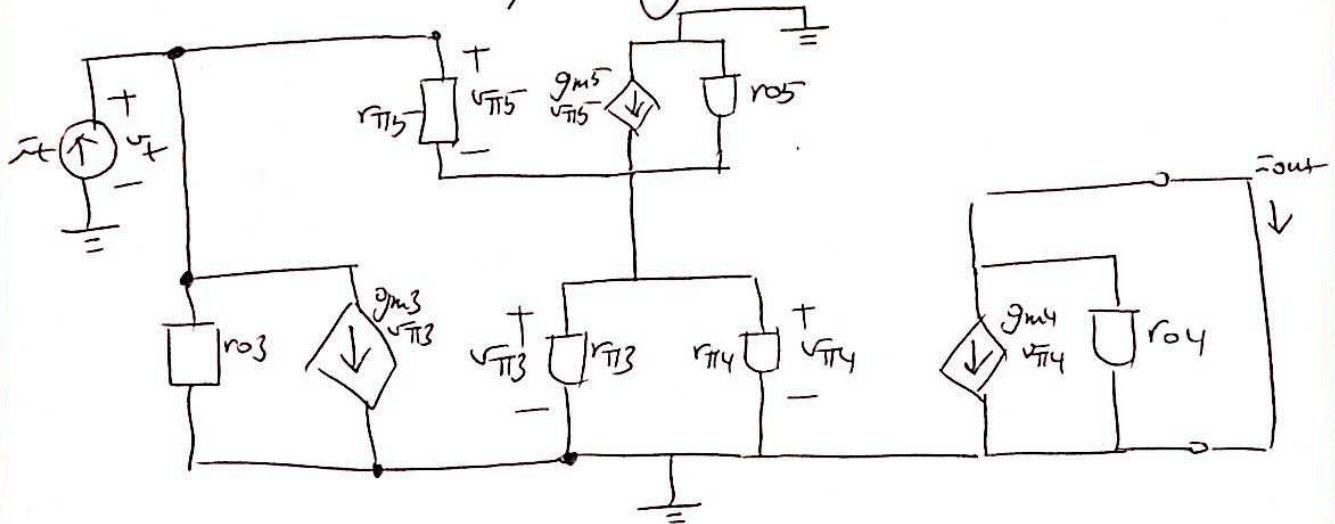\Rightarrow compute $r_{in,CA}$ and A_{CA} with the following setup



$$v_t = v_{\pi 3} + v_{\pi 5}$$

$$-i_t + \frac{v_t}{r_{o3}} + g_{m3} v_{\pi 3} + \frac{v_t - v_{\pi 3}}{r_{\pi 5}} = 0$$

$$-g_{m5} v_{\pi 5} + \frac{v_{\pi 3}}{r_{o5}} + \frac{v_{\pi 3}}{r_{\pi 3}} + \frac{v_{\pi 3}}{r_{\pi 4}} + \frac{v_{\pi 3} - v_t}{r_{\pi 5}} = 0$$

comparable
cannot set
rid of any

$$-i_t = \frac{v_t}{r_{o3} \parallel r_{\pi 5}} + v_{\pi 3} \left[g_{m3} - \frac{1}{r_{\pi 5}} \right] = 0$$

note that $g_{m3} \gg \frac{1}{r_{\pi 5}}$

typical values

$$r_{o3} = \frac{V_A}{\beta I_{B3}} \quad r_{\pi 5} = \frac{(\beta+1)V_T}{2I_{B3}}$$

$V_A = 100V$
 $\beta = 100$
 $V_T = 25mV$

$$r_{o3} = \frac{100V}{100 I_{B3}} = \frac{1V}{I_{B3}}$$

$$r_{\pi 5} = \frac{100(26mV)}{2 I_{B3}} = \frac{1.3V}{I_{B3}}$$

Generated by CamScanner

Problem 9.47

$$\frac{v_{\pi 3}}{\frac{1}{g_{m5}} \parallel r_{o5} \parallel r_{\pi 3} \parallel r_{\pi 4} \parallel r_{\pi 5}} = \frac{v_e}{\frac{1}{g_{m5}} \parallel r_{\pi 5}} = \frac{v_e}{\frac{r_{\pi 5}}{(1+\beta)}} \quad \text{Cont.}$$

$$\frac{1}{g_{m5}} \ll r_{o5}$$

$$r_{\pi 3} = r_{\pi 4} \ll r_{\pi 5}$$

LHS: we have $\frac{v_{\pi 3}}{\frac{1}{g_{m5}} \parallel \frac{r_{\pi 3}}{2}}$

$$\frac{1}{g_{m5}} = \frac{(\beta+1)V_T}{2\beta I_{B3}} \approx \frac{V_T}{2I_{B3}} \quad \left(\text{with } \beta \gg 1 \right)$$

$$\frac{r_{\pi 3}}{2} = \frac{V_T}{2I_{B3}}$$

LHS: we then have $\frac{v_{\pi 3}}{r_{\pi 3}/4}$

$$\begin{aligned} \text{LHS} = \text{RHS} &\Rightarrow \frac{v_{\pi 3}}{(r_{\pi 3}/4)} \Rightarrow \frac{v_e}{4I_{B3}} \Rightarrow \frac{v_e}{\frac{r_{\pi 5}}{(1+\beta)}} \Rightarrow \frac{V_T}{2I_{B3}} \\ &\Rightarrow v_{\pi 3} \approx \frac{V_T}{2} \end{aligned}$$

Rashed 9.47
Cont.

$$\tilde{r}_t = \frac{v_t}{r_{o3} // r_{\pi 5}} + \frac{v_t}{2/g_{m3}}$$

$$\frac{2}{g_{m3}} \ll r_{o3}$$

$$r_{\pi 5} = \frac{(\beta+1)V_T}{2I_{B3}} \gg \frac{2}{g_{m3}} = \frac{2V_T}{\beta I_{B3}}$$

$$\frac{v_t}{\tilde{r}_t} \approx \frac{2}{g_{m3}} = r_{in, CH}$$

Compute now A_{CH}

$$v_{\pi 3} = v_{\pi 4} \approx \frac{v_t}{2}$$

$$g_{m4} v_{\pi 4} = -\tilde{r}_{out}$$

$$g_{m4} \frac{v_t}{2} = -\tilde{r}_{out}$$


$$\frac{g_{m4}}{2} \tilde{r}_t = -\tilde{r}_{out}$$

$$\tilde{r}_t = -\tilde{r}_{out} \Rightarrow A_{CH} = -1$$

Setup for computing $r_{out, CH}$

input is open cir.

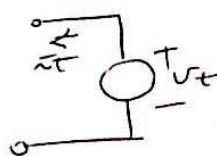no independent source at the input stage
 $v_t = v_{\pi 3} = 0$




connect this at the output

$$\Rightarrow \text{then } r_{out, CH} = r_{o4} = r_{o3}$$


4

we have for the small signal equivalent
of the modified current mirror

Prashid
9.47

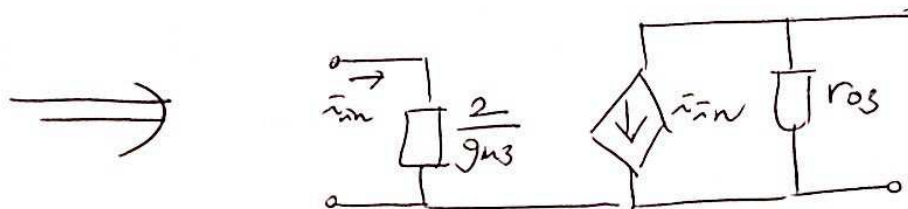

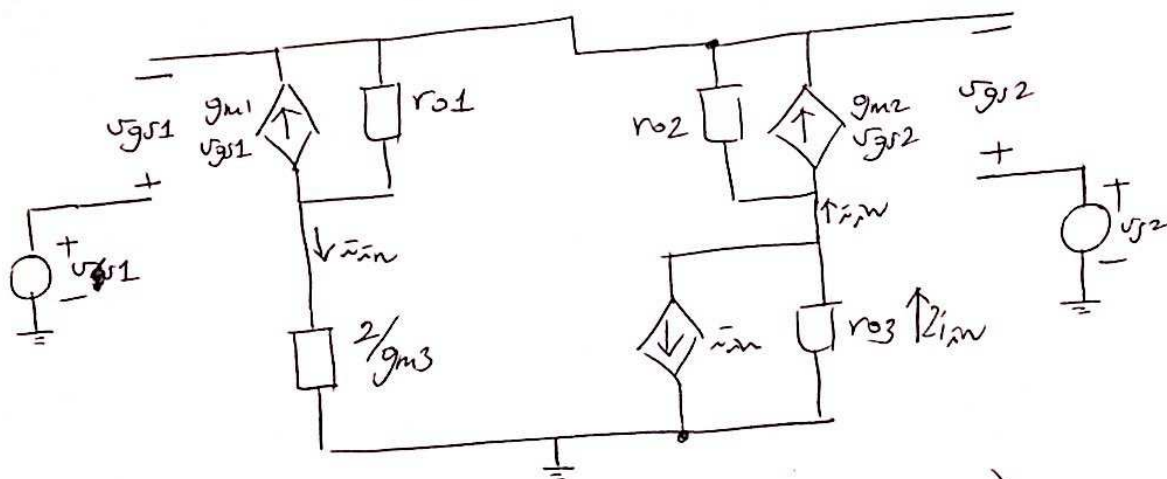⇒ small-signal equivalent of the differential amplifier with the active load



$$\underline{\underline{KVL}}: \frac{2}{g_{m3}} \bar{i}_{in} + 2\bar{i}_{in} r_{o3} + (\bar{i}_{in} - g_{m2} v_{gs2}) r_{o2} + (\bar{i}_{in} + g_{m1} v_{gs1}) r_{o1} = 0$$

note $g_{m1} = g_{m2}$, $r_{o1} = r_{o2}$

also $v_{out} = -2\bar{i}_{in} r_{o3}$

neglect $\left[\frac{2}{g_{m3}} + 2r_{o3} + \underbrace{r_{o2} + r_{o1}}_{2r_{o1}} \right] + g_{m1} r_{o1} (v_{gs1} - v_{gs2}) = 0$

$$2\bar{i}_{in} (r_{o3} + r_{o1}) = -g_{m1} r_{o1} (v_{gs1} - v_{gs2})$$

Generated by CamScanner

Note also that

$$v_{S1} - v_{GS1} = v_{S2} - v_{GS2}$$

$$v_{S1} - v_{S2} = v_{GS1} - v_{GS2}$$

Rashed
9.47
Cont.

$$\underbrace{\left[-2\bar{v}_{in} r_{o3} \right]}_{v_{out}} \left[-\frac{r_{o3} + r_{o1}}{r_{o3}} \right] = -g_{m1} r_{o1} (v_{S1} - v_{S2})$$

$$\frac{v_{out}}{v_{S1} - v_{S2}} = g_{m1} \left[\frac{r_{o1} r_{o3}}{r_{o1} + r_{o3}} \right]$$

$$= g_{m1} (r_{o1} \parallel r_{o3})$$

In the case of common-mode excitation,
 $v_{S1} = v_{S2} \Rightarrow \bar{v}_{in} = 0 \Rightarrow v_{out} = 0$

Then approximately $\frac{v_{out}}{\frac{v_{S1} + v_{S2}}{2}} = 0 \Rightarrow CMRR = +\infty$
 the common mode gain

A more accurate analysis or simulation results are necessary to comment on the common-mode gain and CMRR.


Razavi
10.68

M_5 is the current source.

$R_{out,CS} \Rightarrow R_{out}$ of the current source

$$R_{out,CS} = r_{o5}$$

Differential mode

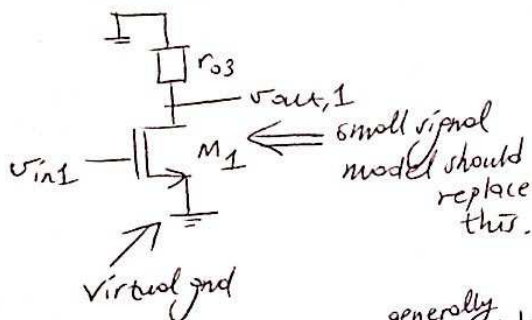

$$\frac{v_{out,1}}{v_{in,1}} = -g_{m1} (r_{o1} \parallel r_{o3})$$

generally neither is much higher than the other


We can also prove that

$$A_d = \frac{v_{out,1} - v_{out,2}}{v_{in,1} - v_{in,2}}$$

\uparrow
Diff mode gain

Since $g_{m1} = g_{m2}$
 $r_{o3} = r_{o4}$
 $r_{o1} = r_{o2}$

Common mode

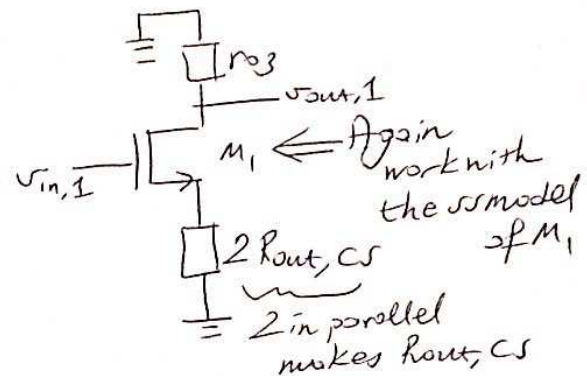

TCA derivations:
(done in many other solutions)

$$A_c = \frac{v_{out,1}}{v_{in,1}} = - \frac{g_{m1}}{1 + g_{m1} 2R_{out,CS}}$$

\uparrow
Common mode gain

$[r_{o3} \parallel r_{out,TCA}]$

and

$$r_{out,TCA} = (1 + g_{m1} r_{o1}) 2R_{out,CS} + r_{o1}$$

(remember the cascode config)

\Rightarrow Note here that $r_{o3} \ll r_{out,TCA}$

Common mode gain
 A_c simplified (approx.)

Razani
10.68
 continued

$$A_c \approx \frac{g_{m1} r_{o3}}{1 + g_{m1}^2 R_{out,CS}}$$

$$\text{then } CMRR = \frac{A_d}{A_c} \approx \frac{\cancel{g_{m1}} \frac{r_{o1} r_{o3}}{r_{o1} + r_{o3}}}{\frac{g_{m1} r_{o3}}{1 + g_{m1}^2 R_{out,CS}}}$$

$$= \frac{r_{o1} (1 + g_{m1}^2 R_{out,CS})}{r_{o1} + r_{o3}}$$

—————

BJT Differential Amplifier**Razavi 10.81**

81. The differential pair depicted in Fig. 10.95 must provide a gain of 5 and a power budget of 4

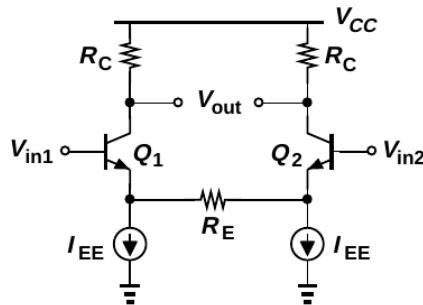


Figure 10.95

mW. Moreover, the gain of the circuit must change by less than 2% if the collector current of either transistor changes by 10%. Assuming $V_{CC} = 2.5$ V and $V_A = \infty$, design the circuit. (Hint: a 10% change in I_C leads to a 10% change in g_m .)

Necessary Knowledge and Skills: BJT differential amplifier with two tail currents, resistor loads, sensitivity computation, differential gain calculation, input/output impedance calculations, power budget in DC, design question.

Power budget

$$\frac{P_{avg}}{10.81}$$

in DC $\Rightarrow v_{in1} = v_{in2}$ (DC voltages)No current thru R_E


$$\text{then DC Power} = V_{CC} \cdot 2I_{EE}$$

$$\text{Power budget} = 4\text{mW} > V_{CC} \cdot 2I_{EE} = (2.5\text{V}) \cdot 2 \cdot I_{EE}$$

$$\text{then } I_{EE} < \frac{4\text{mW}}{5\text{V}} = 0.8\text{mA}$$

Differential Gain

(see TCA related derivations)

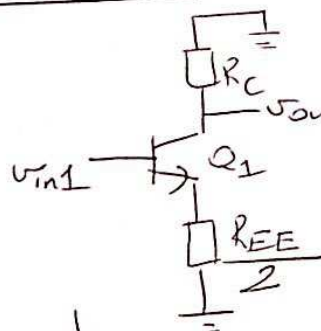half cir

$$A_d = \frac{v_{out1}}{v_{in1}} \approx - \frac{g_{m1}}{1 + g_{m1} \frac{R_{EE}}{2}} \cdot R_C$$

$$\text{Note that } g_{m1} = \frac{I_{C1}}{V_T} \approx \frac{I_{EE}}{25\text{mV}}$$

$$\left| \frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} \right| \approx A_d = 5 \quad \text{specification}$$

$$= \left| - \frac{\frac{I_{C1}}{V_T} \cdot R_C}{1 + \frac{I_{C1}}{V_T} \frac{R_{EE}}{2}} \right|$$

Also another requirement

$$\left| \frac{\Delta A_d}{A_d} \right| < 2\% \quad \text{when} \quad \left| \frac{\Delta I_{C1}}{I_{C1}} \right| = 10\%$$

this means

$$\left| \frac{\Delta A_d}{\Delta I_{C1}} \frac{I_{C1}}{A_d} \right| < \frac{1}{5} \Rightarrow \left| \frac{\partial A_d}{\partial I_{C1}} \right| < \frac{1}{5}$$

sensitivity of A_d w.r.t. I_{C1}

Generated by CamScanner

Razavi
10.81

continued

$$\int_{I_{C1}}^{A_d} = \frac{\partial A_d}{\partial I_{C1}} \frac{I_{C1}}{A_d}$$

$$\text{where } A_d = -R_C \frac{2 I_{C1}}{2 V_T + I_{C1} R_{EE}}$$

$$\begin{aligned} \frac{\partial A_d}{\partial I_{C1}} &= -R_C \left[\frac{2(2V_T + I_{C1} R_{EE}) - R_{EE}(2I_{C1})}{(2V_T + I_{C1} R_{EE})^2} \right] \\ &= -R_C \frac{4V_T}{(2V_T + I_{C1} R_{EE})^2} \end{aligned}$$

$$\begin{aligned} \frac{\partial A_d}{\partial I_{C1}} \frac{I_{C1}}{A_d} &= \left[\cancel{(-R_C)} \frac{\cancel{4V_T}}{(2V_T + I_{C1} R_{EE})^2} \right] \\ &\quad \left[\cancel{\left(\frac{1}{-R_C} \right)} \frac{\cancel{(2V_T + I_{C1} R_{EE})}}{\cancel{2I_{C1}}} \right] \cancel{I_{C1}} \end{aligned}$$

$$= \frac{2V_T}{2V_T + I_{C1} R_{EE}}$$

$$\left| \frac{A_d}{I_{C1}} \right| = \left| \frac{2V_T}{\underbrace{2V_T + I_{C1} R_{EE}}_{\text{already positive}}} \right| < \frac{1}{5}$$

Razan
10.81
Continued

$$\Rightarrow 10V_T < 2V_T + I_{C1} R_{EE}$$

$$8V_T < \underbrace{I_{C1} R_{EE}}_{\approx I_{EE}}$$

$$\underbrace{8V_T}_{25mV} < I_{EE} R_{EE}$$

$$200mV < I_{EE} R_{EE}$$

Our constraints are

$$I_{EE} < 0.8mA$$

$$200mV < I_{EE} R_{EE}$$

$$|A_d| = R_C \frac{2I_{EE}}{2V_T + I_{EE} R_{EE}} = 5$$

$$\text{choose } I_{EE} = 0.6mA$$

$$R_{EE} > \frac{200mV}{0.6mA} = 333\Omega$$

$$\text{choose } R_{EE} = 400\Omega$$

then
$$\frac{2(0.6\text{mA})}{2(25\text{mV}) + (0.6\text{mA})(400\Omega)} R_C = 5$$

Razavi
10.81
continued

$$\frac{1.2\text{mA}}{\underbrace{50\text{mV}}_{0.05\text{V}} + \underbrace{(0.6\text{mA})(0.4\text{k})}_{0.24\text{V}}} R_C = 5$$

$$R_C = \frac{5(0.29)\text{V}}{1.2\text{mA}}$$

$$= \frac{1.35}{1.2} \text{ k}\Omega$$

—————

BJT Differential Amplifier

Sedra 7.38

7.38 Find the voltage gain and input resistance of the amplifier in Fig. P7.38 assuming that $\beta = 100$.

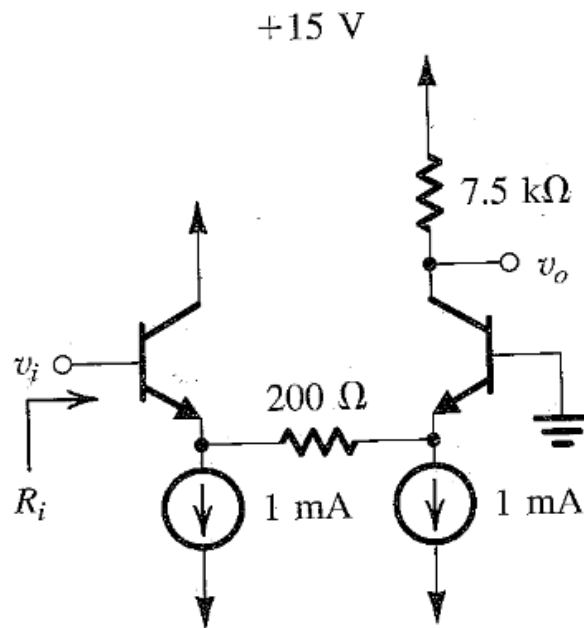


FIGURE P7.38

Necessary Knowledge and Skills: Cascaded amplifiers, common collector (emitter follower) followed by common base, input/output impedance computations, voltage gain calculations.

Sadra
7.38

DC biasing

With $v_{in} = 0V$ in DC
the two transistors Q_1 and Q_2 will almost be
in balance (despite the $7.5k\Omega$ resistance),
and $I_{C,Q1} \approx I_{C,Q2} \approx 1mA$ (in DC)
with the current over $200\Omega \Rightarrow 0V$ (in DC)

$$g_{m1} = \frac{I_{C,Q1}}{V_T} = \frac{1mA}{26mV} \quad \left(\begin{array}{l} \text{the same for } g_{m2} \\ \text{(approx)} \end{array} \right)$$


$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{g_{m1}} \Rightarrow \text{the same for } r_{\pi 2}$$

$$r_{o1} \approx \frac{V_A}{I_{C,Q1}} \quad (\text{can be computed if } V_A \text{ is given}) \Rightarrow \text{the same for } r_{o2}$$

Small signal analysis

We have (in s.s.) a cascade of two amplifiers

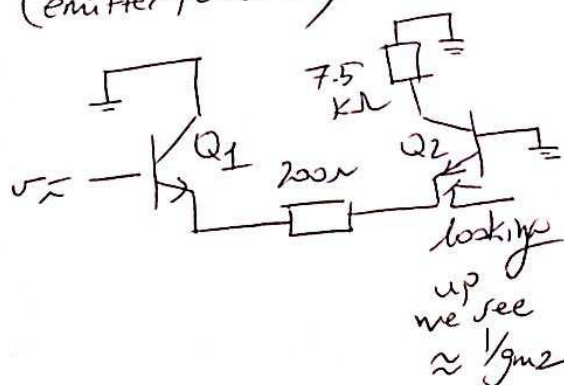
Common collector (emitter follower) + Common base



(in this schematic, replace Q_1 and Q_2 by their s.s. equiv. cir)

Common ~~emitter~~ collector (emitter follower)
stage

Sadra
7-38
continued

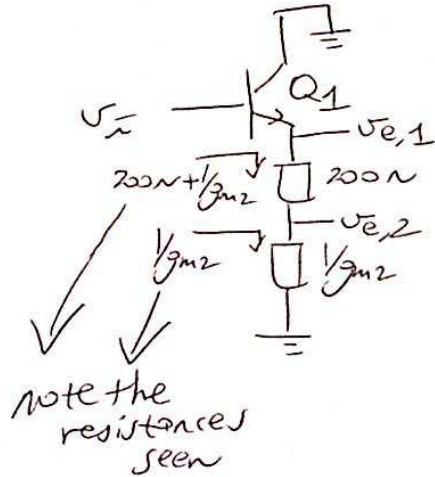


$$\frac{v_{e,1}}{v_{in}} \approx \frac{200\Omega + \frac{1}{g_{m2}}}{200\Omega + \frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

< 1
(see the derivations for common collector voltage gain)

$$\frac{v_{e,2}}{v_{e,1}} = \frac{\frac{1}{g_{m2}}}{200\Omega + \frac{1}{g_{m2}}} \quad (\text{voltage divider})$$

$$\begin{aligned} \text{then } \frac{v_{e,2}}{v_{in}} &= \frac{v_{e,2}}{v_{e,1}} \frac{v_{e,1}}{v_{in}} \\ &= \frac{\frac{1}{g_{m2}}}{200\Omega + \frac{1}{g_{m2}}} \frac{200\Omega + \frac{1}{g_{m2}}}{200\Omega + \frac{1}{g_{m2}} + \frac{1}{g_{m1}}} \\ &= \frac{\frac{1}{g_{m2}}}{200\Omega + \frac{1}{g_{m2}} + \frac{1}{g_{m1}}} \end{aligned}$$

Common base stage

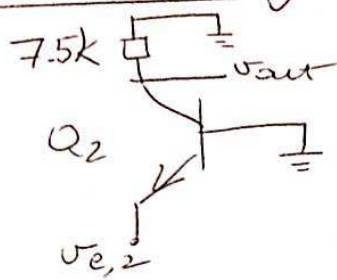

$$\frac{v_{out}}{v_{e,2}} \approx g_{m2} (7.5k\Omega)$$

(see the derivations for common base amplifiers)

then $\frac{v_{out}}{v_{in}} = \frac{v_{e,2}}{v_{in}} \cdot \frac{v_{out}}{v_{e,2}}$

$$\approx \frac{1/g_{m2}}{200\Omega + 1/g_{m2} + 1/g_{m1}} \cdot g_{m2} (7.5k\Omega)$$

$$= \frac{7.5k\Omega}{200\Omega + 1/g_{m2} + 1/g_{m1}} \approx \frac{7.5k\Omega}{250\Omega} = 30$$

$$\approx \left(\frac{1mA}{25mV} \right)^{-1} = 25\Omega$$

see TCA derivations for R_{in} (they apply even if we do not have a TCA here)

$$R_{in} \approx \left[1 + g_{m1} \left[200\Omega + 1/g_{m2} \right] \right] r_{\pi 1}$$

$$\approx \left[1 + g_{m1} 200 + 1 \right] r_{\pi 1} = 2r_{\pi 1} + 200 \cdot 100 = 5k + 20k = 25k$$

$\beta(25\Omega)$
 $g_m r_{\pi} = \beta$

Generated by CamScanner

(3)

