



GTU
Electronics Engineering

ELEC 331
Electronic Circuits 2

Fall Semester

Instructor: Assist. Prof. Önder Şuvak

HW 2
Questions and Answers

Updated October 20, 2017 - 13:37

Assigned:

Due:

Answers Out:


Late Due:

Contents

Title Page	1
Contents	1
Question 1	2
Question	2
Solution	3
Question 2	10
Question	10
Solution	11
Question 3	14
Question	14
Solution	15
Question 4	17
Question	17
Solution	18
Question 5	21
Question	21
Solution	22
Question 6	24
Question	24
Solution	25

BJT Differential Amplifier Design**Razavi 10.31**


31. The circuit of Fig. 10.68 must provide a gain of 50 with $R_1 = R_2 = 5 \text{ k}\Omega$. If $V_{A,n} = 5 \text{ V}$ and $V_{A,p} = 4 \text{ V}$, calculate the required tail current.

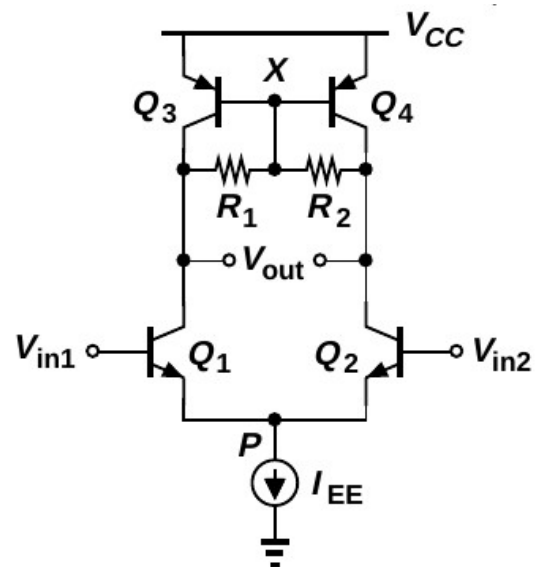**Figure 10.68**

Necessary Knowledge and Skills: BJT small signal analysis, differential mode half circuit analysis, output impedance calculation, voltage gain calculation, parameter selection for design specification


Razavi
10.31

Differential mode half cir

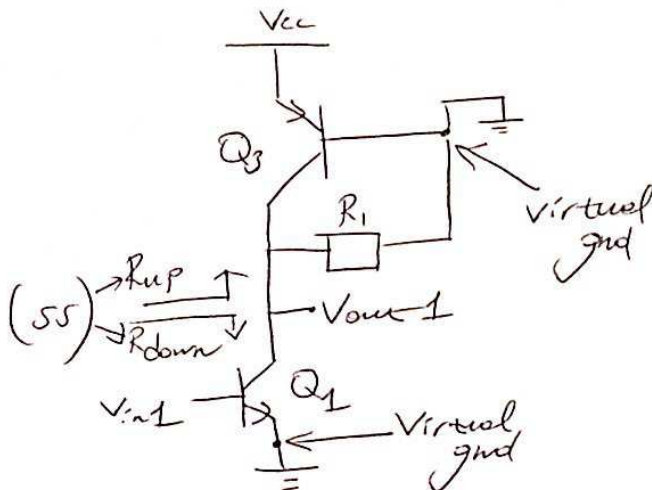

$$R_{down} = r_{o1}$$

Rup computation

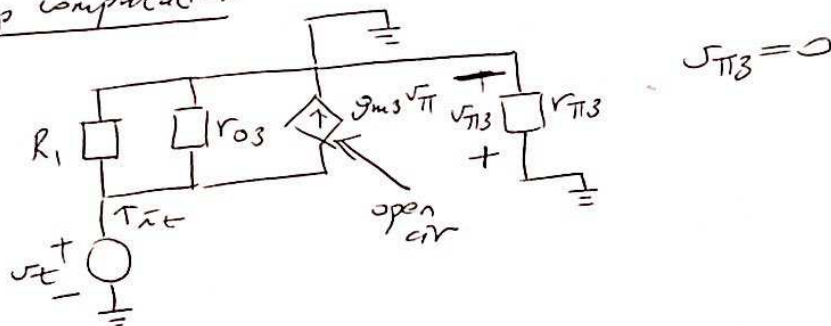

$$R_{up} = \frac{V_t}{I_t} = R_1 \parallel r_{o3}$$

$$\text{then } \frac{V_{out1}}{V_{in1}} = -g_{m1} [R_1 \parallel r_{o3} \parallel r_{o1}]$$

(common emitter conf.)


$$\text{Similarly (with } V_{in2} = -V_{in1}) \quad \frac{V_{out2}}{V_{in2}} = \text{the same}$$

$$\text{and } \frac{V_{out}}{V_{in1} - V_{in2}} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_{m1} [R_1 \parallel r_{o3} \parallel r_{o1}]$$


Generated by CamScanner

Common mode half cir.


Razavi
10.31
continued

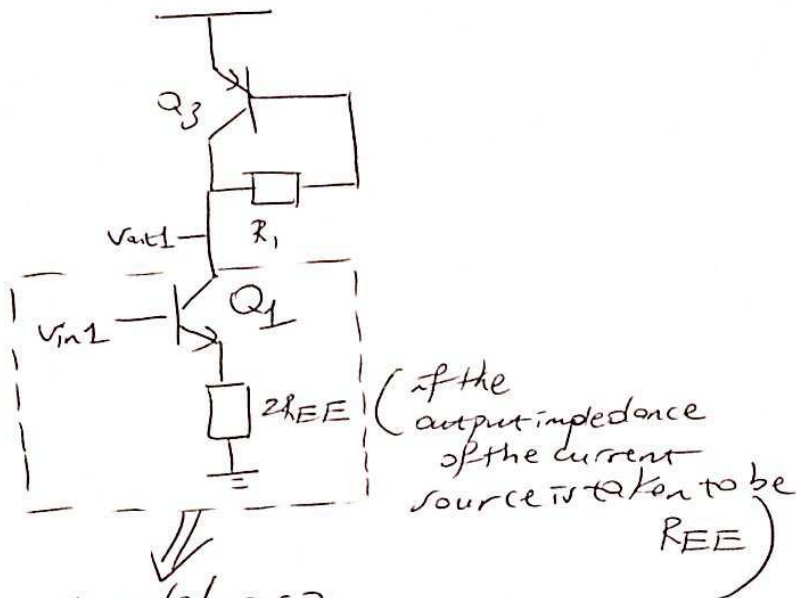

model as a
transconductance
ampl.

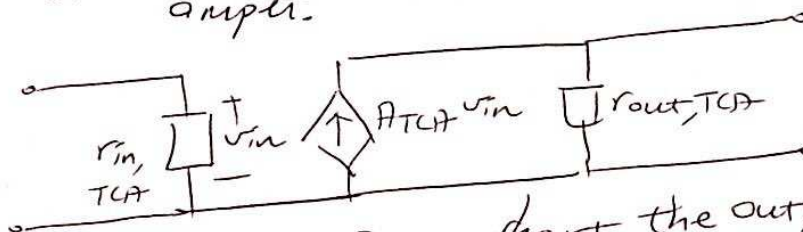

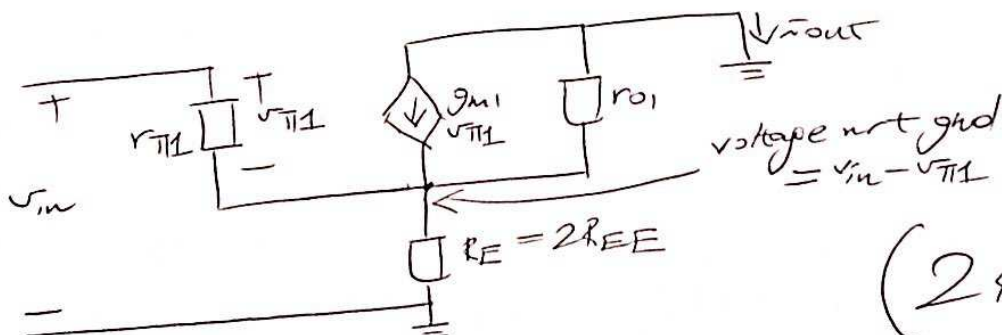to compute A_{TCF} , short the output,
compute $\frac{\tilde{v}_{out}}{\tilde{v}_{in}}$.



$$\frac{v_{in} - v_{\pi 1} - v_{in}}{r_{\pi 1}} + \frac{v_{in} - v_{\pi 1}}{R_E} - g_{m1} v_{\pi 1} + \frac{v_{in} - v_{\pi 1}}{r_{o1}} = 0$$

$$\tilde{v}_{out} - \frac{v_{in} - v_{\pi 1}}{r_{o1}} + g_{m1} v_{\pi 1} = 0$$

Generated by CamScanner

2


$$\frac{v_{in}}{R_E // r_{o1}} = \frac{v_{\pi 1}}{r_{\pi 1} // R_E // \frac{1}{g_{m1}} // r_{o1}}$$

$$\bar{v}_{out} + \frac{v_{\pi 1}}{r_{o1} // \frac{1}{g_{m1}}} = \frac{v_{in}}{r_{o1}}$$

P. 720
10.31
Continued
(Assume $r_{\pi 1}, r_{o1}$ big)

$$\left. \begin{aligned} v_{in} \frac{1/g_{m1} // R_E}{R_E} &= v_{\pi 1} \\ \bar{v}_{out} + \frac{v_{\pi 1}}{1/g_{m1}} &= 0 \end{aligned} \right\} \bar{v}_{out} + v_{in} \frac{\cancel{1/g_{m1} // R_E}}{\cancel{1/g_{m1}} + R_E} = 0$$
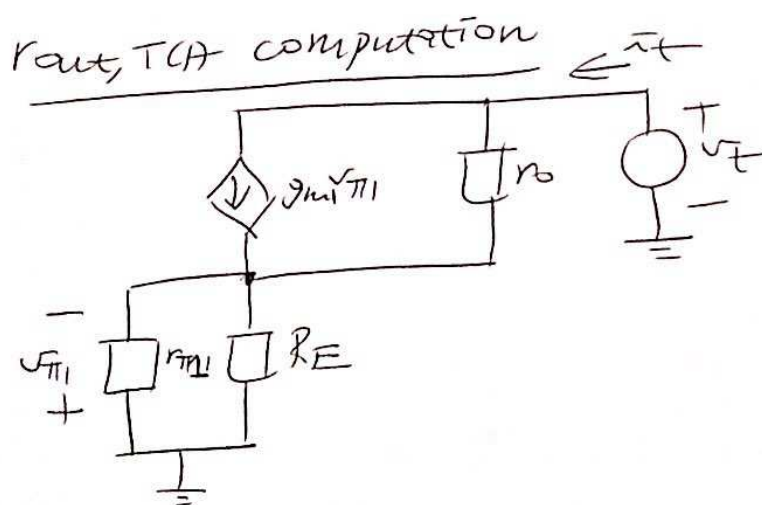
$$\text{then } A_{TCA} = \frac{\bar{v}_{out}}{v_{in}} = - \frac{g_{m1}}{1 + g_{m1} R_E}$$



(KVL)


Razavi
10.31
continued

$$\left(\tilde{v}_t - g_{m1} v_{\pi 1} \right) r_{o1} + \underbrace{\tilde{v}_t (r_{\pi 1} // R_E)}_{= \tilde{v}_t} = \tilde{v}_t$$

$$\tilde{v}_t \left[r_{o1} (1 + g_{m1} (r_{\pi 1} // R_E)) + (r_{\pi 1} // R_E) \right] = \tilde{v}_t$$

$$\frac{\tilde{v}_t}{\tilde{v}_t} = r_{o1} (1 + g_{m1} R_E) = r_{out, TC1}$$

Now consider

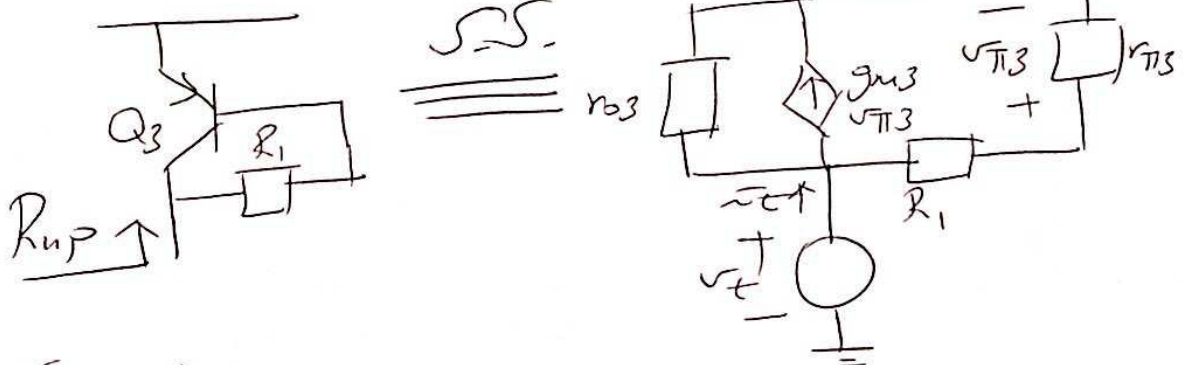

$$(KCL) -\tilde{v}_t + \frac{\tilde{v}_t}{r_{o3}} + g_{m3} v_{\pi 3} + \frac{\tilde{v}_t}{R_1 + r_{\pi 3}} = 0$$

$$v_{\pi 3} = \tilde{v}_t \frac{r_{\pi 3}}{R_1 + r_{\pi 3}}$$

Generated by CamScanner

4

$$-\bar{v}_t + \frac{v_t}{r_{o3} \parallel \frac{R_1 + r_{\pi 3}}{1 + \beta_3}} = 0$$

Razaw
10.31
continued

$$R_{up} = \frac{v_t}{\bar{v}_t} = r_{o3} \parallel \frac{R_1 + r_{\pi 3}}{1 + \beta_3}$$

(since $\beta_3 = g_{m3} r_{\pi 3}$)

$$\frac{v_{out1}}{v_{in1}} = A_{TCA} \left[r_{out, TCA} \parallel R_{up} \right]$$

for common mode

$$\text{Common mode gain} \approx - \frac{g_{m1}}{1 + g_{m1} 2R_{EE}}$$

lesser than g_{m1}

$$\left[r_{o1} (1 + g_{m1} 2R_{EE}) \parallel \left(r_{o3} \parallel \frac{R_1 + r_{\pi 3}}{1 + \beta_3} \right) \right]$$

bigger than r_{o1} , big

big

may be very small if R_1 is small

$$CMRR = \frac{\text{Diff mode gain}}{\text{Common mode gain}}$$

Generated by CamScanner (5)

$\frac{R_{azami}}{10.31}$
continued

$$|C_{MRR}| \approx \frac{g_{m1} (R_1 // r_{o3} // r_{o4})}{\frac{g_{m1}}{1 + g_{m1} 2R_{EE}} \cdot \frac{R_1 + r_{\pi 3}}{1 + \beta_3}}$$

maybe small (pointing to R_1)
big (pointing to r_{o3})
big (pointing to r_{o4})

$$\approx \left(1 + g_{m1} 2R_{EE} \right) \frac{R_1 (1 + \beta_3)}{R_1 + r_{\pi 3}}$$

—

Design question

Razavi
10.31
continued

$$I_{C,Q1} = I_{C,Q2} = I_{C,Q3} = I_{C,Q4} \approx \frac{I_{EE}}{2}$$

if the base currents of Q_3 and Q_4 are negligible.

$$g_{m1} = \frac{I_{C,Q1}}{V_T} = \frac{I_{EE}}{2V_T} \quad \curvearrowright 26\text{mV}$$

$$R_1 = 5\text{k}\Omega$$

$$r_{o3} = \frac{V_{A,P}}{I_{C,Q3}} = \frac{4\text{V}}{I_{EE}/2} = \frac{8}{I_{EE}}$$

$$r_{o1} = \frac{V_{A,n}}{I_{C,Q1}} = \frac{5\text{V}}{I_{EE}/2} = \frac{10}{I_{EE}}$$

$$\begin{aligned} |G_{m1}| &= g_{m1} [R_1 \parallel r_{o3} \parallel r_{o1}] \\ &= \frac{I_{EE}}{2V_T} \left[5\text{k} \parallel \frac{8}{I_{EE}} \parallel \frac{10}{I_{EE}} \right] = 50 \end{aligned}$$

↑
design spec

calculate I_{EE} !

MOS Amplifier

Razavi 10.51

- 51.** A student who has a single-ended voltage source constructs the circuit shown in Fig. 10.75, hoping to obtain differential outputs. Assume perfect symmetry but $\lambda = 0$ for simplicity.

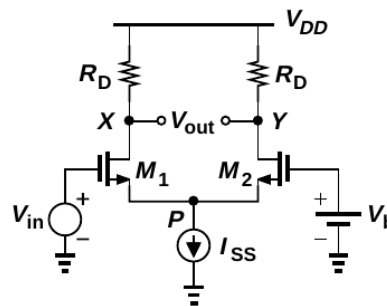



Figure 10.75

- Viewing M_1 as a common-source stage degenerated by the impedance seen at the source of M_2 , calculate v_X in terms of v_{in} .
- Viewing M_1 as a source follower and M_2 as a common-gate stage, calculate v_Y in terms of v_{in} .
- Add the results obtained in (a) and (b) with proper polarities. If the voltage gain is defined as $(v_X - v_Y)/v_{in}$, how does it compare with the gain of differentially-driven pairs?

Necessary Knowledge and Skills: Common source/gate amplifiers, small signal equivalent MOS, differential pair gain and other calculations, performance comparisons


small signal equiv of the cir

Razavi
10.51

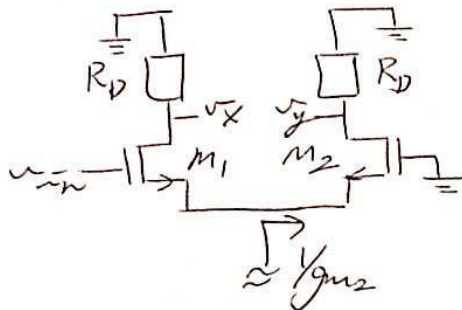

(Need to replace M_1 and M_2 by their small signal equivalent cir.)

Calculate $\frac{v_x}{v_{in}}$

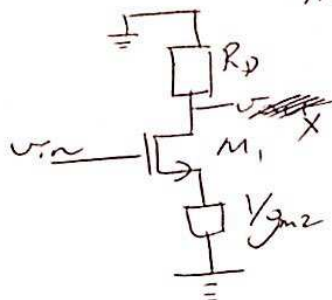

(source degenerated common source amplifier)

(See TCA related computations)

$$\frac{v_x}{v_{in}} = -g_{m1} \frac{1}{1 + g_{m1} \frac{1}{g_{m2}}}$$

$$\rightarrow [R_D \parallel r_{out, TCA}]$$

$$\text{where } r_{out, TCA} = \frac{1}{(1 + g_{m1} r_{o1}) g_{m2}} + r_{o1}$$

$$\text{since } \lambda = 0 \Rightarrow r_{o1} = \infty$$

\Rightarrow We have, for perfectly symmetric diff-amp,


$$g_m = g_{m1} = g_{m2}$$

$$\text{then } \frac{v_x}{v_{in}} = -\frac{g_m}{2} R_D$$

Calculate $\frac{v_y}{v_{in}}$

Problem 10.51
continued

Analyze a cascade of amplifiers

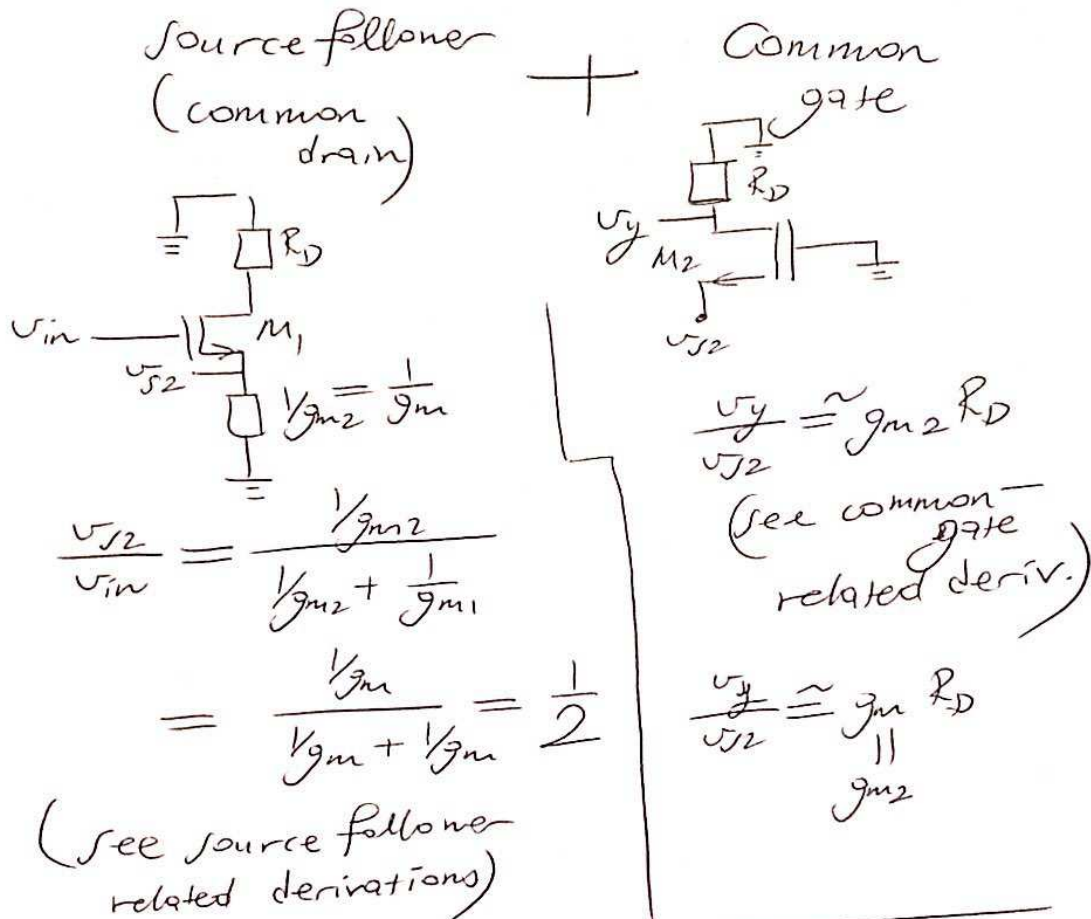


overall $\Rightarrow \frac{v_y}{v_{in}} = \frac{g_m R_D}{2}$

$$\frac{v_{out}}{v_{in}} = \frac{v_x - v_y}{v_{in}} = \frac{\left(-\frac{g_m R_D}{2} - \frac{g_m R_D}{2}\right) v_{in}}{v_{in}}$$


$$= -g_m R_D$$

With diff. driven pairs
(on the other hand)

Reason
10.51
continued

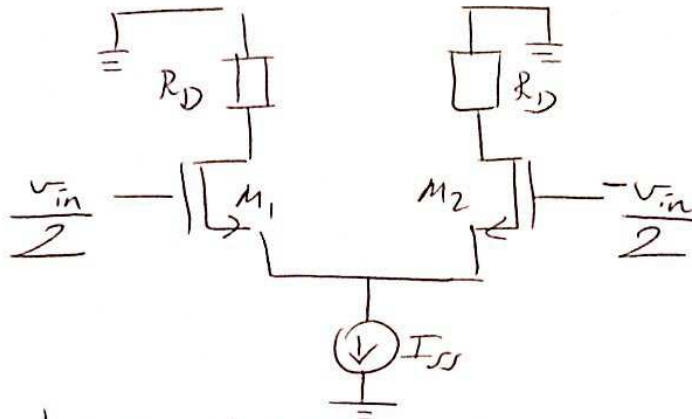

half cir (diff mode)

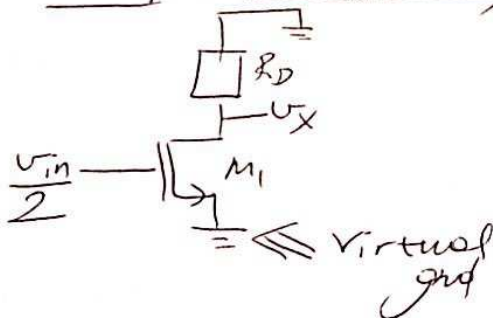

$$v_x = \left(\frac{v_{in}}{2}\right) \left[\frac{-g_{m1} (R_D \parallel r_{o1})}{g_m \parallel (+\infty)} \right]$$

$$= -g_m R_D \frac{v_{in}}{2}$$

Similarly $v_y = \left(-\frac{v_{in}}{2}\right) \left[\frac{-g_{m2} (R_D \parallel r_{o2})}{g_m \parallel +\infty} \right]$

$$= g_m R_D \frac{v_{in}}{2}$$


Then $\frac{v_x - v_y}{v_{in}} = \frac{-g_m R_D \frac{v_{in}}{2} - g_m R_D \frac{v_{in}}{2}}{v_{in}}$

$$= -g_m R_D$$

We get the same result!

MOS Differential Pair**Razavi 10.53 c**

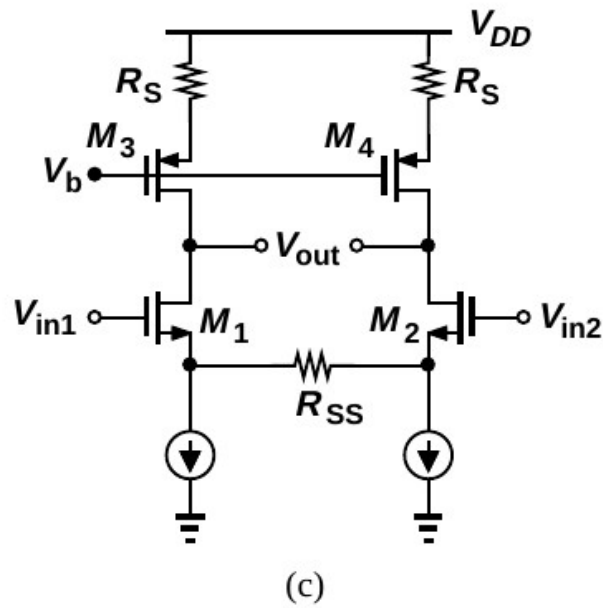
53. Calculate the differential voltage gain of the circuits depicted in Fig. 10.77. Assume perfect symmetry and $\lambda > 0$. You may need to compute the gain as $A_v = -G_m R_{out}$ in some cases.




Necessary Knowledge and Skills: MOS small signal analysis, output impedance calculation, common/differential mode half circuits, cascode structure, virtual ground in differential mode, voltage gain computation

Razak
10.53

Diff.
mode
half cir.

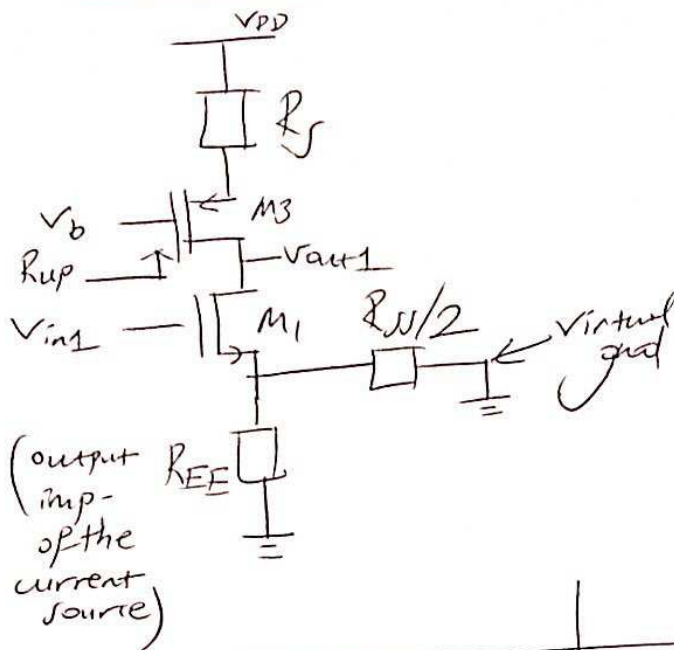

Common
mode
half cir.

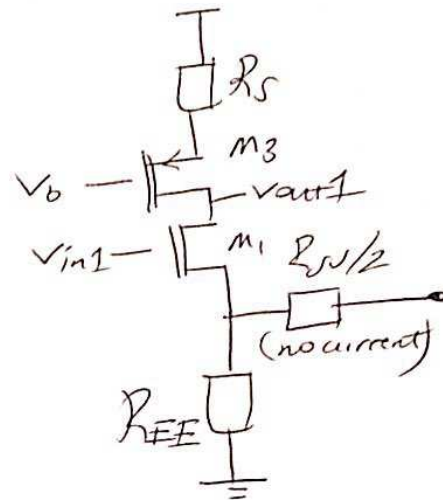

Diff. mode analysis

see TCA (transconductance ampl. analysis) in other answers and lecture notes.

see cascode output impedance comput. in other answers.

$$A_{TCA,d} = - \frac{g_{m1}}{1 + g_{m1} R_{E,d}}$$

$$R_{E,d} = R_{EE} \parallel \frac{R_{S1}}{2}$$

$$r_{out,TCA,d} = r_{o1} (1 + g_{m1} R_{E,d})$$

$$R_{up} = (1 + g_{m3} r_{o3}) R_S + r_{o3}$$

Common mode analysis

needed here as well

needed here

$$A_{TCA,c} = - \frac{g_{m1}}{1 + g_{m1} R_{E,c}}$$

$$R_{E,c} = R_{EE}$$

$$r_{out,TCA,c} = r_{o1} (1 + g_{m1} R_{E,c})$$

the same

Generated by CamScanner

Diff. mode

$$\frac{v_{out1}}{v_{in1}} = A_{TCA,d} \left[r_{out,TCA,d} // R_{up} \right]$$

Common mode

$$\frac{v_{out,1}}{v_{in1}} = A_{TCA,c} \left(r_{out,TCA,c} // R_{up} \right)$$

if $\frac{R_{SS}}{2} \ll R_{EE}$ (desired) (*)

$|CMRR| = \frac{\text{Diffmode gain}}{\text{common mode gain}} \approx \frac{R_{SS}}{2}$ could be comparable

$$\frac{g_{m1}}{1 + g_{m1} \left(R_{EE} // \frac{R_S}{2} \right)}$$

$$\frac{g_{m1}}{1 + g_{m1} R_{EE}}$$

$$\frac{r_{out,TCA,d} // R_{up}}{r_{out,TCA,c} // R_{up}}$$

this ratio is smaller than 1

$(r_{out,TCA,d} < r_{out,TCA,c})$

see (*)


altogether

$$\frac{1 + g_{m1} R_{EE}}{1 + g_{m1} \frac{R_S}{2}} \gg 1$$

Generated by CamScanner (2)

BJT Differential Amplifier with Parasitics**Razavi 10.55**


55. Due to a manufacturing error, a parasitic resistance, R_P , has appeared in the circuit of Fig. 10.78. Calculate the voltage gain.

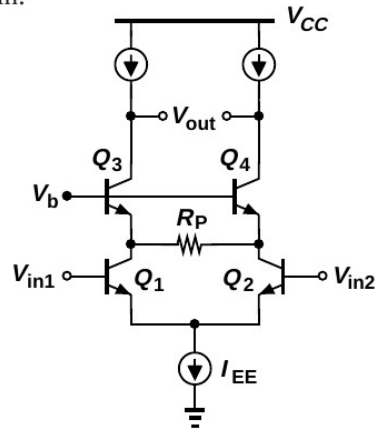**Figure 10.78**


Necessary Knowledge and Skills: BJT small signal analysis, differential mode half circuit analysis, voltage gain computation, virtual ground in differential mode

Study the common base amplifier
as a ~~transconductance~~ current
amplifier

Razavi
10.55

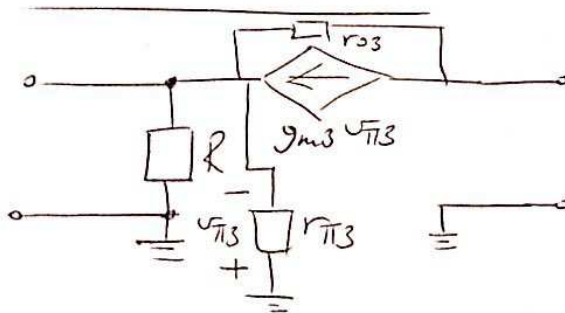

in large
signal

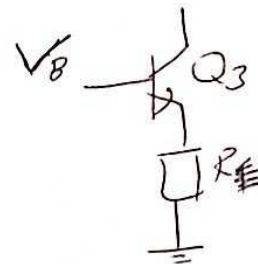

$r_{in, CB}$ computation

(connect v_t
at the input,
short the output)

$$-i_t + \frac{v_t}{R} + \frac{v_t}{r_{\pi 3}} + \frac{v_t}{r_{o3}} - g_{m3} v_{\pi 3} = 0$$

$$v_t = -v_{\pi 3}$$

$$\frac{v_t}{i_t} = r_{in, CB} = R \parallel r_{\pi 3} \parallel r_{o3} \parallel \frac{1}{g_{m3}}$$

$$\approx R \parallel \frac{1}{g_{m3}} \quad \left(\text{if } r_{\pi 3}, r_{o3} \text{ are very big} \right)$$

$$r_{out, CB} = (1 + g_{m3} r_{o3}) (r_{\pi 3} \parallel R) + r_{o3}$$

(see other answers and lecture notes for
the derivation)

A_{CA} computation (connect \bar{v}_{in} at the input, short the output)

Razavi
10.55
continued

$$-\bar{v}_{in} + \frac{v_{in}}{R} + \frac{v_{in}}{r_{\pi 3}} - g_{m3} v_{\pi 3} + \frac{v_{in}}{r_{o3}} = 0$$

$$\bar{v}_{out} + g_{m3} v_{\pi 3} - \frac{v_{in}}{r_{o3}} = 0$$

$$v_{\pi 3} = -v_{in}$$

$$\frac{v_{in}}{R \parallel r_{\pi 3} \parallel r_{o3} \parallel \frac{1}{g_{m3}}} = \bar{v}_{in}$$

$$\bar{v}_{out} = \frac{v_{in}}{\frac{1}{g_{m3}} \parallel r_{o3}}$$


$$A_{CA} = \frac{\bar{v}_{out}}{\bar{v}_{in}} \approx \frac{R \parallel \frac{1}{g_{m3}}}{\frac{1}{g_{m3}}}$$

(if $r_{\pi 3}$ and r_{o3} are very big)

$$= \frac{R \cdot \frac{1}{g_{m3}}}{R + \frac{1}{g_{m3}}}$$


$$= \frac{g_{m3} R}{1 + g_{m3} R} < 1$$

Differential mode
half cir

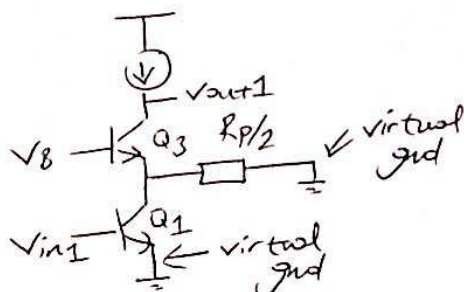

transconductance $\Rightarrow -g_{m1}$
of Q_1
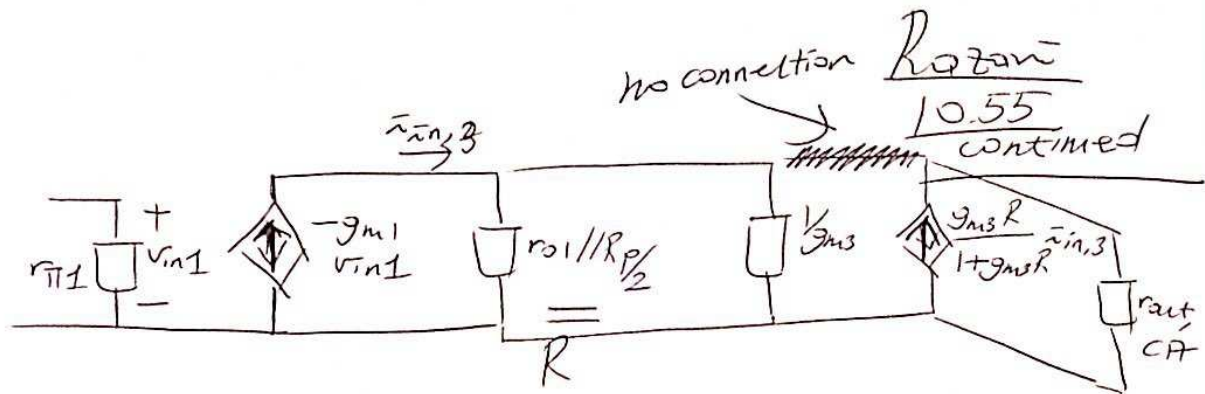
$$R(\text{as in the deriv. above}) = r_{o1} \parallel \frac{R_P}{2}$$



Transconductance of the whole ampl. (cascaded TCA and CA)

$$G = -g_{m1} \frac{g_{m3} R}{1 + g_{m3} R}$$

$$R_{out} = R_{out, CA}$$

then voltage gain of diff mode = $\frac{V_{out,1}}{V_{in,1}} = G R_{out}$

$$= -g_{m1} \frac{g_{m3} [r_{o1} \parallel \frac{R_p}{2}]}{1 + g_{m3} [r_{o1} \parallel \frac{R_p}{2}]} \left[(1 + g_{m3} r_{o3}) (r_{\pi 3} \parallel r_{o1} \parallel \frac{R_p}{2}) + r_{o3} \right]$$

Smaller than would be if $R_p = +\infty$
it were that

note that $\frac{R_p}{2} \ll r_{o1}$
and in any case
the whole expr $< \frac{g_{m3} r_{o1}}{1 + g_{m3} r_{o1}}$

with $\frac{R_p \ll r_{o1}}{2}$
can replace with $\frac{R_p}{2}$

Generated by CamScanner

MOS Diff. Amp. (Mismatch)

Sedra 7.14

7.14 A design error has resulted in a gross mismatch in the circuit of Fig. P7.14. Specifically, Q_2 has twice the W/L ratio of Q_1 . If v_{id} is a small sine-wave signal, find:

- I_{D1} and I_{D2} .
- V_{OV} for each of Q_1 and Q_2 .
- The differential gain A_d in terms of R_D , I , and V_{OV} .

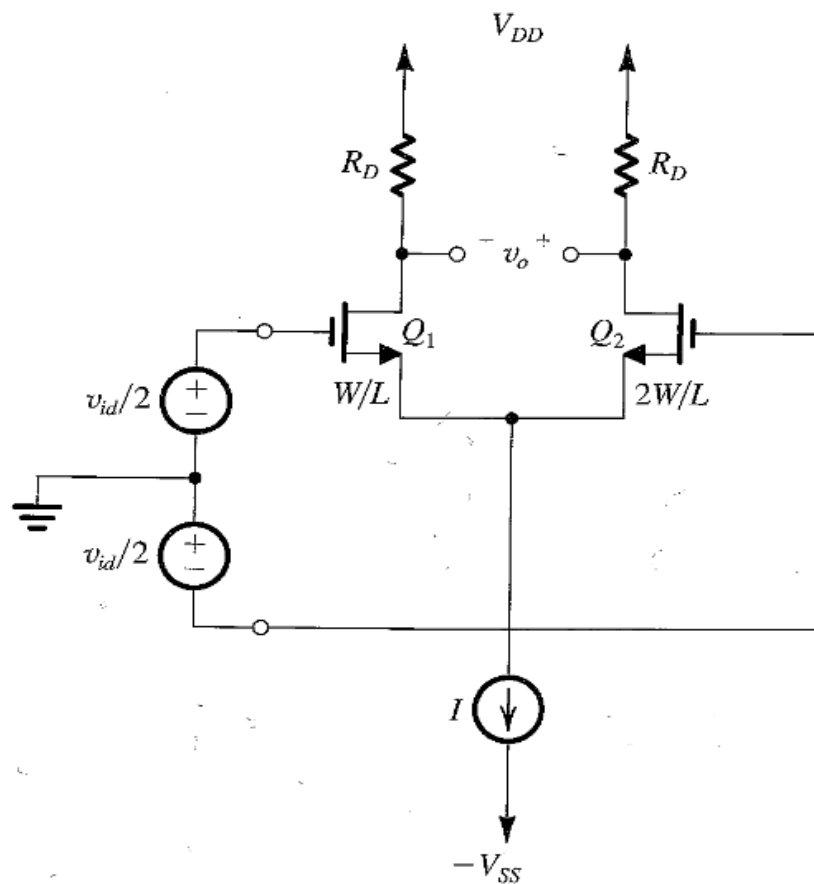


FIGURE P7.14

Necessary Knowledge and Skills: MOS differential, transistor mismatch, differential gain computation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

Sedra
7.14

$$\text{in DC} \Rightarrow V_{G1} = V_{G2} = 0V$$

$$V_{S1} - V_{S2} = V_S \text{ (common)}$$

$$I = I_{D1} + I_{D2}$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0 - V_S - V_T)^2$$

$$+ \frac{1}{2} \mu_n C_{ox} \frac{2W}{L} (0 - V_S - V_T)^2$$

$$= \frac{3}{2} \mu_n C_{ox} \frac{W}{L} (-V_S - V_T)^2$$

$$\Rightarrow I_{D1} = \frac{I}{3} \quad I_{D2} = \frac{2I}{3}$$

$$\left. \begin{array}{l} V_{OV1} = V_{GS1} - V_T \\ V_{OV2} = V_{GS2} - V_T \end{array} \right\} \begin{array}{l} V_{OV} = \sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}} \\ \text{(the same)} \end{array}$$

$$\text{formula for } g_m = \frac{2I_D}{V_{OV}}$$

$$g_{m1} = \frac{2I}{3 \sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}}}$$

$$= \frac{2I}{3V_{OV}}$$

$$g_{m2} = \frac{2 \cdot 2I}{3 \sqrt{\frac{2I}{3\mu_n C_{ox} \frac{W}{L}}}}$$

$$= \frac{4I}{3V_{OV}}$$

Generated by CamScanner

Note that virtual gnd in transistor mismatch is questionable \Rightarrow needs further analysis cont. Sedra
7.14

Accept for now that virt. gnd exists.

$$\left. \begin{aligned} v_{o1} &= -g_{m1} v_{d/2} R_D \\ v_{o2} &= -g_{m2} \left(-\frac{v_d}{2}\right) R_D \end{aligned} \right\}$$


$$\frac{v_{o2} - v_{o1}}{\frac{v_d}{2} - \left(-\frac{v_d}{2}\right)} = \frac{1}{v_d} \left[\frac{4I}{3V_{OV}} \frac{1}{2} v_d R_D - \left(-\frac{2I}{3V_{OV}} \frac{1}{2} v_d R_D \right) \right]$$

$$= \frac{1}{v_d} \frac{1}{2} v_d R_D \frac{I}{V_{OV}} \left(\frac{4}{3} + \frac{2}{3} \right)$$

$$\text{Diff mode gain} = \frac{I R_D}{V_{OV}}$$

BJT Differential Amp. With Current Source**Rashid 9.39**

9.39 A differential amplifier is shown in Fig. P9.39. The transistors are identical. Assume $V_{BE} = 0.7$ V, $V_T = 26$ mV, $\beta_F = 50$, and $V_A = 40$ V. Calculate the values of A_d , R_{id} , A_c , R_{ic} , and CMRR.

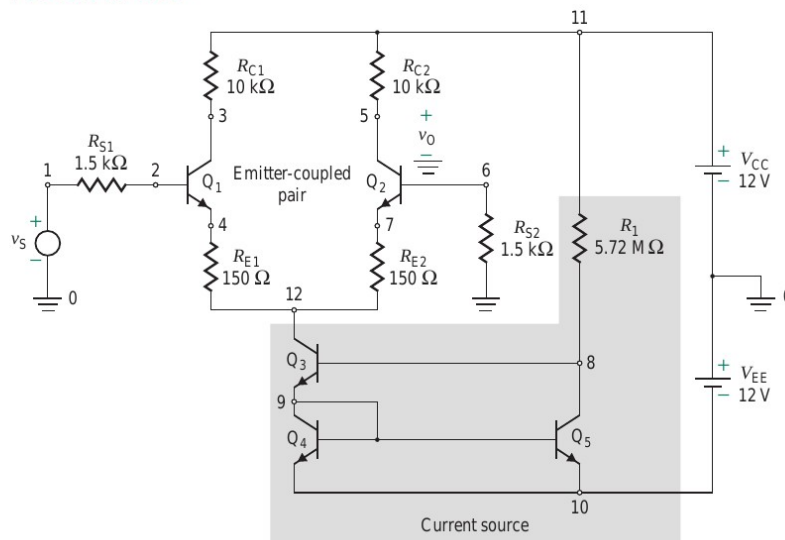P**FIGURE P9.39**

Necessary Knowledge and Skills: Current source output current and impedance computation, BJT differential pair, BJT small signal analysis, common/differential mode half circuit analysis, voltage gain computations in common/differential modes, CMRR calculation

Calculate the tail current

Rashid
9.39

$$V_{11} = 12 \text{ V}$$

$$V_{10} = -12 \text{ V}$$


$$V_8 = -V_{10} + V_{BE4} + V_{BE3}$$

$$= -12 + 0.7 + 0.7$$

$$= -10.6 \text{ V}$$

$$\frac{V_{11} - V_8}{R_1 = 5.72 \text{ m}\Omega} = I_{\text{ref}} \approx I_{\text{tail}}$$

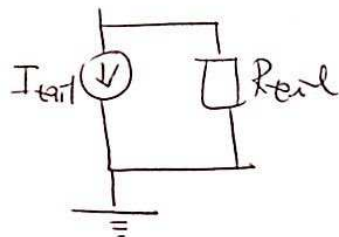The current can as usual be modeled as soln of the problem




See Rashid 9.31
for the calculation of R_{tail}

$$R_{\text{tail}} \approx r_{o3} \left(1 + \frac{\beta_2}{2} \right) \rightarrow \text{given}$$

$$\frac{V_A}{I_{\text{tail}}}$$

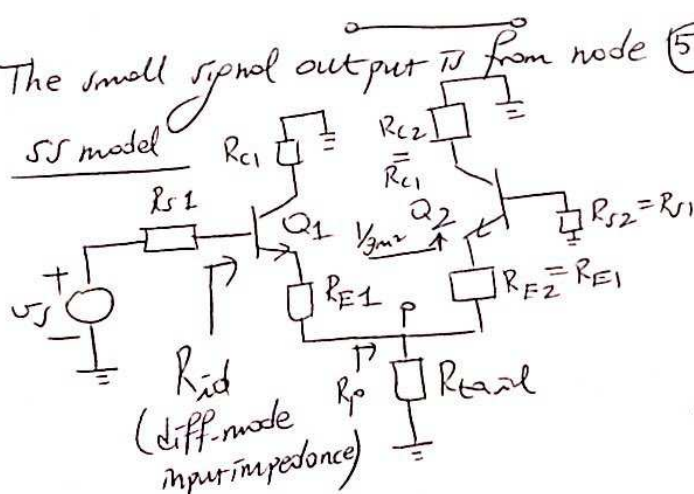The small signal output is from node (5) to the gnd.



Let $R_C = R_{C1} = R_{C2}$
 $R_E = R_{E1} = R_{E2}$
 $R_S = R_{S1} = R_{S2}$

$$g_m = g_{m1} = g_{m2}$$

$$g_m = \frac{I_C}{V_T} = \frac{I_{\text{tail}}/2}{26 \text{ mV}}$$

$$= \frac{I_{\text{tail}}}{52 \text{ mV}}$$

Generated by CamScanner

R_p at node P (\rightarrow)

Resist
9.39
Cont.

$$R_p = R_{out} // [R_E + 1/g_m]$$


$$R_{in} \approx [1 + g_m (R_E + R_p)] r_{\pi 1} \quad \left(\begin{array}{l} \text{make use of} \\ \text{TCA related} \\ \text{deriv.} \end{array} \right)$$

The amplifier in diff. mode can be analyzed as a cascade of two amplifiers:

emitter follower	+	Common base
$\frac{v_{e1}}{v_{b1}} = \frac{R_E + R_p}{R_E + R_p + 1/g_m} \quad \left(\begin{array}{l} \text{see} \\ \text{emitter} \\ \text{follower} \\ \text{related} \\ \text{deriv.} \end{array} \right)$ $\frac{v_{b1}}{v_s} = \frac{R_{in}}{R_s + R_{in}} \quad \left(\begin{array}{l} \text{voltage} \\ \text{divider} \end{array} \right)$ $\frac{v_p}{v_{e1}} = \frac{R_p}{R_p + R_E} \quad \left(\begin{array}{l} \text{voltage} \\ \text{divider} \end{array} \right)$ $\frac{v_{e2}}{v_p} = \frac{1/g_m}{1/g_m + R_E} \quad \left(\begin{array}{l} \text{voltage} \\ \text{divider} \end{array} \right)$		$\frac{v_s}{v_{e2}} = \frac{v_{c2}}{v_{e2}} \approx g_m R_c$ <p>(see related derivations)</p>

$$A_d = \frac{v_{c2}}{v_s} = \frac{v_{b1}}{v_s} \cdot \frac{v_{e1}}{v_{b1}} \cdot \frac{v_p}{v_{e1}} \cdot \frac{v_{e2}}{v_p} \cdot \frac{v_{c2}}{v_{e2}}$$

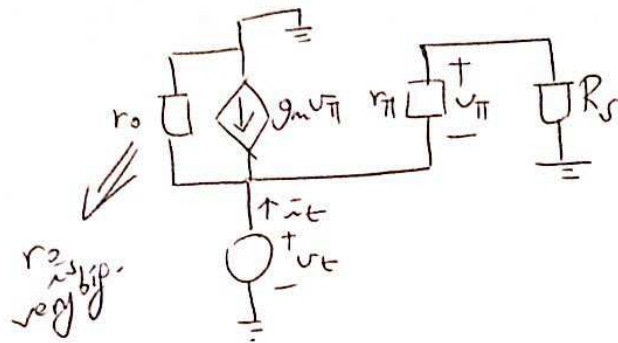\Rightarrow multiply the related terms given above




Common
base
input imp.

Rashed
9-39
Cont

$$\left. \begin{aligned} -g_m v_{\pi} - \tilde{v}_t + \frac{v_t}{r_{\pi} + R_S} &= 0 \\ v_t \frac{r_{\pi}}{r_{\pi} + R_S} &= -v_{\pi} \end{aligned} \right\}$$

$$v_t \left(\frac{1 + g_m r_{\pi}}{r_{\pi} + R_S} \right) = \tilde{v}_t$$
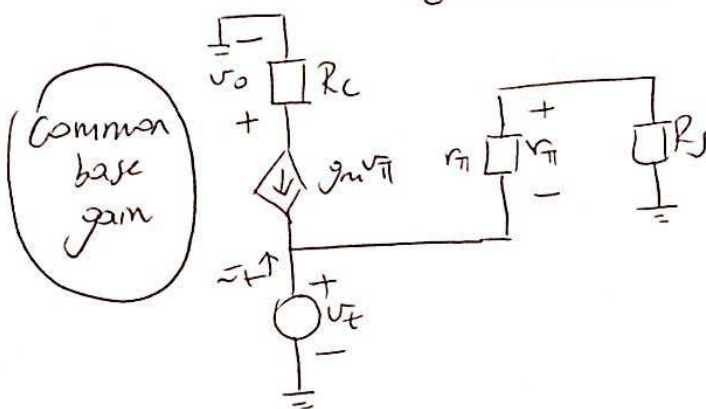
$$\frac{v_t}{\tilde{v}_t} = \frac{r_{\pi} + R_S}{1 + \beta} \approx \frac{1}{g_m} \quad \text{if } r_{\pi} \gg R_S$$



Common
base
gain

$$v_o = -g_m v_{\pi} R_C$$


$$v_o = -g_m R_C \left(-v_t \frac{r_{\pi}}{r_{\pi} + R_S} \right)$$

$$\frac{v_o}{v_t} = g_m R_C \frac{r_{\pi}}{r_{\pi} + R_S}$$

$$\approx g_m R_C \quad \text{if } r_{\pi} \gg R_S$$

Above are better approx in the analysis
of the common base stage (when R_S is nontrivially big
compared to r_{π})

Common mode half cir

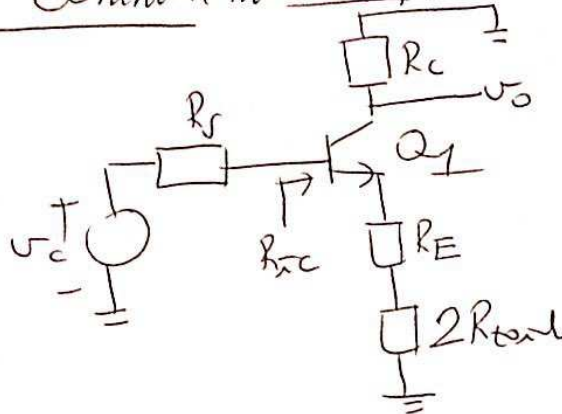

Required
9.39
Cont.

$$A_c = \frac{v_o}{v_c} = \frac{v_{b1}}{v_c} \frac{v_o}{v_{b1}}$$

$$= \frac{R_{\pi c}}{R_{\pi c} + R_s} \left[-g_m \frac{1}{1 + g_m (R_E + 2R_{tail})} \right] \left(R_C \parallel r_{out, TCH} \right)$$

generally $R_C \ll r_{out, TCH}$
 \uparrow

(see TCH related computations)

$$R_{\pi c} \approx \left[1 + g_m (R_E + 2R_{tail}) \right] r_{\pi}$$

$$r_{out, TCH} \approx \left[1 + g_m (R_E + 2R_{tail}) \right] r_o$$

Then $CMRR = \left| \frac{A_d}{A_c} \right|$ (Substitute all the terms and calculate)

