



GYTE
Electronics Engineering

ELEC 331
Electronic Circuits 2

Fall 2014

Instructor: Assist. Prof. Önder Şuvak

HW 14
Questions and Answers

Updated January 4, 2015 - 01:12

Assigned: 20141222

Due: 20141229

Answers Out: 20141230

Late Due: 20150105

Contents

Title Page	1
Contents	1
Question 1	2
Question	2
Solution	3
Question 2	5
Question	5
Solution	6
Question 3	9
Question	9
Solution	10
Question 4	12
Question	12
Solution	14
Question 5	30
Question	30
Solution	31

BJT Current Source

Sedra 6.144

D6.144 (a) For the circuit in Fig. P6.144, assume BJTs with high β and $v_{BE} = 0.7$ V at 1 mA. Find the value of R that will result in $I_O = 10$ μ A.

(b) For the design in (a), find R_o assuming $\beta = 100$ and $V_A = 100$ V.

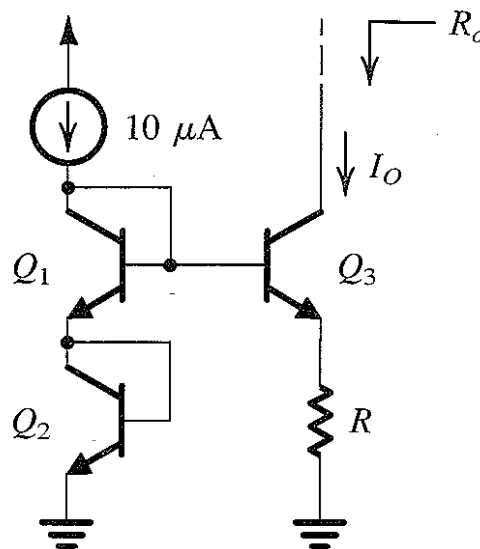


FIGURE P6.144

Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: Current source, current reference, finite beta effect, output impedance, design question.

Prob 6.144

$$I_{C1} = I_S \exp\left(\frac{V_{BE1}}{V_T}\right)$$

$$I_{C2} = I_S \exp\left(\frac{V_{BE2}}{V_T}\right)$$

$$I_{C3} = I_S \exp\left(\frac{V_{BE3}}{V_T}\right)$$

$$I_{C1} = I_{C2} = 10 \mu A \quad a)$$

$$I_{C3} = 10 \mu A$$

$I_S \Rightarrow$ the same for Q_1 and Q_2 and Q_3

$V_T \Rightarrow$ the same for all

then

$$V_{BE1} = V_{BE2} = V_{BE3} = V_{BE}$$

$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$

these calculation apply for

$$0.7 V = 25 mV \ln \frac{1 mA}{I_S} \Rightarrow \text{compute } I_S$$

$$(V_{BE}, I_C) = (0.7 V, 1 mA)$$

$$I_S = \frac{1 mA}{\exp\left(\frac{0.7 V}{25 mV}\right)}$$

then

$$V_{BE} = 25 mV \ln \frac{10 \mu A}{I_S}$$

for $I_C = 10 \mu A$

plug in this I_S


compute!

Note that $R I_O = V_{BE2}$ since

$$R = \frac{V_{BE2}}{I_O} = \frac{V_{BE2}}{10 \mu A}$$

$$V_{BE2} + \cancel{V_{BE1}} - \cancel{V_{BE3}} - R I_O = 0$$

there are the same, see above.

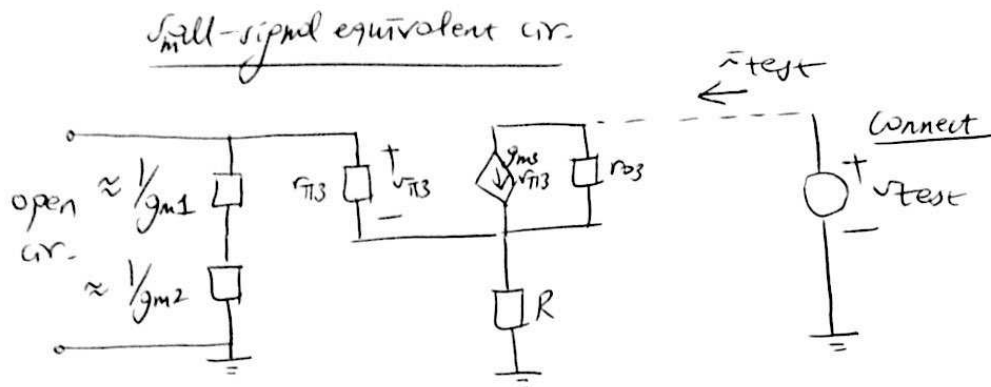Sedra 6.144
cont.

$$r_{\pi 3} \gg \frac{1}{g_{m1}} + \frac{1}{g_{m2}}$$

$$R_o \approx \frac{v_{test}}{\bar{i}_{test}} = (1 + g_{m3} r_{o3}) (R // r_{\pi 3}) + r_{o3}$$

Note that

$$r_{o3} = \frac{V_A}{I_{C3}} = \frac{100V}{10\mu A} = \frac{100}{10 \times 10^{-6}} = 10 M\Omega$$

$$g_{m3} = \frac{I_{C3}}{V_T} = \frac{10\mu A}{25mV} = \frac{10 \times 10^{-6}}{25 \times 10^{-3}} = 0.4 \times 10^{-3} S = 0.4 mS$$

$$r_{\pi 3} = \frac{\beta}{g_{m3}} = \frac{250}{0.4 \times 10^{-3} S} = 250 K\Omega$$

$R \Rightarrow$ computed in part (a)

then compute R_o !

BJT Differential Amplifier

Sedra 7.41

7.41 For the differential amplifier shown in Fig. P7.41, identify and sketch the differential half-circuit and the common-mode half-circuit. Find the differential gain, the differential input resistance, the common-mode gain, and the common-mode input resistance. For these transistors, $\beta = 100$ and $V_A = 100$ V.

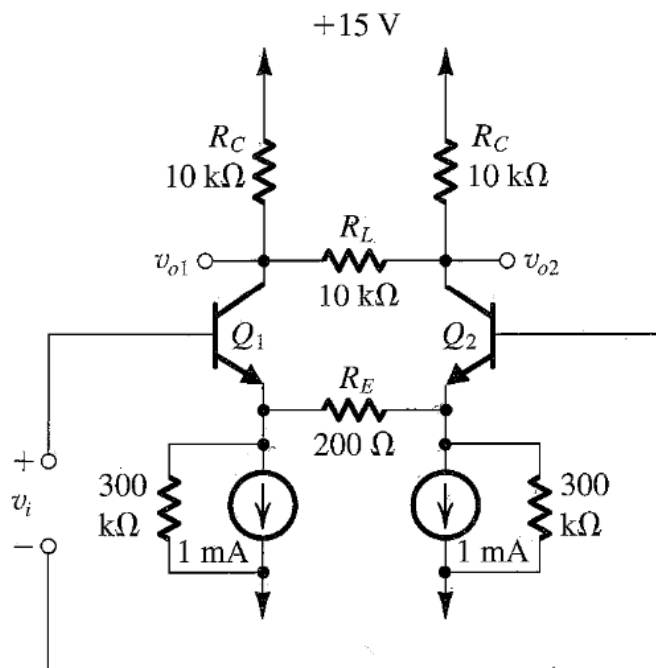


FIGURE P7.41

Notes: None.

Additional Tasks: Solve the following problem applied to the given circuit.

(d) If $v_{B1} = 0.1 \sin 2\pi \times 60t + 0.005 \sin 2\pi \times 1000t$ volts, $v_{B2} = 0.1 \sin 2\pi \times 60t - 0.005 \sin 2\pi \times 1000t$, volts, find v_o .


Necessary Knowledge and Skills: BJT symmetrical differential amplifier, common and differential mode gain, input impedances, CMRR.

Sedra 7.41DC analysiswhen $v_{in} = 0$ (no differential input) \Rightarrow No current over R_L and R_E $\Rightarrow I_{C1} = I_{C2} \approx 1 \text{ mA}$ \Rightarrow small signal parameter (applies to Q_1 and Q_2)

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}} = 40 \text{ mS}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{40 \text{ mS}} = 2.5 \text{ k}\Omega$$


$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

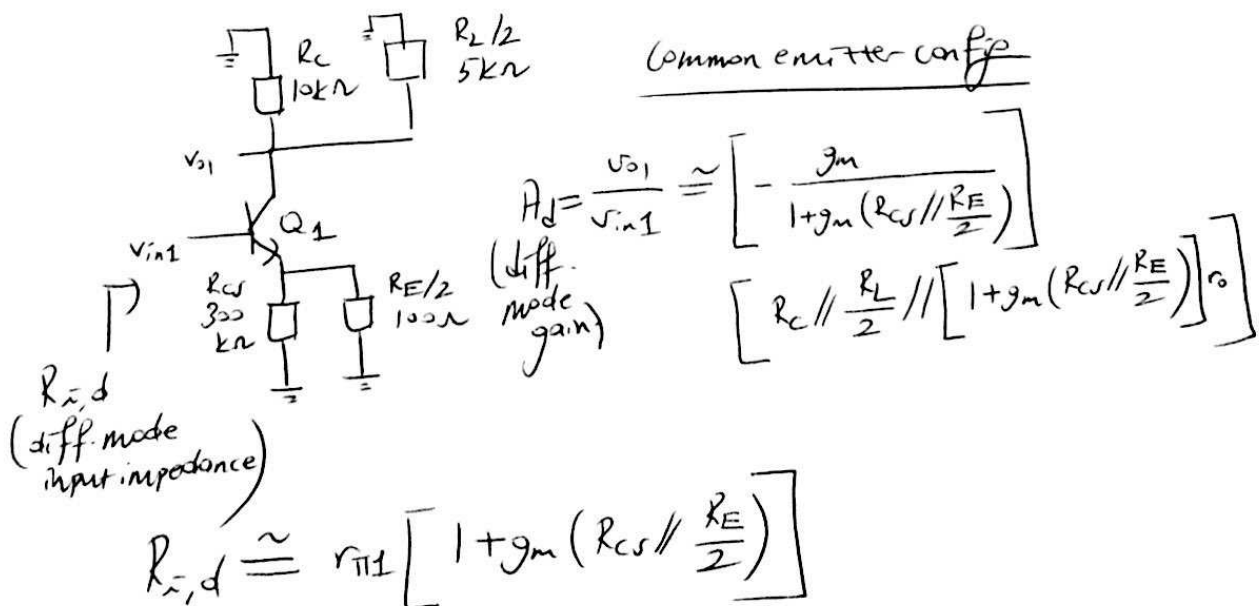Small signal analysisDiff mode half cir \Rightarrow In the middle of R_L and R_E we have virtual gnd.

Scanned by CamScanner

Common Mode Half Cir.Sedra 7.41
contin.

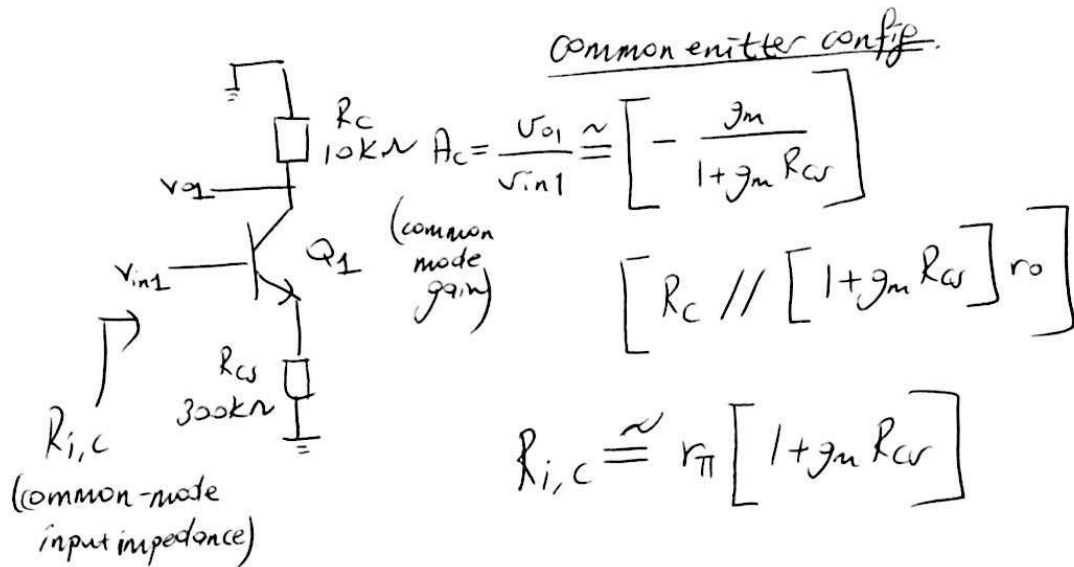With common mode input, there is no current over R_L or R_E .



$$CMRR = \left| \frac{A_d}{A_c} \right|$$

$$\left. \begin{aligned} v_{B1} &= v_c + \frac{v_d}{2} \\ v_{B2} &= v_c - \frac{v_d}{2} \end{aligned} \right\} \begin{aligned} v_c &= \frac{v_{B1} + v_{B2}}{2} = 0.1 \sin(2\pi \cdot 60t) \text{ V} \\ v_d &= v_{B1} - v_{B2} = 0.01 \sin(2\pi \cdot 1000t) \text{ V} \end{aligned}$$

Make use of superposition

⇒ Activate diff mode only



$$v_{o1} = A_d \frac{v_d}{2}$$

$$v_{o2} = -A_d \frac{v_d}{2}$$

⇒ Activate common mode only



$$v_{o1} = A_c v_c$$

$$v_{o2} = A_c v_c$$


Scanned by CamScanner (2)

By superposition

$$\Rightarrow v_{o1} = A_d \frac{v_d}{2} + A_c v_c$$

$$v_{o2} = -A_d \frac{v_d}{2} + A_c v_c$$

$$\Rightarrow v_{o1} - v_{o2} = A_d v_d$$

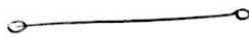

Sedra 7.41
contin-

} A_d
 A_c computed
above

Practical Feedback Circuits

Malik 9.29

9.29 For each circuit of Fig. P9.29, identify the type of feedback and find the numerical value of β using the appropriate two-port parameter of the feedback circuit. State whether the feedback is dc or ac. If both, find the two-port parameter values for both.

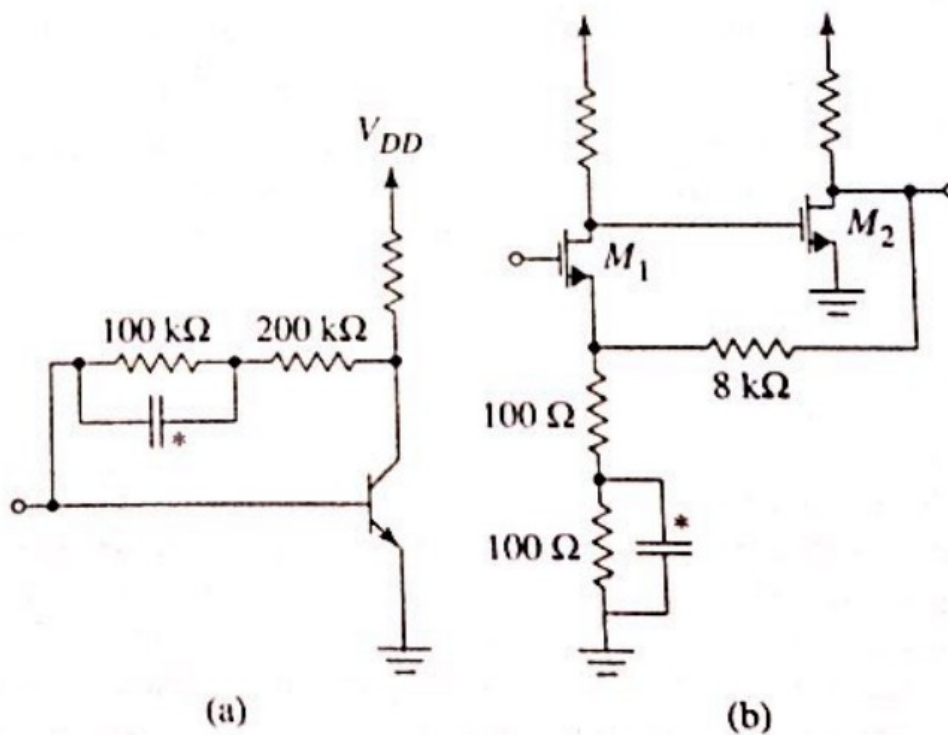


Figure P9.29

Notes: None.


Additional Tasks: Do full analyses of the feedback circuits in small signal.

Necessary Knowledge and Skills: Type of feedback determination, distinguishing ac/dc feedback, two-port parameters of feedback networks.


Matk 9.29

Feedback is both AC and DC in each of the circuits given.

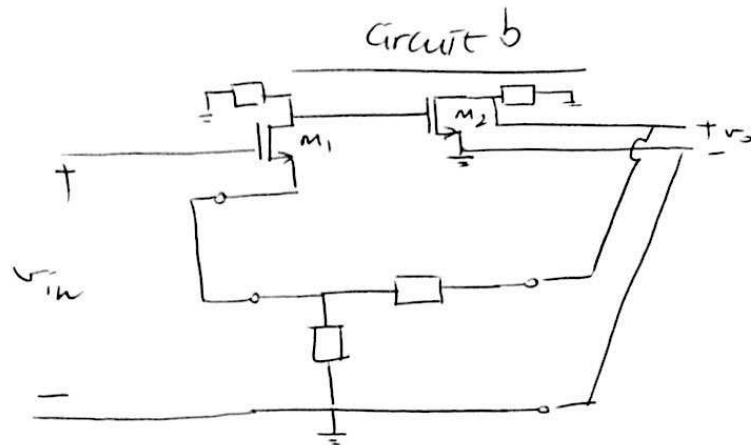Voltage-series feedback for a voltage amplifier



Two port parameters

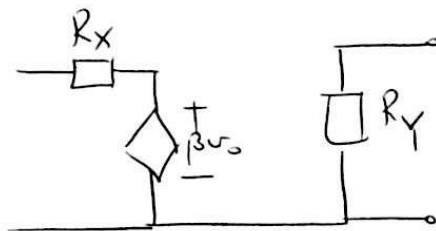

in ac feedback

$$\beta = \frac{100}{8k} = \frac{1}{80}$$

$$R_X = 100\Omega // 8k\Omega$$

$$R_Y = 8.1k\Omega$$

in dc feedback

$$\beta = \frac{100+100}{8k} = \frac{1}{40}$$


$$R_X = (100+100)\Omega // 8k\Omega$$

$$R_Y = 8.2k\Omega$$


Mod 9.29

contin.

Circuit a

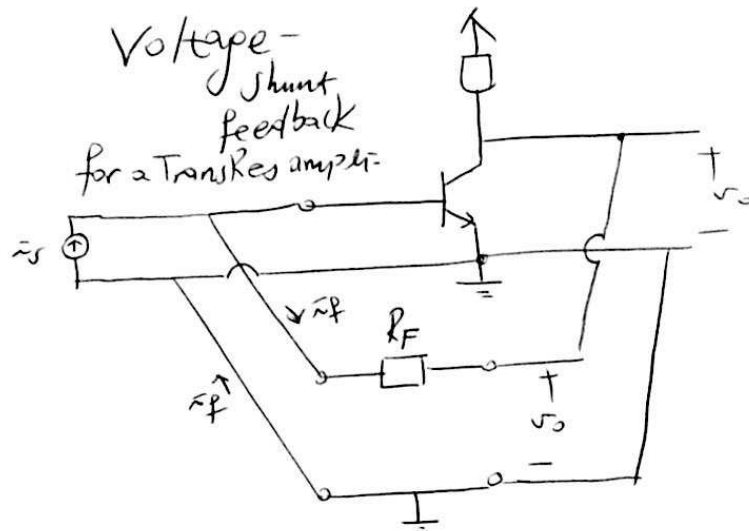

Feedback network model

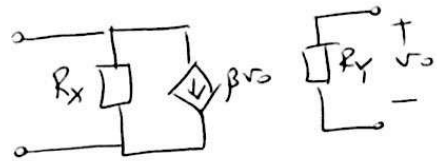

Two port parameters (see related)

Formula	ac feedback	dc feedback
$\beta = -\frac{1}{R_F}$	$-\frac{1}{200k\Omega}$	$-\frac{1}{300k\Omega}$
$R_X = R_F$	$200k\Omega$	$300k\Omega$
$R_Y = R_F$	$200k\Omega$	$300k\Omega$

Scanned by CamScanner

2

CMOS Basic Op-Amp

Rashid 14.19

14.19 The CMOS amplifier in Fig. 14.20 is operated at a biasing current of $I_Q = 50 \mu\text{A}$. The parameters of the MOSFETs are $K_x = 10 \mu\text{A}/\text{V}^2$, $|V_{M(\text{NMOS})}| = V_{M(\text{PMOS})} = 60 \text{ V}$, $V_t = 1 \text{ V}$, and $W/L = 80 \mu\text{m}/10 \mu\text{m}$, except for Q_7 , for which $W/L = 160 \mu\text{m}/10 \mu\text{m}$. Assume $V_{DD} = V_{SS} = 5 \text{ V}$.

D

- Find V_{GS} , g_m , and r_o for all MOSFETs.
- Find the low-frequency voltage gain of the amplifier A_{vO} .
- Find the value of the external resistance R_{ref} .
- Find the value of compensation capacitance C_x that gives a unity-gain bandwidth of 1 MHz and the corresponding slew rate.
- Find the value of resistance R_x to be connected in series with C_x in order to move the zero frequency to infinity.
- Find the common-mode input voltage range.
- Find the output voltage range.

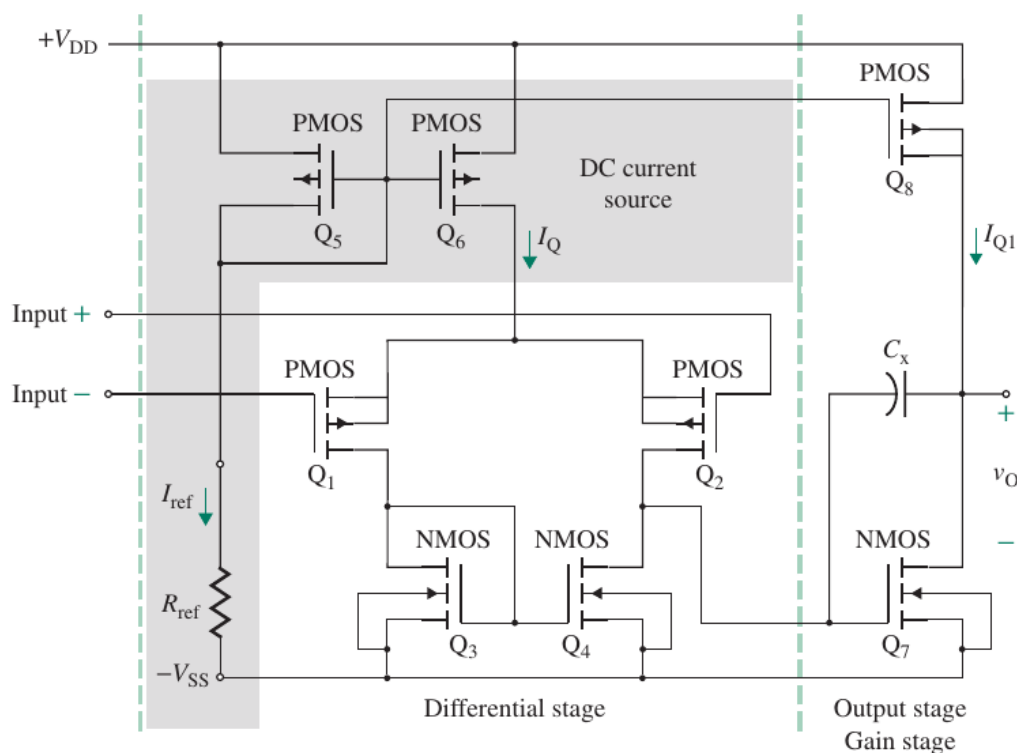


FIGURE 14.20 Schematic for op-amp MC14573 (Copyright of Motorola. Used by permission.)

CMOS Basic Op-Amp

Rashid 14.19

Notes: See Rashid Section 14.4.2 for a similar example.

Additional Tasks: Point out the errors in the schematic.

Necessary Knowledge and Skills: CMOS basic OpAmp, voltage gain, slew rate, Miller effect, MOS current source, unity-gain bandwidth, gain-bandwidth product, voltage ranges to keep transistors in saturation.

Rashid
14-19

Errors in the schematic

→ Bulks of Q_5 and Q_6 should be connected to $+V_{DD}$
PMOS transistors

→ The Bulk of Q_p should be connected to $+V_{DD}$
PMOS transistor

Systematic DC offset cancellation

See Sedra & Smith section 7.7-1 (or the answer to Sedra & Smith 9-2)

$$2 \frac{\left(\frac{W}{L}\right)_8}{\left(\frac{W}{L}\right)_6} = \frac{\left(\frac{W}{L}\right)_7}{\left(\frac{W}{L}\right)_4} \quad \text{which holds for the op-amp in this question.}$$

DC currents $\Rightarrow I_{D5} = I_{D6} = I_Q = I_{ref} = 50 \mu A$ part (a)
 since $\left(\frac{W}{L}\right)$ ratios for Q_5 and Q_6 are the same.

$$\Rightarrow I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I_Q}{2} = 25 \mu A$$

$$\Rightarrow I_{D8} = I_{D7} = I_Q = 50 \mu A$$

since Q_6 and Q_8 have the same $\left(\frac{W}{L}\right)$ ratio.

Prashant
14.19
contin-

The formula for the Drain current

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \text{ for NMOS}$$

part (a)
continued

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_t|)^2 \text{ for PMOS}$$

It is given in the question that

$$K_x = \frac{1}{2} \mu_n C_{ox} = \frac{1}{2} \mu_p C_{ox} = 10 \mu A/V^2$$

We have the I_D and $\frac{W}{L}$ for each transistor

\Rightarrow Calculate numerically $(V_{GS} - V_t)$ or $V_{SG} - |V_t|$ for each transistor

\Rightarrow Calculate V_{GS} or V_{SG} for each transistor

$\Rightarrow r_o = \frac{|V_m|}{I_D}$ $|V_m| = 60V$ compute r_o for each transistor

$$\begin{aligned} \Rightarrow g_m &= \frac{\partial I_D}{\partial V_{GS}} = 2 K_x \frac{W}{L} (V_{GS} - V_t) \\ &= \frac{2 I_D}{V_{GS} - V_t} \left(\text{or } \frac{2 I_D}{V_{SG} - |V_t|} \right) \\ &\quad \text{for PMOS} \end{aligned}$$

Calculate g_m numerically for each transistor

Since M_1 and M_2 are identical
 $(Q_1) \quad (Q_2)$
 and biased with the same current:

$$g_{m1} = g_{m2}$$

\Rightarrow gain of the differential stage

$$\frac{v_{g7}}{v_{in,+} - v_{in,-}} \approx -g_{m1} (r_{o2} \parallel r_{o4})$$

(see the
derivation
for a diff amp
with current mirror
active load)

\Rightarrow gain of the common source stage

$$\frac{v_{d7}}{v_{g7}} \approx -g_{m7} (r_{o3} \parallel r_{o7})$$

$$\Rightarrow A_{Vo} = \frac{v_{g7}}{v_{in,+} - v_{in,-}} \cdot \frac{v_{d7}}{v_{g7}}$$

calculate
numerically

(KVL)

$$V_{DD} - V_{SG,5} - I_{ref} R_{ref} = -V_{SS}$$


part (c)

$$V_{DD} = V_{SS} = 5V$$

$V_{SG,5}$ computed in part (a)

$I_{ref} = I_Q = 50 \mu A$ ($(\frac{W}{L})$ ratios of Q_5 and Q_6
are the same)


\Rightarrow Compute R_{ref} .

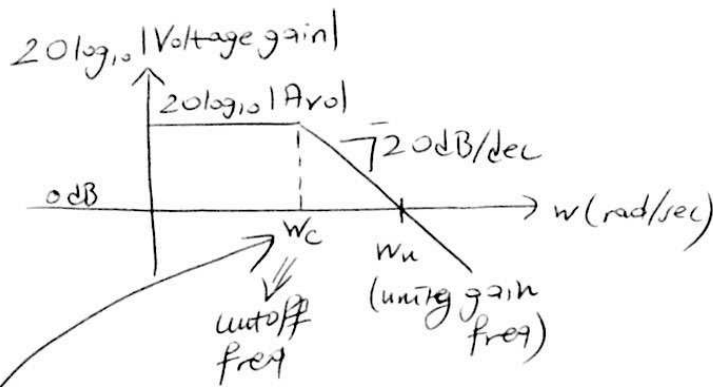

Rashed
14-19
Continued
part (d)

See the derivations to confirm : $A_{V0} \cdot \omega_c = \omega_u$
 (for this single dominant pole system)

Use the Miller's thm to transform C_x

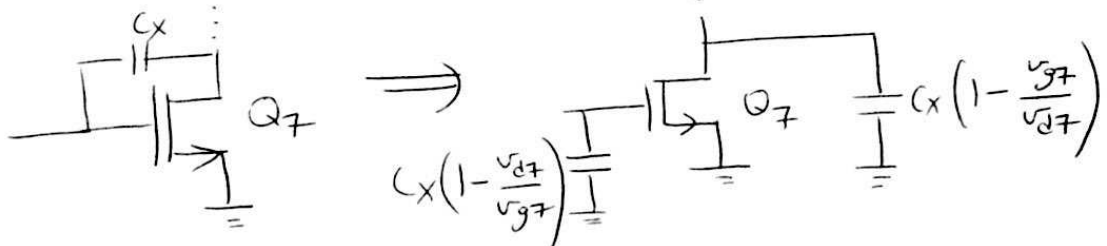

corresponds to
 the time constant
 that will dominate
 in the OCTC calculation
 for ω_c

Now use the
 OCTC method:

$$\omega_c \approx \frac{1}{C_x \left(1 - \frac{v_{dt}}{v_{gt}}\right) \cdot (r_{o2} \parallel r_{o4})}$$

Thevenin Resistance
for this cap.

Scanned by CamScanner

4

$$w_u = 1 \text{ MHz (given)}$$

$$\frac{\text{Rashed}}{14-19}$$

part(d)
contin-

$$\approx A_{VO} w_c$$

$$= A_{VO} \frac{1}{C_X \left(1 - \frac{v_{d7}}{v_{g7}}\right) (r_{o2} // r_{o4})}$$

$$= g_{m1} (r_{o2} // r_{o4}) g_{m7} (r_{o8} // r_{o7}) \frac{1}{C_X (1 + g_{m7} (r_{o8} // r_{o7})) (r_{o2} // r_{o4})}$$

$$\approx g_{m1} (r_{o2} // r_{o4}) g_{m7} (r_{o8} // r_{o7}) \frac{1}{C_X g_{m7} (r_{o8} // r_{o7}) (r_{o2} // r_{o4})}$$

$$= \frac{g_{m1} \rightarrow \text{computed}}{C_X \rightarrow \text{compute numerically now}}$$

$$\text{New rate} = \frac{I_Q}{C_X} = \frac{50 \mu\text{A}}{C_X} \rightarrow \text{computed above}$$

(see the related
derivations)

Now
compute
the slew
rate.

Rashed
14.19
continued

$$V_{SD6} \geq V_{SG6} - |V_t|$$

for Q_6 to remain in saturation. part (f)

$$V_{SG1} = V_{SG2} \text{ (identical transistors)}$$

then the maximum common-mode voltage

$$V_{CM,max} = \underset{\substack{\downarrow \\ \text{given}}}{V_{DD}} - \left[\underset{\substack{\downarrow \\ \text{see part (a)}}}{V_{SG6}} - \underset{\substack{\downarrow \\ \text{given}}}{|V_t|} \right] - \underset{\substack{\downarrow \\ \text{see part (a)}}}{V_{SG1}}$$

$$V_{SD1} \geq V_{SG1} - |V_t| \quad \text{for } Q_1 \text{ to remain in saturation}$$

$$|V_t| \geq V_{SG1} - V_{SD1} = V_{DG1}$$

$$V_{GD1} \geq -|V_t|$$

$$V_{G1} - V_{D1} \geq -|V_t|$$

$$V_{G1} \geq -|V_t| + V_{D1}$$

$$V_{G1} \geq \underset{\substack{\downarrow \\ \text{given}}}{-|V_t|} + \underset{\substack{\downarrow \\ \text{given}}}{-V_{SS}} + \underset{\substack{\downarrow \\ \text{see part (a)}}}{V_{GS3}}$$

then the minimum common-mode voltage

$$V_{CM,min} = -|V_t| - V_{SS} + V_{GS3}$$

Scanned by CamScanner

⑥

$$V_{SD,8} \geq V_{SG,8} - |V_t|$$

for Q_8 to remain
in saturation part (g)

Rashed
14-19
contin.

$$V_{DS,7} \geq V_{GS,7} - V_t \text{ for}$$

Q_7 to remain
in saturation

$$V_{O,max} = +V_{DD} - (V_{SG,8} - |V_t|)$$


$$V_{O,min} = -V_{SS} + (V_{GS,7} - V_t)$$

all the values ^{above} were given
or computed in part (a)

—————

See the discussion on pg 929-930 of Rashid.

Rashid
14.19
Continued
part e)

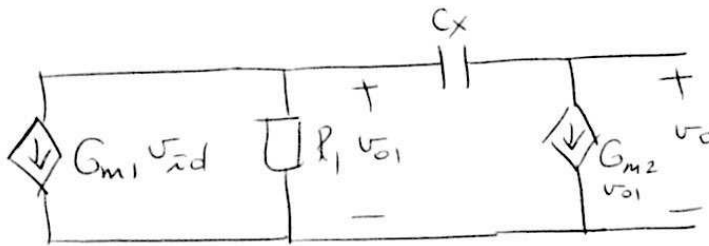

By KCL

$$G_{m2} v_{01} = (v_{01} - v_0) \omega C_x \quad \text{magnitude wise}$$

for ω_z we should have $v_0 = 0$


\Downarrow
zero location

$$G_{m2} v_{01} = v_{01} \omega_z C_x$$

$$\omega_z = \frac{G_{m2}}{C_x}$$

this freq
may be close to
the unity gain freq
and cause phase shift.

A remedy is:

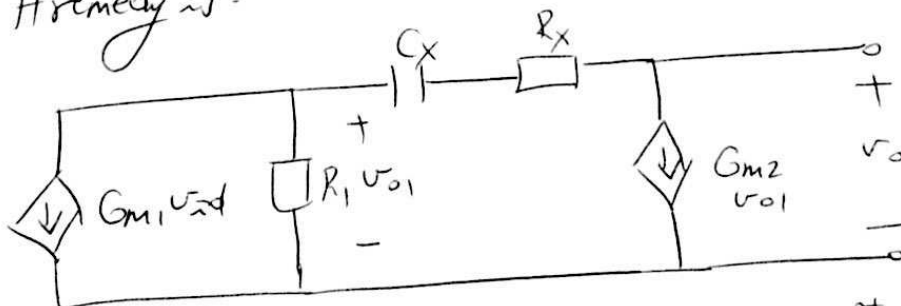

$$(By KCL) \quad G_{m2} v_{01} = \frac{v_{01} - v_0}{R_x + \frac{1}{j\omega C_x}}$$

again at ω_z
we have $v_0 \approx 0$

$$G_{m2} v_{01} = \frac{v_{01} j\omega_z C_x}{1 + j\omega_z R_x C_x}$$

$$G_{m2} + j\omega_z R_x C_x G_{m2} = j\omega_z C_x \Rightarrow G_{m2} + j\omega_z C_x (R_x G_{m2} - 1) = 0$$

Scanned by CamScanner

Then we obtain a term as

$$G_{m2} \left[1 + j \frac{\omega z}{C_X \left(R_X - \frac{1}{G_{m2}} \right)} \right]$$


The zero freq $\left[C_X \left(R_X - \frac{1}{G_{m2}} \right) \right]^{-1}$ is $\rightarrow \infty$

$$\text{if } R_X = \frac{1}{G_{m2}}$$

—————

Rashed
14-19
continued
 part (e)
contin.

Transfer function analysis

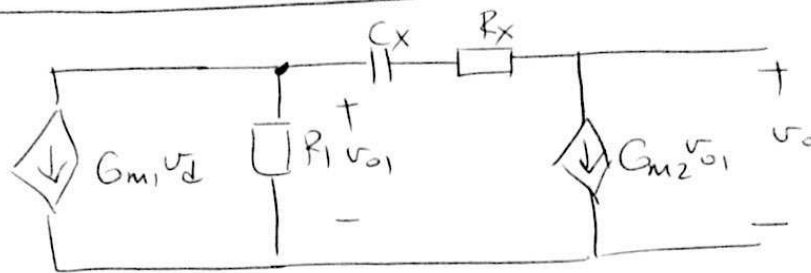

Ravind
14.19
Contin
part(e)
Contin

KCL

$$G_{M1} v_d + \frac{v_{o1}}{R_1} + \underbrace{\frac{v_{o1} - v_o}{Z_X}}_{G_{M2} v_{o1}} = 0$$

$$G_{M1} v_d + \frac{v_{o1}}{R_1 \parallel \frac{1}{G_{M2}}} = 0 \quad (*)$$

and we have

$$v_o = -G_{M2} v_{o1} [Z_X] + v_{o1}$$

$$= v_{o1} [1 - G_{M2} Z_X]$$

$$\frac{v_o}{v_d} = \frac{v_{o1}}{v_d} [1 - G_{M2} Z_X]$$

Compute $\frac{v_{o1}}{v_d}$ from (*)

$$\frac{v_{o1}}{v_d} = -G_{M1} \left[R_1 \parallel \frac{1}{G_{M2}} \right] = -G_{M1} \frac{R_1 \frac{1}{G_{M2}}}{R_1 + \frac{1}{G_{M2}}} = \frac{-G_{M1} R_1}{1 + G_{M2} R_1}$$

then

$$\frac{v_o}{v_d} = - \frac{G_{M1} R_1}{1 + G_{M2} R_1} [1 - G_{M2} Z_X]$$

Scanned by CamScanner

(10)

$$\begin{aligned}
 \frac{v_o}{v_d} &= - \frac{G_{m1} R_1}{1 + G_{m2} R_1} \left[1 - G_{m2} \left[R_x + \frac{1}{j\omega C_x} \right] \right] && \frac{\text{Rashed}}{14.19} \\
 &= \frac{G_{m1} R_1}{1 + G_{m2} R_1} \left[(G_{m2} R_x - 1) + \frac{G_{m2}}{j\omega C_x} \right] && \frac{\text{contin.}}{\text{part(e)}} \\
 &= \frac{G_{m1} R_1}{1 + G_{m2} R_1} \left[\frac{1 + j\omega C_x (R_x - \frac{1}{G_{m2}})}{j\omega C_x} \right] && G_{m2}
 \end{aligned}$$

The zero frequency ω_z above is clearly

$$\omega_z = \frac{1}{C_x \left(R_x - \frac{1}{G_{m2}} \right)}$$


and $R_x = \frac{1}{G_{m2}}$ will send $\omega_z \rightarrow +\infty$




A more insightful analysis of the circuit is through feedback concepts and some approximations.

Rashed
14-19
part (e)
continued

The opamp circuit can be modeled as in

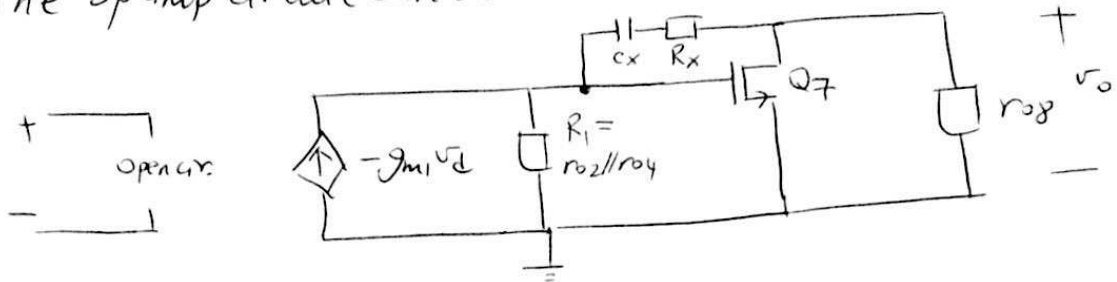

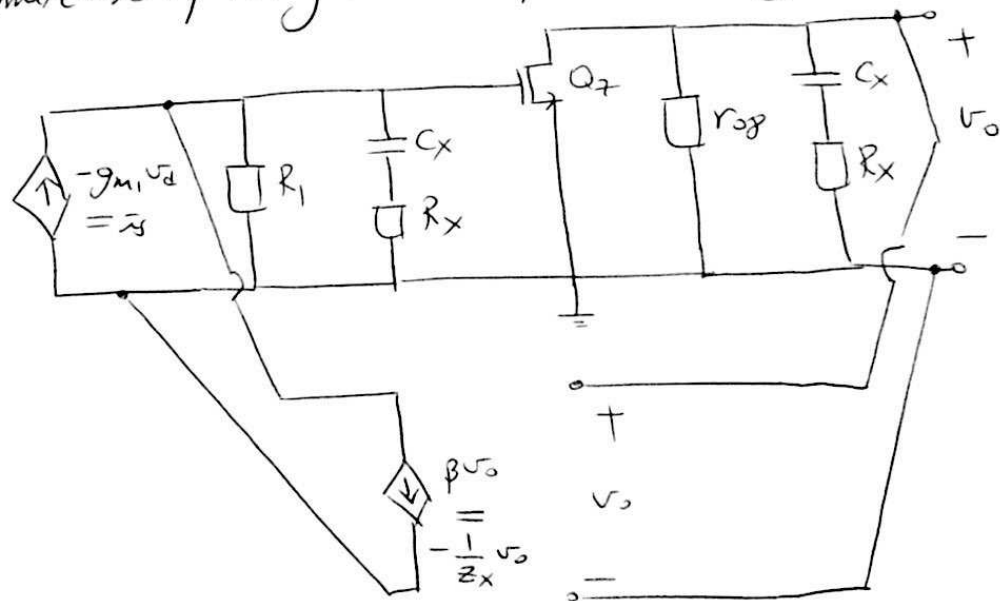Now make use of voltage-shunt feedback analysis.



where

$$Z_x = R_x + \frac{1}{j\omega C_x}$$

Now kill β and compute A_{TRA}
for the transresistance
amplifier.

Rashed
14-19
part (e)
continued

$$A_{TRA} = \frac{v_o}{\tilde{v}_s} = [R_1 \parallel Z_x] [-g_{m7}] [R_2 \parallel Z_x]$$

and compute the gain with feedback

$$\begin{aligned} A_F &= \frac{A_{TRA}}{1 + \beta A_{TRA}} = \frac{v_o}{\tilde{v}_s} \\ &= \frac{-g_{m7} [R_1 \parallel Z_x] [R_2 \parallel Z_x]}{1 + g_{m7} [R_1 \parallel Z_x] [R_2 \parallel Z_x] \frac{1}{Z_x}} \end{aligned}$$

Now recall that $\tilde{v}_s = -g_{m1} v_d$

$$\frac{v_o}{\tilde{v}_s} = \frac{v_o}{-g_{m1} v_d}$$

then the voltage gain of the opamp is

$$\frac{v_o}{v_d} = \frac{g_{m1} g_{m7} [R_1 \parallel Z_x] [R_2 \parallel Z_x]}{1 + g_{m7} [R_1 \parallel Z_x] [R_2 \parallel Z_x] \frac{1}{Z_x}}$$

play with the gain expression:

$$\frac{v_o}{v_d} = \frac{g_{m1} g_{m7} \frac{R_1 z_x}{R_1 + z_x} \frac{R_2 z_x}{R_2 + z_x}}{1 + g_{m7} \frac{R_1 z_x}{R_1 + z_x} \frac{R_2 z_x}{R_2 + z_x} \frac{1}{z_x}}$$

$$= \frac{g_{m1} g_{m7} R_1 R_2 z_x^2}{(R_1 + z_x)(R_2 + z_x) + g_{m7} R_1 R_2 z_x}$$

$$= \frac{g_{m1} g_{m7} R_1 R_2 z_x^2}{R_1 R_2 + z_x (R_1 + R_2 + g_{m7} R_1 R_2) + z_x^2}$$

Note that
 $g_{m7} R_1 R_2 \gg R_1 + R_2$

$$\approx \frac{g_{m1} g_{m7} R_1 R_2 z_x^2}{R_1 R_2 + z_x (g_{m7} R_1 R_2) + z_x^2}$$

Now compute the roots of the denom.

$$\text{roots} = \frac{-g_{m7} R_1 R_2 \pm \sqrt{(g_{m7} R_1 R_2)^2 - 4 R_1 R_2}}{2} \quad (**)$$

Note that $(g_{m7} R_1 R_2)^2 \gg 4 R_1 R_2$

approximate $\sqrt{(g_{m7} R_1 R_2)^2 - 4 R_1 R_2} \approx +g_{m7} R_1 R_2 - 2 r_{sm}$

For some small resistance r_{sm} .

Then the roots are

$$\text{root}_1 = -g_{m1} g_{m2} R_1 R_2 + r_{sm} \\ \approx -g_{m1} g_{m2} R_1 R_2$$

$$\text{root}_2 = -r_{sm}$$

The gain expression now becomes

$$\frac{v_o}{v_d} = \frac{g_{m1} g_{m2} R_1 R_2 z_x^2}{(z_x + r_{sm})(z_x + g_{m1} g_{m2} R_1 R_2)}$$

Recall that $z_x = R_x + \frac{1}{j\omega C_x}$

Then

$$\frac{z_x^2}{(z_x + r_{sm})(z_x + g_{m1} g_{m2} R_1 R_2)} = \frac{(1 + j\omega C_x R_x)^2}{[1 + j\omega C_x (R_x + r_{sm})][1 + j\omega C_x (R_x + g_{m1} g_{m2} R_1 R_2)]}$$

and we have

$$\frac{(1 + j\omega C_x R_x)^2}{1 + j\omega C_x (R_x + r_{sm})} \approx \frac{(1 + j\omega 2C_x R_x)(1 - j\omega C_x (R_x + r_{sm}))}{1 + \omega^2 [C_x (R_x + r_{sm})]^2}$$

depends on ω^2 , omit this

$$\approx \frac{1 + j\omega 2C_x R_x - j\omega C_x R_x - j\omega C_x r_{sm}}{1}$$

$$\approx 1 + j\omega C_x (R_x - r_{sm})$$

Then the gain expression becomes

$$\frac{v_o}{v_d} = \underbrace{g_{m1} g_{m7} R_1 R_2}_{\text{midband gain}} \frac{1 + j\omega C_x (R_x - r_{sm})}{1 + j\omega C_x (R_x + g_{m7} R_1 R_2)}$$

Rashid
14.19
part (e)
contin

zero freq $\omega_z = \frac{1}{C_x (R_x - r_{sm})}$

pole freq $\omega_p = \frac{1}{C_x (R_x + g_{m7} R_1 R_2)}$

Note that $g_{m1} g_{m7} R_1 R_2$ is the midband gain

And with R_x a small value

$$\omega_p \approx \frac{1}{C_x (1 + g_{m7} R_2) \cdot R_1}$$

\downarrow \downarrow
 $r_{o2} \parallel r_{o7}$ $r_{o2} \parallel r_{o4}$
Miller multiplied cap. Theremun Resist. of the

Note that

$\omega_z \rightarrow +\infty$ if $R_x \approx r_{sm}$

We should find an expression for r_{sm} from (**) on pg 14.

through binomial expansions.
This will yield an answer close to $\frac{1}{g_{m7}}$.


Scanned by CamScanner

16

Colpitts Oscillator

Sedra 13.21

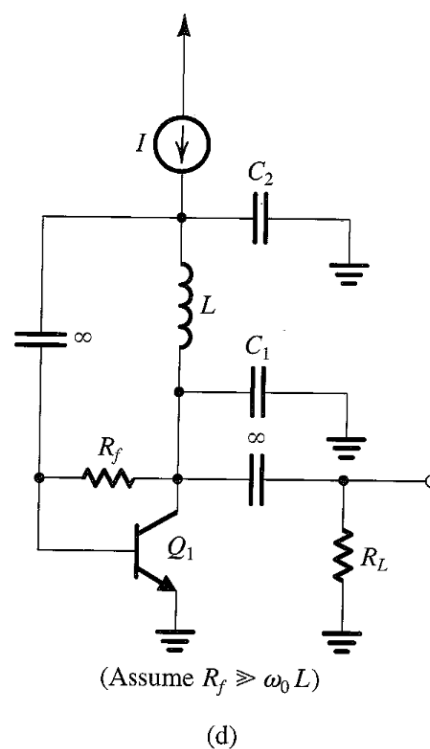****13.21** Figure P13.21 shows four oscillator circuits of the Colpitts type, complete with bias detail. For each circuit, derive an equation governing circuit operation, and find the frequency of oscillation and the gain condition that ensures that oscillations start.




Notes: Draw the small-signal equivalent circuit, omit the output impedance of the transistor, and then analyze.

Additional Tasks: None.


Necessary Knowledge and Skills: Colpitts oscillator, frequency, gain condition for self-starting oscillations.

The circuit in DC (L is short cir.
all cap are open cir.)

Sedra
13.21

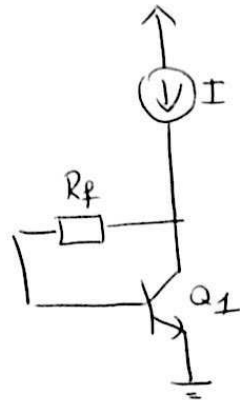

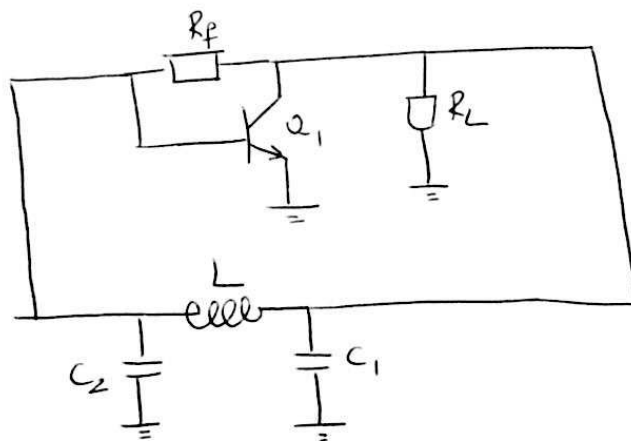
Small signal equivalent cir (C_{∞} are short cir.
 I (current source) is open cir.)




Note L and R_f come in parallel.
But we are given that $R_f \gg \omega_0 L$
Then $R_f \parallel (j\omega_0 L) \approx j\omega_0 L$
 $\Rightarrow R_f$ can be treated as open cir.

See the related document for
analyzing LC networks in RF osc.

Sedra 13.21
contin.

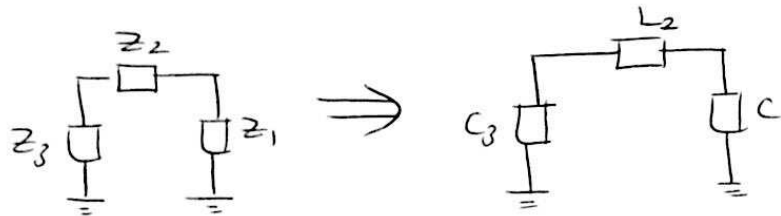

in our case

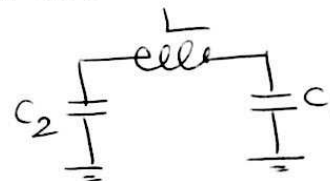

$$\omega_0 = \frac{1}{\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

$$g_m R_L \geq \frac{C_2}{C_1}$$

gain condition
for self-starting osc.



