



GEBZE TEKNİK ÜNİVERSİTESİ- MÜHENDİSLİK FAKÜLTESİ

ELEKTRONİK MÜHENDİSLİĞİ

ELM 331 – Elektronik II


Bonus Ödevler

Mete Can GAZİ

141024020

Homework Bonus 3 : THD (total harmonic distribution) nedir? THD katsayıları nelerdir?

Distorted Waveform :

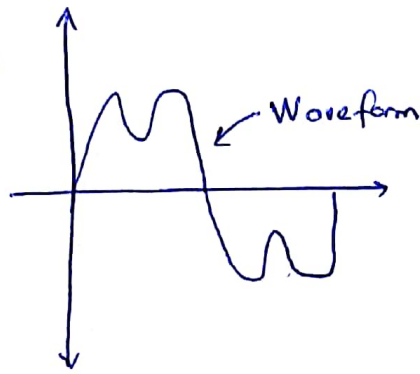

For example :

60Hz is fundamentals wave form.

2nd harmonic component 120Hz

3rd " " 180Hz

4th " " 240Hz

⋮

For $V_{olt(rms)}$ \rightarrow $THD = \frac{\sqrt{\sum_{n=2}^{\infty} V_n^2}}{V_1} \cdot 100\%$

V_1 \leftarrow Fundamentals Frequency's Amplitude

other frequency Amplitude

For Watt \rightarrow $THD = \sqrt{\frac{\sum_{n=2}^{\infty} P_n}{P_1}} \cdot 100$

Note: $V_{rms} = \frac{V_{pk}}{\sqrt{2}}$

Homework Bonus 4: CH12'den 2 soru

Soru 1 (Soru 75 - Design Problem): We wish to design the transimpedance amplifier depicted Fig 12.101 for a closed-loop gain of $1\text{ k}\Omega$. Assume each transistor carries a collector bias current of 1 mA , $\beta = 100$, $V_A = \infty$ and R_F is very large.

a) Determine the values of R_C and R_M for open-loop gain and an open loop gain output impedance of 500Ω .

b) Compute the required value of R_F

c) Closed loop output/input impedance?

$$\begin{aligned} \text{a) Open loop gain} &= R_C (g_{m2} R_M) \\ &= 20\text{ k}\Omega \end{aligned}$$

$$f_{m2} = \frac{I}{V_T} = \frac{1\text{ mA}}{26\text{ mV}} = 38.5\text{ mS}$$

$$R_C, R_M = \frac{20\text{ k}\Omega}{38.5\text{ mS}} \Rightarrow$$

$$\begin{aligned} R_M &= 500\Omega \\ R_C &= 1040\Omega \end{aligned}$$

Open loop output impedance = R_M

$$R_M = 500\Omega$$

b) closed loop gain:

$$\frac{20\text{ k}\Omega}{1 + \frac{20\text{ k}\Omega}{R_F}} = 1\text{ k}\Omega$$

$$R_F = 1053\Omega$$

$$\begin{aligned} \text{c) Closed loop input impedance: } &\frac{\frac{1}{38.5\text{ mS}}}{1 + \frac{20\text{ k}\Omega}{1050\Omega}} = \underline{\underline{1.3\Omega}} \end{aligned}$$

$$\text{output: } 500\Omega \left(\frac{1}{20} \right) = \underline{\underline{25\Omega}}$$

Soln 2 (Soln 76): Design the circuit illustrated in Fig. 12.105 for an open-loop voltage gain of 20, an open loop output impedance of $2k\Omega$, and a closed loop voltage gain of 4. Assume $\lambda = 0$, is the solution unique? If not, how should the circuit parameters be chosen to minimize power dissipation?

$$\text{open-loop voltage gain} = \frac{R_{D1}}{\frac{1}{g_{m1}} + R_1 \parallel R_2} \cdot [g_{m2} (R_1 \parallel R_2)] = 20$$

$$\text{close-loop gain} = \frac{20}{1 + 20 \left(\frac{R_2}{R_1 + R_2} \right)} = 4 \rightarrow \frac{R_2}{R_1 + R_2} = 0.2$$

voltage divider

$$0.2 R_1 + 0.2 R_2 = R_2$$

$$R_1 + R_2 = 2k\Omega$$

$$R_2 = 0.4k\Omega \quad R_1 = 1.6k\Omega$$

$$\frac{R_{D1}}{\frac{1}{g_{m1}} + 2k\Omega} [g_{m2} \times 320\Omega] = 20$$

$$\frac{g_{m1} R_{D1}}{1 + 2k\Omega g_{m1}} \times g_{m2} = 0.0625$$

$$\boxed{g_{m1} = g_{m2}} = 20\text{mS}$$

$$R_{D1} = 6400\Omega = 6.4k\Omega$$

Homework Bonus 5: Which type of feedback is good for which type amplifier?


Answer with explanation?

Pozitif feedback sistemlerinde gain çok yüksektir. Kuracağımız sistemde band genişliğinden çok kazanç önemli ise, bu tip yükseltgeçlere pozitif feedback eklenmelidir.

Negatif feedback sistemlerinde gain düşük olmasına rağmen band genişliği yüksektir ve bunun yanında daha stabildir. Sistemlerimizde bu özelliklere ihtiyaç varsa yükselteç'e negative feedback eklenmelidir.

Homework Bonus 6:

1) Current - Series Feedback

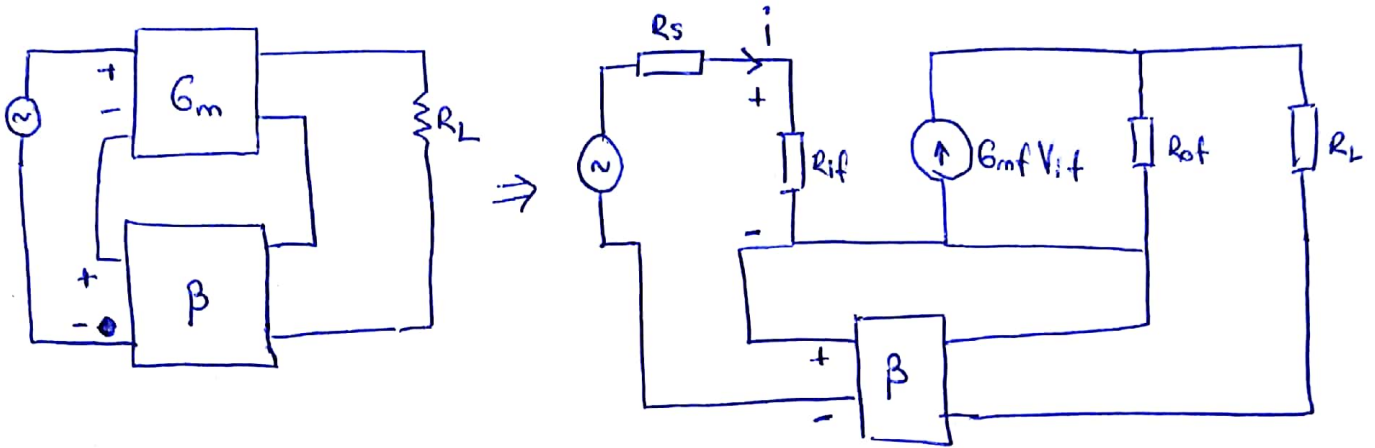



$$G_{mf} = \left. \frac{i_o}{V_{if}} \right|_{R_L=0} = \frac{i_o}{v_i + v_f} = \frac{G_m v_i}{(1 + \beta G_m) v_i} = \frac{G_m}{1 + \beta G_m}$$

$$R_{if} = \left. \frac{V_{if}}{i_i} \right|_{R_L=0} = \frac{v_i + v_f}{i_i} = \frac{(1 + \beta G_m) v_i}{i_i} = (1 + \beta G_m) R_i$$

$$R_{of} = \left. \frac{V_o}{i_o} \right|_{R_L=V_o, V_{if}=0} = \frac{i_i \cdot R_o}{i_o} = \frac{(i_o + G_m v_i) R_o}{i_o} = \frac{(i_o + G_m \beta i_o) R_o}{i_o}$$

$$R_{of} = (1 + \beta G_m) R_o$$

2) Shunt - Shunt Configuration

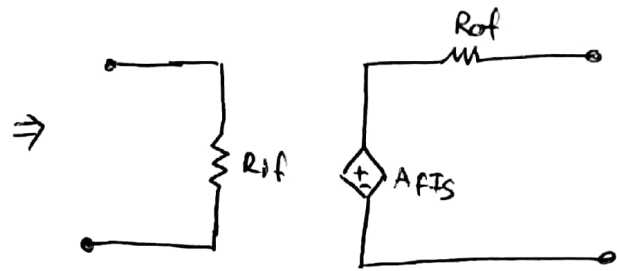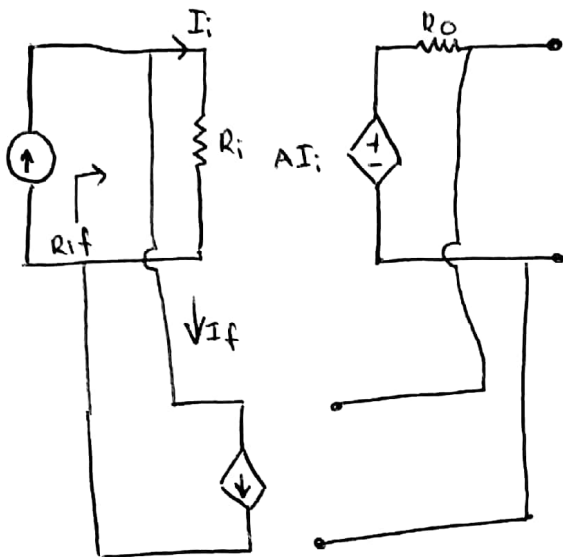


$$A_f = \frac{V_o}{I_s} = \frac{A}{1 + A\beta}$$

$$R_{if} = R_i / (1 + A\beta)$$

$$R_{of} = R_o / (1 + A\beta)$$

Homework Buss 7: CE amplifier with OCTC

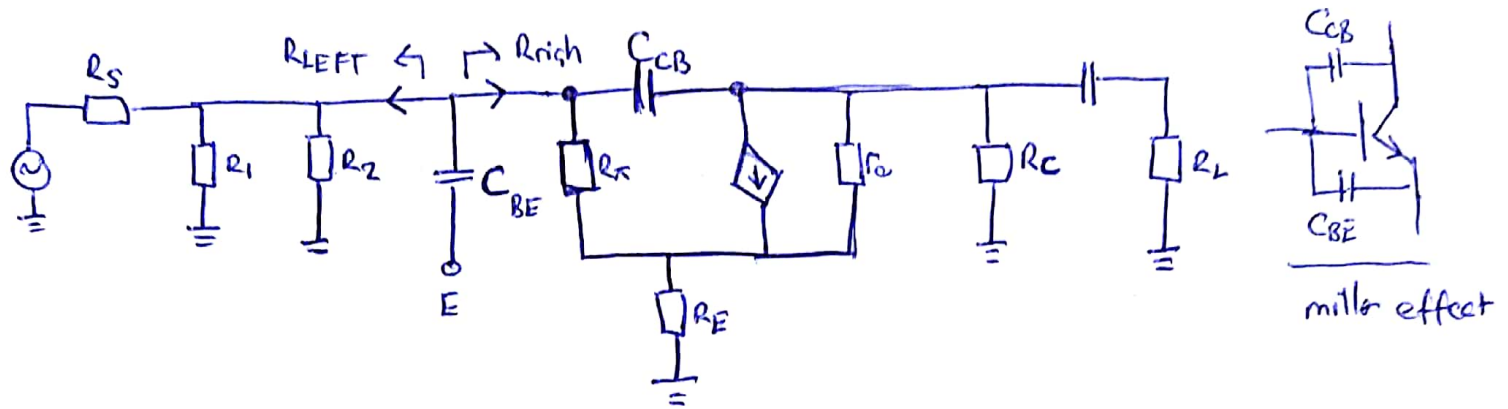

$$C_{BE} \text{ sees } \rightarrow \underbrace{R_1 \parallel R_2 + R_S}_{R_{EFT}} + \underbrace{R_E \cdot R_C + r_o \cdot R_E (1 + g_m r_\pi)}_{R_{right}} \rightarrow \text{using derivations documents}$$

$$\tau_{CBE} = C_{BE} \cdot R_{CBE}$$

$$C_{CB} \text{ sees } \rightarrow [R_S + R_1 \parallel R_2] + [R_C \parallel (r_o + R_E)]$$

$$\tau_{CCB} = C_{CB} \cdot R_{CCB}$$

$$\omega_H = \frac{1}{\tau_{CCB}} + \frac{1}{\tau_{CBE}}$$

