



GTU
Electronics Engineering

ELEC 331
Electronic Circuits 2

Fall Semester

Instructor: Assist. Prof. Önder Şuvak

HW 7
Questions and Answers

Updated November 17, 2017 - 12:56

Assigned:

Due:

Answers Out:

Late Due:

Contents

| | |
|--------------------|-----------|
| Title Page | 1 |
| Contents | 1 |
| Question 1 | 2 |
| Question | 2 |
| Solution | 3 |
| Question 2 | 5 |
| Question | 5 |
| Solution | 6 |
| Question 3 | 7 |
| Question | 7 |
| Solution | 8 |
| Question 4 | 9 |
| Question | 9 |
| Solution | 11 |
| Question 5 | 13 |
| Question | 13 |
| Solution | 14 |

Effects of Feedback on Distortion

Sedra 8.20

D8.20 A particular amplifier has a nonlinear transfer characteristic that can be approximated as follows:


- (a) For small input signals, $|v_I| \leq 10 \text{ mV}$, $v_O/v_I = 10^3$
- (b) For intermediate input signals, $10 \text{ mV} \leq |v_I| \leq 50 \text{ mV}$, $v_O/v_I = 10^2$
- (c) For large input signals, $|v_I| \geq 50 \text{ mV}$, the output saturates

If the amplifier is connected in a negative-feedback loop, find the feedback factor β that reduces the factor-of-10 change in gain (occurring at $|v_I| = 10 \text{ mV}$) to only a 10% change. What is the transfer characteristic of the amplifier with feedback?

Notes: None.

Additional Tasks: None.

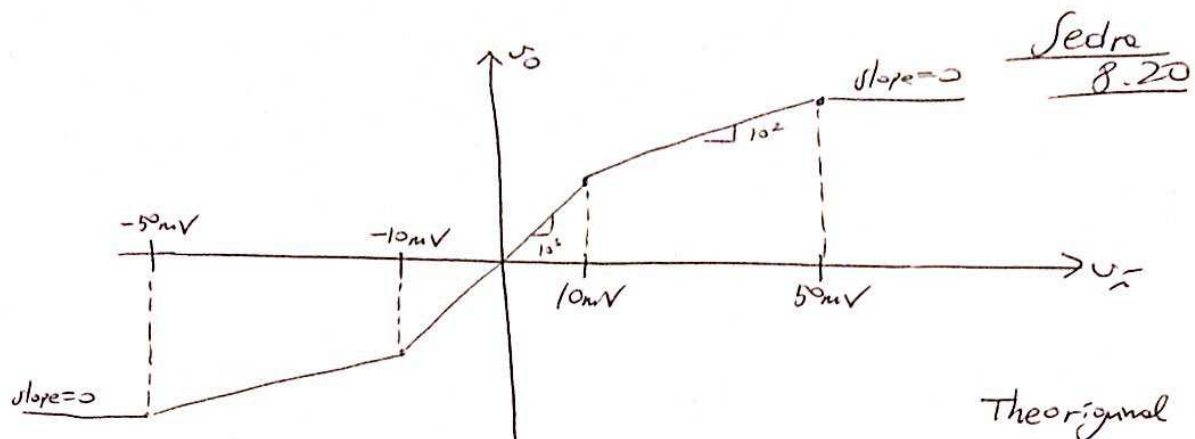Necessary Knowledge and Skills: Gain calculations for a feedback amplifier.



$$\text{Let } A_1 = 10^3$$

$$A_2 = 10^2$$

with feedback

$$A_{1,f} = \frac{A_1}{1 + A_1 \beta}$$

$$A_{2,f} = \frac{A_2}{1 + A_2 \beta}$$

} the same feedback factor β needs to be used.

With feedback, we will still have

$$A_{1,f} > A_{2,f}$$

It is required that we have

$$A_{1,f} = A_{2,f} (1 + 10\%)$$

$$\frac{A_1}{1 + A_1 \beta} = \frac{A_2}{1 + A_2 \beta} (1.1) \Rightarrow \text{solve for } \beta$$

$$\frac{10^3}{1 + 10^3 \beta} = \frac{10^2}{1 + 10^2 \beta} (1.1)$$

Sedra
8.20
contin.

$$10(1 + 100\beta) = (1 + 1000\beta)1.1$$

$$10 + 1000\beta = 1.1 + 1100\beta$$

$$8.9 = 100\beta$$


$$\beta = \frac{8.9}{100}$$

$$\text{then } A_{1,f} = \frac{10^3}{1 + 10^3 \frac{8.9}{10^2}} = \frac{1000}{90} = 11.1$$

$$A_{2,f} = \frac{10^2}{1 + 10^2 \frac{8.9}{10^2}} = \frac{100}{9.9} \approx 10.101$$

10% difference

The new (and old) VTC

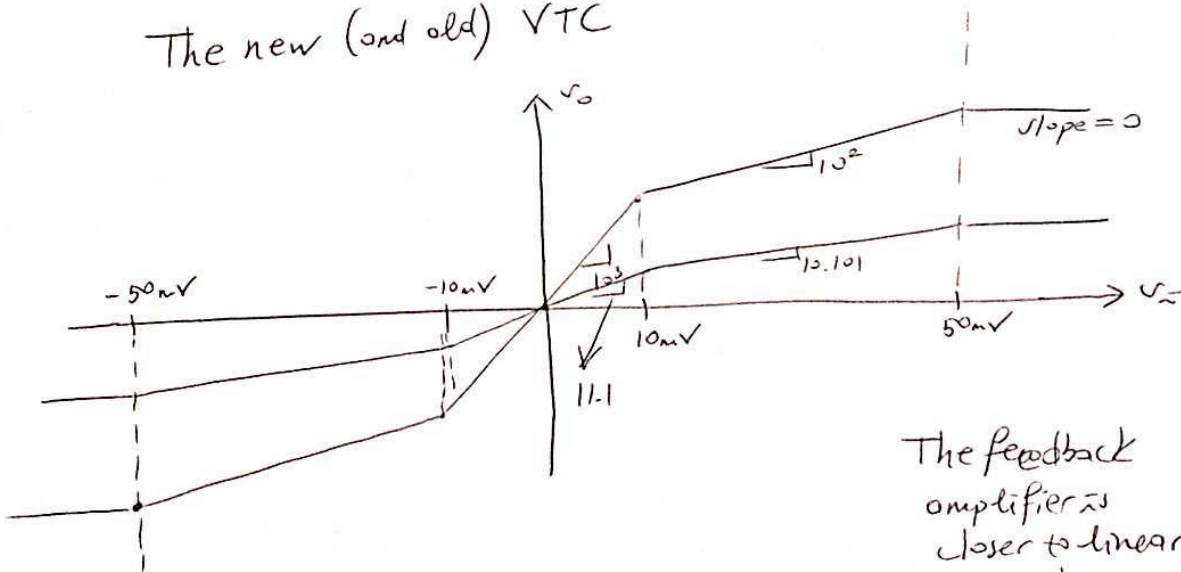

The feedback amplifier is closer to linear (almost has a uniform gain at all ranges of input.)

Note: Such VTC graphs as above need to be interpreted as in:

- The component of the input $\leq 10 \text{ mV}$ gets $A_1 (A_{1,f})$ gain
- The component of the input in excess of 10 mV but $\leq 50 \text{ mV}$ obtains $A_2 (A_{2,f})$ gain
- The component of the input in excess of 50 mV obtains no gain.

Scanned by CamScanner (2)

Effects of Feedback on Sensitivities

Rashid 10.5

10.5 A feedback amplifier is to have a closed-loop gain of $A_f = 60$ dB and a sensitivity of 10% to the open-loop gain A . Determine the open-loop gain with a unity feedback $\beta = 1$.

Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: Effects of feedback on sensitivities, improvement factor.

There is something wrong in the statement of the question, neglect ^{Rashid} the $(\beta=1)$ information. 10.5

$$A_f = 60 \text{ dB in dB}$$

$$20 \log_{10} A_f = 60$$

$$A_f = 1000$$

$$\int_{A_f}^A = \frac{2A_f}{2A} \frac{A}{A_f}$$

$$= \frac{1}{1+\beta A} \underbrace{\int_A^A}_{100\%=1} = \frac{1}{1+A\beta} = 10\% = \frac{1}{10}$$

$$\text{Then } 1 + A\beta = 10 \Rightarrow A\beta = 9$$

$$A_f = \frac{A}{1 + A\beta} = \frac{A}{10} = 1000$$

$$\text{then } A = 10^4$$

$$\text{and } \beta = \frac{9}{A} = \frac{9}{10^4} = 9 \times 10^{-4}$$

Effects of Feedback on Bandwidth**Rashid 10.7**

- 10.7** The feedback factor of an amplifier is $\beta = 0.8$. The open-loop gain A can be expressed in Laplace's domain of s as

$$A(s) = \frac{250s}{(1 + 0.1s)(1 + 0.001s)}$$

Determine **(a)** the closed-loop low-frequency gain A_{of} , **(b)** the closed-loop bandwidth BW, and **(c)** the gain–bandwidth product GBW.

Notes: None.

Additional Tasks: None.


Necessary Knowledge and Skills: Bode plots, transfer functions, low and high frequency cut-off, effects of negative feedback on cut-off frequencies.

Rashed
10.7

$$A(s) = 2500 \frac{s}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{1000}\right)}$$

For computing the midband gain $A(s) \approx 2500 \frac{s}{\left(\frac{s}{10}\right)(1)}$

$$= 2500$$

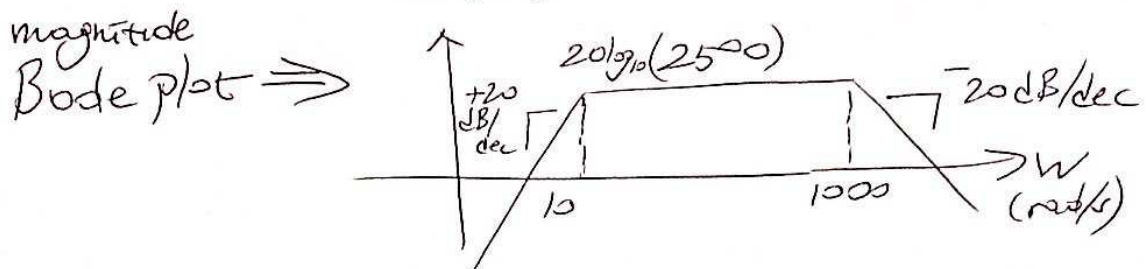

$$1 + G\beta = 1 + 2500 \cdot 0.8 = 2001 = A_{\text{cl}} \left(\begin{array}{l} \text{closed-loop} \\ \text{low-freq} \\ \text{gain} \end{array} \right)$$

$$\text{low freq cut-off} \Rightarrow \frac{10}{1 + G\beta} = \frac{10}{2001} \approx \frac{57}{10000} = 0.005 \text{ rad/sec}$$

$$\text{high freq cut-off} \Rightarrow \frac{1000(1 + G\beta)}{(1000)(2001)} \approx 2 \text{ MHz}$$

$$GBW = 2500 \cdot 1000 = 2.5 \text{ MHz} (\dots)$$

Effects of Feedback on Distortion

Malik 9.9

9.9 Figure P9.9a shows a nonfeedback amplifier of voltage gain A that delivers 5 W to a 5 ohm speaker when the amplifier

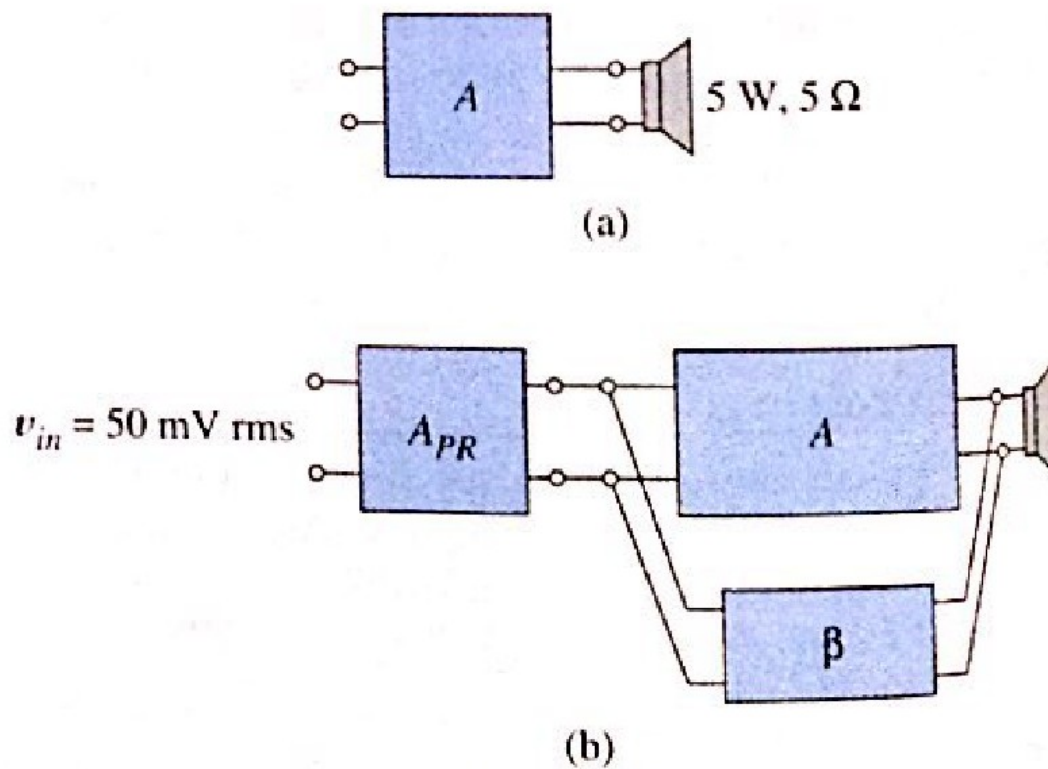


Figure P9.9

Effects of Feedback on Distortion**Malik 9.9**

input voltage is 50 mV rms. The nonlinear distortion in the amplifier output is 1% of the output signal value.

- (a) Find the numerical value of the gain A .
- (b) Find the value of β required in Fig. P9.9b to reduce the distortion to 0.1%, with the same output signal amplitude.
- (c) Find the value of gain A_{PR} required in the preamp.

Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: Effects of feedback on distortion, improvement factor, distortion reduction, preamplification (low distortion).

Mohit K
9.9

$$\frac{V_{out, RMS}^2}{R_L} = P_{out, rms}$$

$$V_{out, RMS} = \sqrt{5W \cdot 5\Omega}$$

$$= 5V_{rms}$$

$$\text{Gain } A = \frac{V_{out, RMS}}{V_{in, RMS}}$$

$$= \frac{5V_{rms}}{50mV_{rms}} = 100$$

The gain of both configurations should be the same.

$$A_{PR} \cdot \frac{A}{1 + A\beta} = A$$

A_{PR} : gain of the preamplifier
 $\frac{A}{1 + A\beta}$: gain of the amplifier with feedback
 A : gain of the ~~second~~ first configuration

gain of the ~~first~~ second configuration

$$\text{Therefore } A_{PR} = 1 + A\beta$$

A_{PR} is a low gain value, then this pre-amplifier can be designed to have almost no distortion.

Molrik
9.9
contin.

$$\text{Distortion}_2 = \frac{\text{Distortion}_1}{1 + A\beta}$$

$$0.1\% = \frac{1\%}{1 + A\beta}$$

$$\text{then } 1 + A\beta = 10$$

$$A\beta = 9$$

$$\beta = \frac{9}{A} = \frac{9}{100} = 0.09$$

$$A_{PR} = 1 + A\beta = 10$$

} the ampli with this gain does not introduce distortion

$$\frac{A}{1 + A\beta} = \frac{100}{10} = 10$$

} this ampli introduces 0.1% distortion for an output of 5V, rms.

Effects of Feedback**Malik 9.14**

9.14 For an amplifier with shunt feedback, $R_{if} = 110 \Omega$, $R_o = 2 \text{ k}\Omega$, $R_{of} = 26 \text{ k}\Omega$, $A_f = 20$, $\omega_H = 10^4 \text{ rad/s}$ and $\omega_{L,f} = 10 \text{ rad/s}$.

(a–e) Find R_i , A , β , $\omega_{H,f}$, and ω_L .

(f) Changing a resistor in amplifier A from $10 \text{ k}\Omega$ to $11 \text{ k}\Omega$ changes A_f from 20 to 21. Use sensitivity to find the new value of A .

Notes: None.

Additional Tasks: None.

Necessary Knowledge and Skills: Effects of feedback on I/O impedances, gain, and cut-off frequencies, sensitivities.

Mohit
9.14

$$\text{shunt feedback} \Rightarrow \frac{R_i}{1 + \beta A} = R_{if}$$

where R_i is the input impedance without feedback

R_{if} is the input imp. with feedback

A is the forward gain

β is the feedback factor

$(1 + \beta A)$ is the improvement factor

We are not yet sure if
current-shunt or
voltage-shunt
feedback is employed.

$R_o = 2\text{ k}\Omega$
 $R_{of} = 26\text{ k}\Omega$ } output impedance increased with current feedback.

Therefore, indeed, current-shunt feedback is employed.
This is a current amplifier with current shunt feedback. A and β are unitless.

$$(1 + A\beta) R_o = R_o f$$

$$1 + A\beta = 13$$

$$A\beta = 12$$

Marks
9.14
contin.

$$A_f = \frac{A}{1 + A\beta} = 20 \Rightarrow A = \underbrace{(1 + A\beta)}_{13} \underbrace{A_f}_{20} = 260 \text{ (unitless)}$$

$$\beta = \frac{12}{A} = \frac{12}{260} \text{ (unitless)}$$

$$w_{H,f} = w_H (1 + A\beta) = (10^4 \text{ rad/s})(13) = 1.3 \times 10^5 \text{ rad/sec}$$

$$w_L = w_{L,f} (1 + A\beta) = (10 \text{ rad/s})(13) = 130 \text{ rad/sec}$$

$$\begin{aligned} \text{unity gain frequency} &\approx A_f \cdot w_{H,f} \\ \text{(or G.B.W) product} &= A \cdot w_H = \frac{A}{(1 + A\beta)} (w_H)(1 + A\beta) \\ &= 260 \cdot 10^4 = 2.6 \times 10^6 \text{ rad/sec} \end{aligned}$$

We know from
sensitivity
calculations

$$S_P^{Af} = \frac{S_P^A}{1 + \beta A}$$

Malik
9.14
contin.

Then we have

$$S_P^{Af} \approx \frac{\frac{\Delta Af}{Af}}{\frac{\Delta P}{P}} = \frac{1}{1 + \beta A} \frac{\frac{\Delta A}{A}}{\frac{\Delta P}{P}} \approx S_P^A \frac{1}{1 + \beta A}$$

$$\frac{\Delta Af}{Af} = \frac{1}{1 + \beta A} \frac{\Delta A}{A}$$

$$\frac{(21-20)}{20} = \frac{1}{13} \frac{\Delta A}{260}$$

$$\Delta A = 260 \frac{13}{20} = 169$$

$$A_{\text{new}} = A + \Delta A = 260 + 169 = 429$$

Note that $A: 260 \rightarrow 429$ (65% change)

while $A_f: 20 \rightarrow 21$ (5% change)

